

## Water Resources - Experiment #1


### Appendix 2: Signal Conditioning Circuit - with op-amp

The glass electrode is but one component of our pH sensing system. Sensor systems generally include, in addition to a *transducer* (the glass electrode), a *signal conditioning* component, a *data transmission* component and, back home, a *data readout/storage* subsystem. We are concerned here with our signal conditioning subsystem.

Because the output impedance of the glass electrode is so high, perhaps on the order of  $10^{10}$  ohms, the device, considered as a voltage source, would be “loaded down” by any ordinary readout device presenting lower impedance - e.g., our digital voltmeter - and hence the voltage the latter displayed would not be a true measure of *pH*.

To ensure we do get a true reading, we use an operational amplifier (“op-amp”) that presents a high impedance, much higher than that even of the electrode, to the electrode’s output. In this case, the op-amp will draw very little current - in fact we assume it draws none - so the input to the op-amp will be the true voltage. The circuit is designed such that the output of the op-amp is equal to its input and delivers adequate current to our digital voltmeter, readout. How this works we now attempt to explain.

A schematic of the signal conditioning circuit is shown in the figure. To understand its function we note first that an op-amp, in open loop mode (no feedback loop) has enormous gain - on the order of  $10^5$  or  $10^6$ . That is, if the voltage difference between the noninverting and inverting inputs differs from zero - say the noninverting voltage input exceeds the voltage at the inverting input then  $V_{out}$  will grow positive - big time<sup>1</sup>. (Actually it will grow until it reaches the supply voltage of +4.5 volts and be nailed there). Conversely, if the noninverting voltage input drops below the voltage at the inverting input -  $V_{out}$  will grow negative, big time.

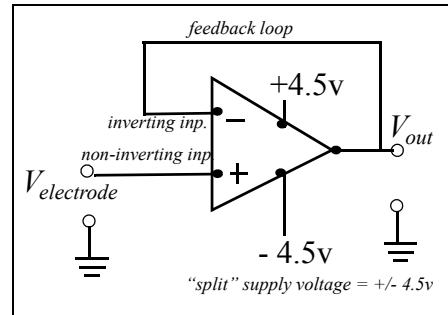

Now consider what happens with the feedback loop in place - connecting the output to the inverting input - so that  $V_{out}$  is held to the voltage at the inverting input. (The resistance of the feedback line is taken as zero). If the voltage at the *noninverting* input differs from the voltage at the *inverting* input - say it increases relative to the latter - then  $V_{out}$  will increase due to the op-amp’s gain. But it can’t increase “big time” because once it, and consequently the inverting input voltage, reaches the voltage at the *noninverting* input, growth must cease for any further increase would produce a *noninverting* voltage dropping below the voltage at the inverting input and  $V_{out}$  would

---

1. The labeling of the two inputs to the op-amp as “inverting” and “noninverting” will be explained in time.

Roughly speaking, the output of the op-amp is out of phase with an inverting input by  $180^\circ$  while the noninverting input is in phase with the output. The plus and minus signs do *not* mean that a negative voltage must be supplied to the inverting input, nor a positive voltage to the non-inverting input.

correspondingly decrease. The result is that for changing  $V_{electrode}$  the output voltage “follows” the input voltage<sup>1</sup>.



$$V_{out} = V_{electrode}$$

Since the op-amp presents such a high impedance to the glass electrode (in fact the argument above assumed infinite impedance) the  $V_{electrode}$  is truly  $V_{electrode}$  and we have successfully conditioned our raw signal as presented by our transducer.


---

1. An op-amp used in this way is called a “follower”. Ref: P. Horowitz, W. Hill, *The Art of Electronics*, Cambridge University Press, 1980, p. 176 (1999 edition).

Circuit board layout.

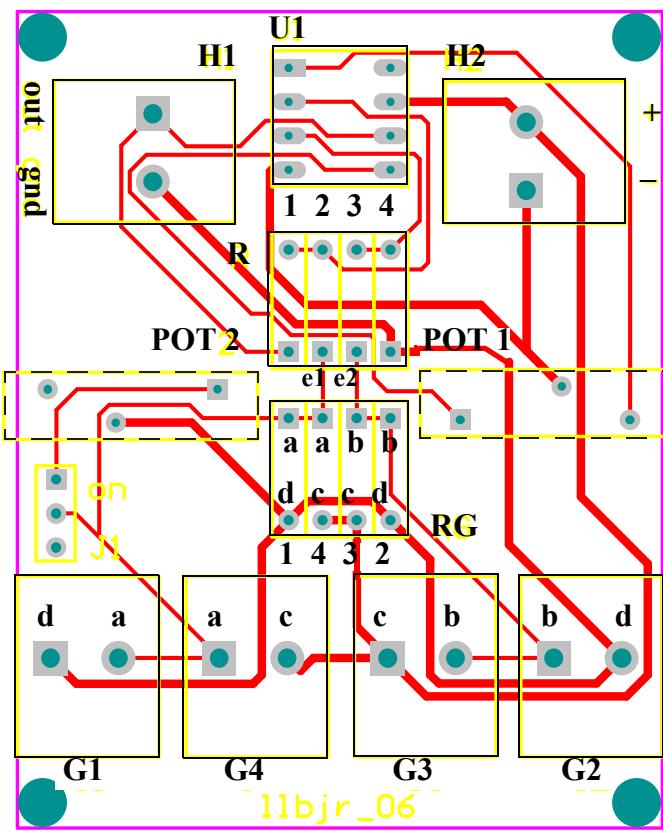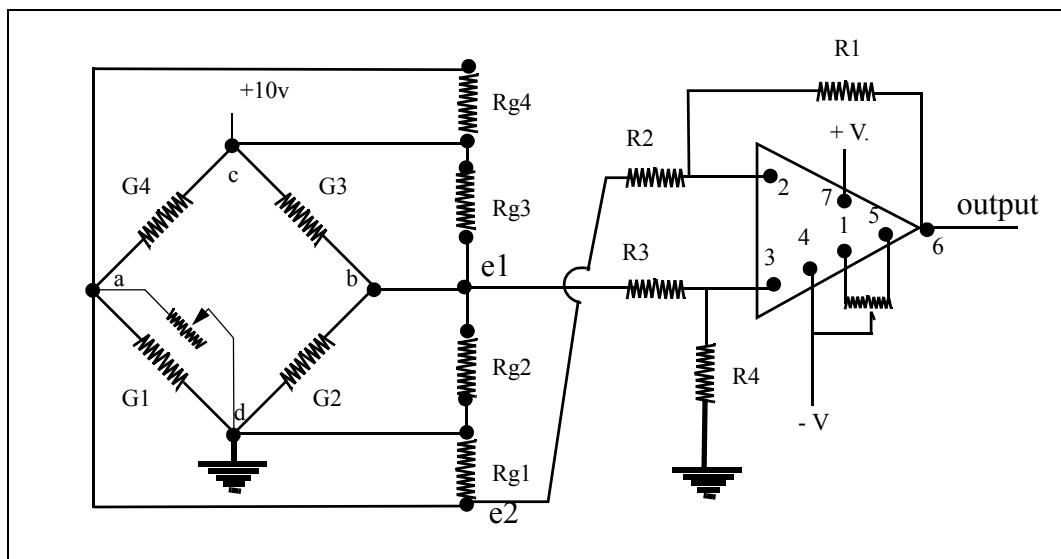

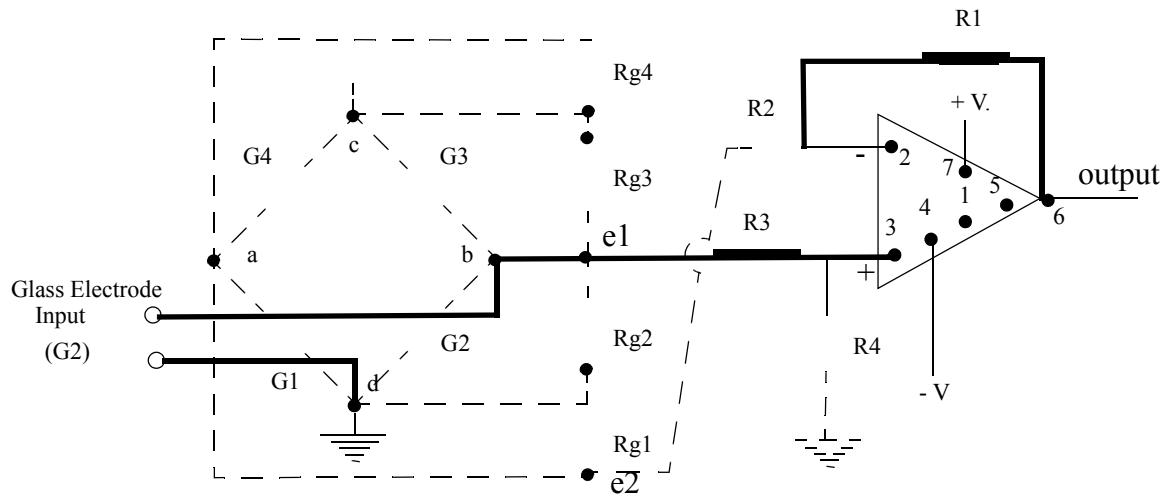Top figure is circuit diagram as it would appear in a text book. The bottom figure is the printed circuit board layout. (Overwritten to make readable).



The above shows the signal conditioning circuit for use with the Glass Electrode. The full circuit, including the “bridge” will be used in the structure’s lab.