Massachusetts Institute of Technology Department of Electrical Engineering and Computer Science 6.012 Microelectronic Devices and Circuits Homework #4

Problem 1

Consider the CMOS inverter pictured below. Take channel length modulation into account.



Parameter	NMOS	PMOS
V _{TO}	0.5 V	-0.5 V
μ	220 cm ² /Vs	110 cm ² /Vs
λ	0.1 V ⁻¹	0.1 V ⁻¹
Tox	15 nm	15 nm

\bullet Dimensions of W and L are in μm

- a) Calculate V_M , the voltage midpoint.
- b) Calculate A_V , the voltage gain at $V_{IN}=V_M$.
- c) Calculate N_{ML} and N_{MH} , the noise margin low and noise margin high.
- d) Calculate t_{PHL} and t_{PLH}, the propagation delay from high-to-low and propagation delay from low-to-high.

Problem 2

We will now use the following SPICE model and compare our hand calculations from Problem 1 with simulated results.

.MODEL N15 NMOS LEVEL=1 VT0=0.5 TOX=1.5e-8 U0=220 LAMBDA=1.0e-1 +GAMMA=0.6 CJ=1e-4 CJSW=5e-10 PB=0.95 .MODEL P15 PMOS LEVEL=1 VT0=-0.5 TOX=1.5e-8 U0=110 LAMBDA=1.0e-1 +GAMMA=0.6 CJ=3e-4 CJSW=3.5e-10 PB=0.9

- a) Use the DC sweep on the input voltage to simulate transfer characteristics using SPICE. Compare V_M, A_V, N_{ML}, N_{MH}, with the calculated results.
- b) Use the Pulse input to simulate an input waveform shown below using SPICE. Compare t_{PHL} and t_{PLH} with your hand calculations.



Problem 3

Consider the circuit below, which consists of an NMOS device and PMOS current source load.

- a) Calculate the width of the PMOS device so its saturation current is 50μ A.
- b) Calculate V_M , V_{OH} , V_{OL} . Remember, for hand calculations we assume $V_{OH}=V_{MAX}$, and $V_{OL}=V_{MIN}$.
- c) Calculate the voltage gain of this circuit, when $V_{IN}=V_{M}$.
- d) Calculate V_{OUT} when $V_{IN}=3$.



6.012 Microelectronic Devices and Circuits Spring 2009

For information about citing these materials or our Terms of Use, visit: http://ocw.mit.edu/terms.