



6.776

High Speed Communication Circuits
Lecture 10
Noise Modeling in Amplifiers

Michael Perrott
Massachusetts Institute of Technology
March 8, 2005

Copyright © 2005 by Michael H. Perrott

Notation for Mean, Variance, and Correlation

- Consider random variables x and y with probability density functions $f_x(x)$ and $f_y(y)$ and joint probability function $f_{xy}(x,y)$
 - Expected value (mean) of x is

$$\bar{x} = E(x) = \int_{-\infty}^{\infty} x f_x(x) dx$$

- Note: we will often abuse notation and denote \bar{x} as a random variable (i.e., noise) rather than its mean
 - The variance of x (assuming it has zero mean) is

$$\overline{x^2} = E(x^*x) = \int_{-\infty}^{\infty} x^*x f_x(x) dx$$


- A useful statistic is

$$\overline{xy} = E(xy) = \int_{-\infty}^{\infty} xy f_{xy}(x, y) dx dy$$


- If the above is zero, x and y are said to be uncorrelated

Relationship Between Variance and Spectral Density

Two-Sided Spectrum

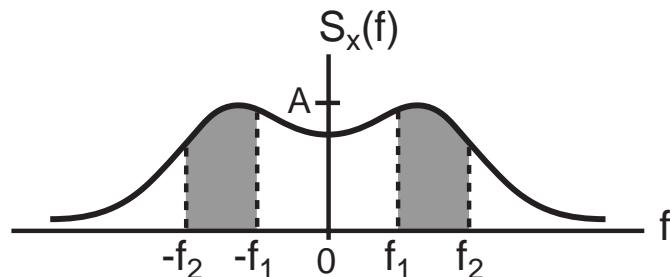

One-Sided Spectrum

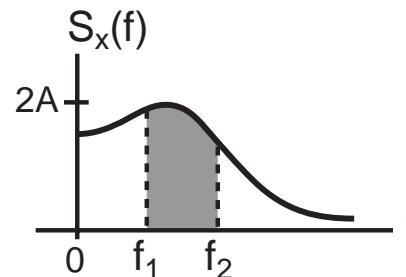


- **Two-sided spectrum**

$$\overline{x^2} = \int_{-f_2}^{-f_1} S_x(f) df + \int_{f_1}^{f_2} S_x(f) df$$

- Since spectrum is symmetric $\Rightarrow \overline{x^2} = 2 \int_{f_1}^{f_2} S_x(f) df$

- **One-sided spectrum defined over positive frequencies**
 - Magnitude defined as twice that of its corresponding two-sided spectrum
- In the next few lectures, we assume a one-sided spectrum for all noise analysis

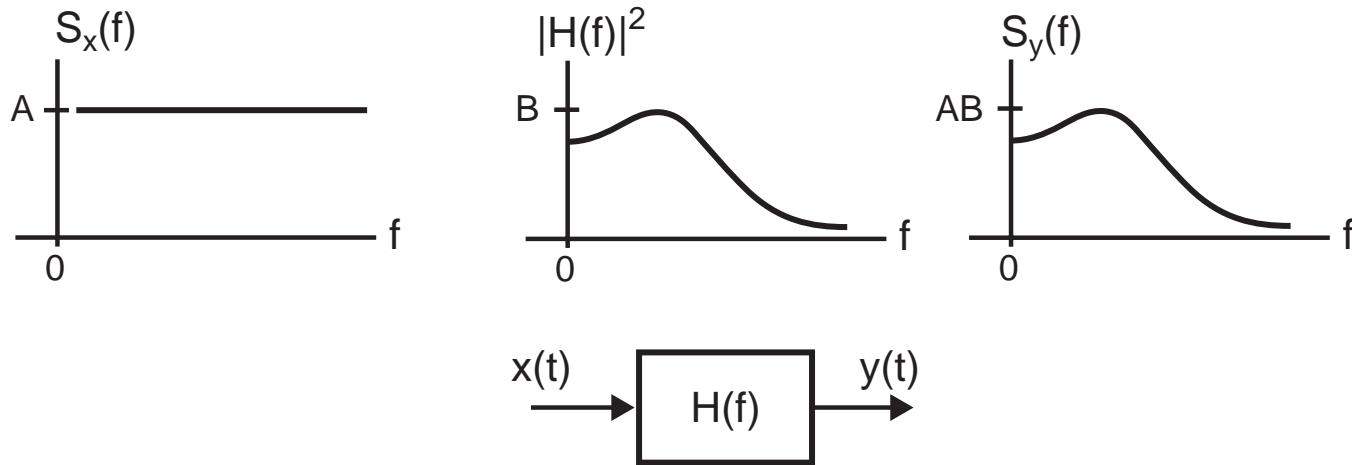The Impact of Filtering on Spectral Density



- For the random signal passing through a linear, time-invariant system with transfer function $H(f)$



$$S_y(f) = |H(f)|^2 S_x(f)$$

- We see that if $x(t)$ is amplified by gain A , we have

$$S_y(f) = A^2 S_x(f) \Rightarrow \overline{y^2} = A^2 \overline{x^2}$$

Noise in Resistors

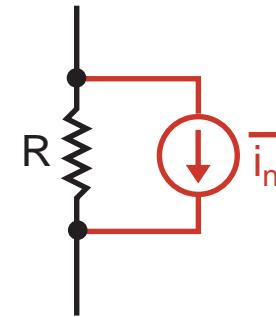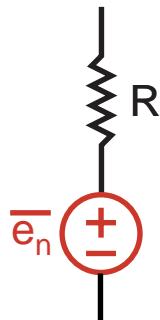- Can be described in terms of either voltage or current



$$\overline{e_n^2} = 4kT R \Delta f$$

$$\overline{i_n^2} = 4kT \frac{1}{R} \Delta f$$

- k is Boltzmann's constant


$$k = 1.38 \times 10^{-23} J/K$$

- T is temperature (in Kelvins)
 - Usually assume room temperature of 27 degrees Celsius

$$\Rightarrow T = 300K$$


Noise In Inductors and Capacitors

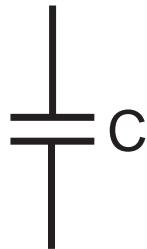- Ideal capacitors and inductors have no noise!



- In practice, however, they will have parasitic resistance
 - Induces noise
 - Parameterized by adding resistances in parallel/series with inductor/capacitor
 - Include parasitic resistor noise sources

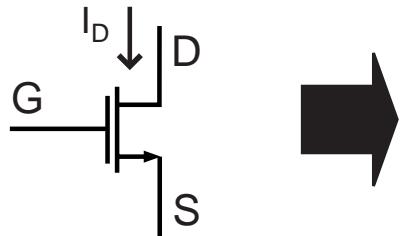Noise in CMOS Transistors (Assumed in Saturation)




Transistor Noise Sources

Drain Noise (Thermal and 1/f)

Gate Noise (Induced and Routing Parasitic)

- **Modeling of noise in transistors must include several noise sources**
 - **Drain noise**
 - Thermal and 1/f – influenced by transistor size and bias
 - **Gate noise**
 - Induced from channel – influenced by transistor size and bias
 - Caused by routing resistance to gate (including resistance of polysilicon gate)
 - Can be made negligible with proper layout such as fingering of devices

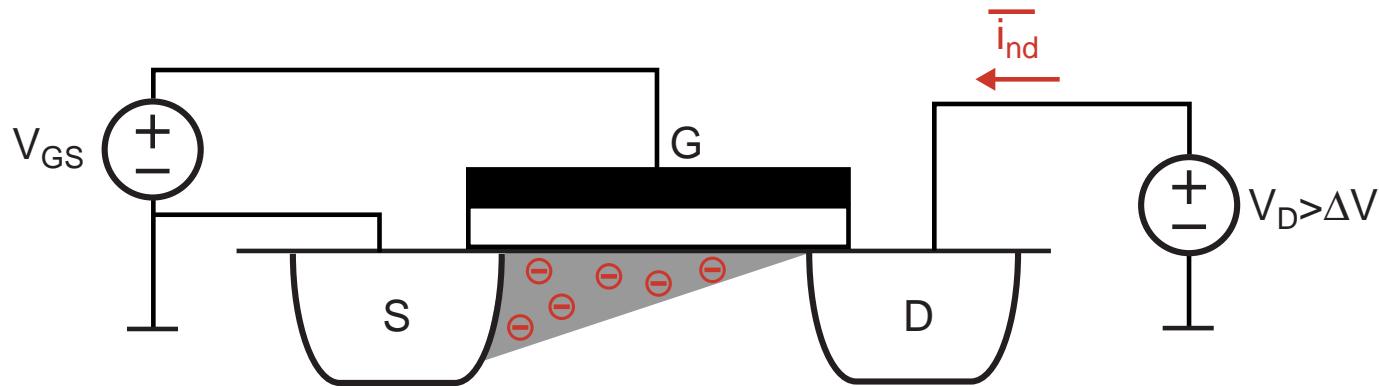
Drain Noise – Thermal (Assume Device in Saturation)




- Thermally agitated carriers in the channel cause a randomly varying current

$$\overline{i_{nd}^2} \Big|_{th} = 4kT\gamma g_{do}\Delta f$$

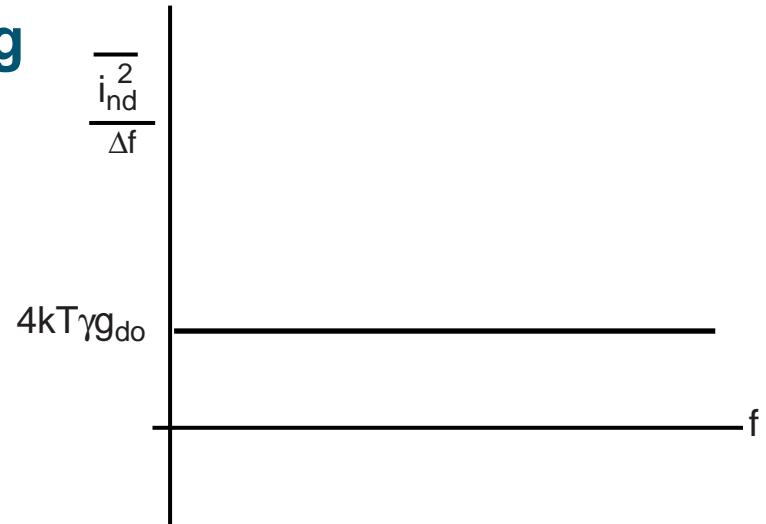- γ is called excess noise factor
 - = 2/3 in long channel
 - = 2 to 3 (or higher!) in short channel NMOS (less in PMOS)
- g_{do} will be discussed shortly (Note: $g_{do} = g_m/\alpha$)



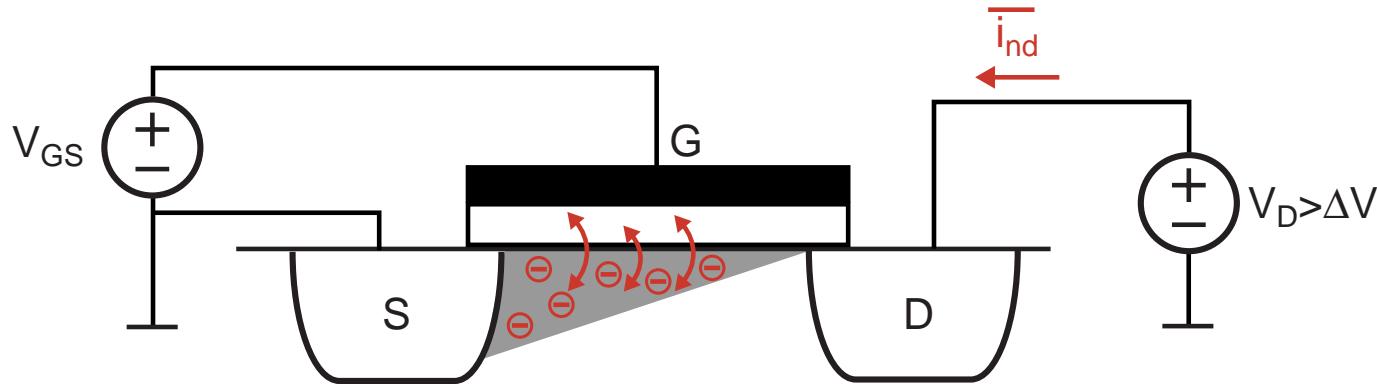
Drain Noise – 1/f (Assume Device in Saturation)




- Traps at channel/oxide interface randomly capture/release carriers

$$\overline{i_{nd}^2} \Big|_{1/f} = \frac{K_f}{f^n} \Delta f \approx \frac{K}{f} \frac{g_m^2}{WLC_{ox}^2} \Delta f$$

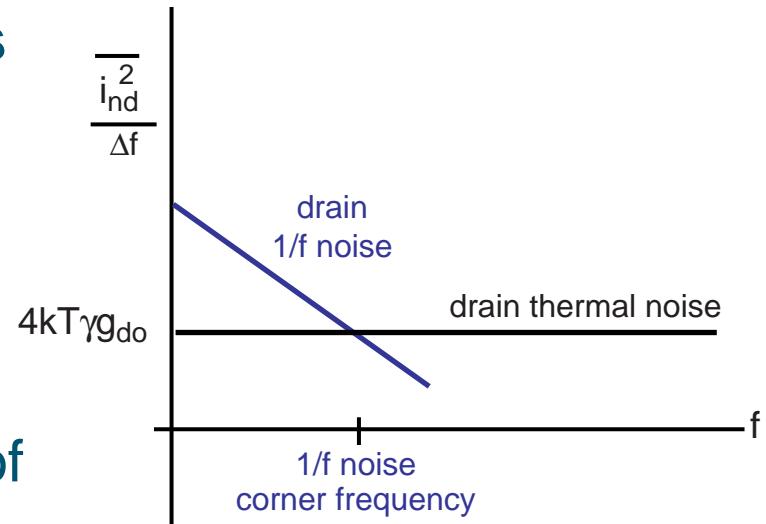- Parameterized by K_f and n
 - Provided by fab (note $n \approx 1$)
 - Currently: K_f of PMOS $\ll K_f$ of NMOS due to buried channel
- To minimize: want large area (high WL)



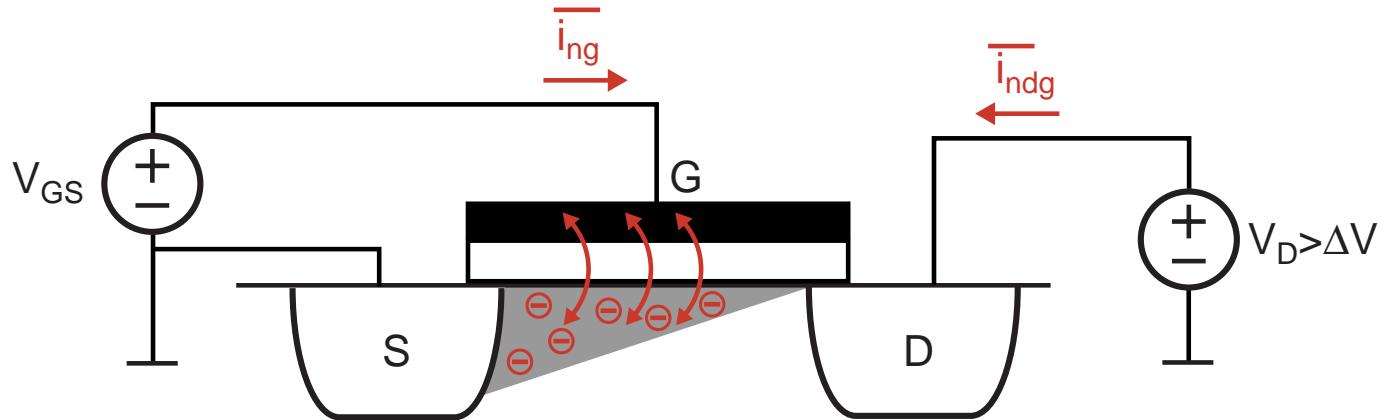
Induced Gate Noise (Assume Device in Saturation)



- Fluctuating channel potential couples capacitively into the gate terminal, causing a noise gate current

$$\overline{i_{ng}^2} = 4kT\delta g_{do} \left(\frac{2\pi f}{\sqrt{5}/\alpha(g_m/C_{gs})} \right)^2 \Delta f$$

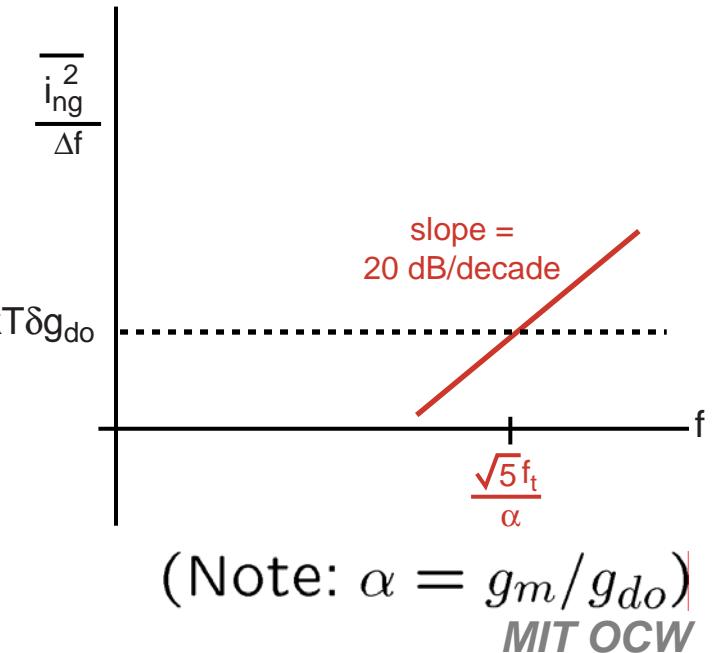- δ is gate noise coefficient
 - Typically assumed to be 2γ
- Correlated to drain noise!



Useful References on MOSFET Noise

- **Thermal Noise**
 - B. Wang et. al., “MOSFET Thermal Noise Modeling for Analog Integrated Circuits”, JSSC, July 1994
- **Gate Noise**
 - Jung-Suk Goo, “High Frequency Noise in CMOS Low Noise Amplifiers”, PhD Thesis, Stanford University, August 2001
 - <http://www-tcad.stanford.edu/tcad/pubs/theses/goopdf.pdf>
 - Jung-Suk Goo et. al., “The Equivalence of van der Ziel and BSIM4 Models in Modeling the Induced Gate Noise of MOSFETS”, IEDM 2000, 35.2.1-35.2.4
 - Todd Sepke, “Investigation of Noise Sources in Scaled CMOS Field-Effect Transistors”, MS Thesis, MIT, June 2002

Drain-Source Conductance: g_{do}

- g_{do} is defined as channel resistance with $V_{ds}=0$
 - Transistor in triode, so that

$$I_d = \mu_n C_{ox} \frac{W}{L} \left((V_{gs} - V_T) V_{ds} - \frac{V_{ds}^2}{2} \right)$$

$$\Rightarrow g_{do} = \left. \frac{dI_d}{dV_{ds}} \right|_{V_{ds}=0} = \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_T)$$

- Equals g_m for long channel devices
- Key parameters for 0.18 μ NMOS devices



$$\mu_n = 327.4 \text{ cm}^2/(V \cdot s)$$

$$t_{ox} = 4.1 \times 10^{-9} \text{ m} \quad \epsilon_o = 3.9(8.85 \times 10^{-12}) \text{ F/m}$$

$$\Rightarrow \mu_n C_{ox} = \mu_n \frac{\epsilon_o}{t_{ox}} = 275.6 \times 10^{-6} \text{ F}/(V \cdot s)$$



$$V_T = 0.48 \text{ V}$$

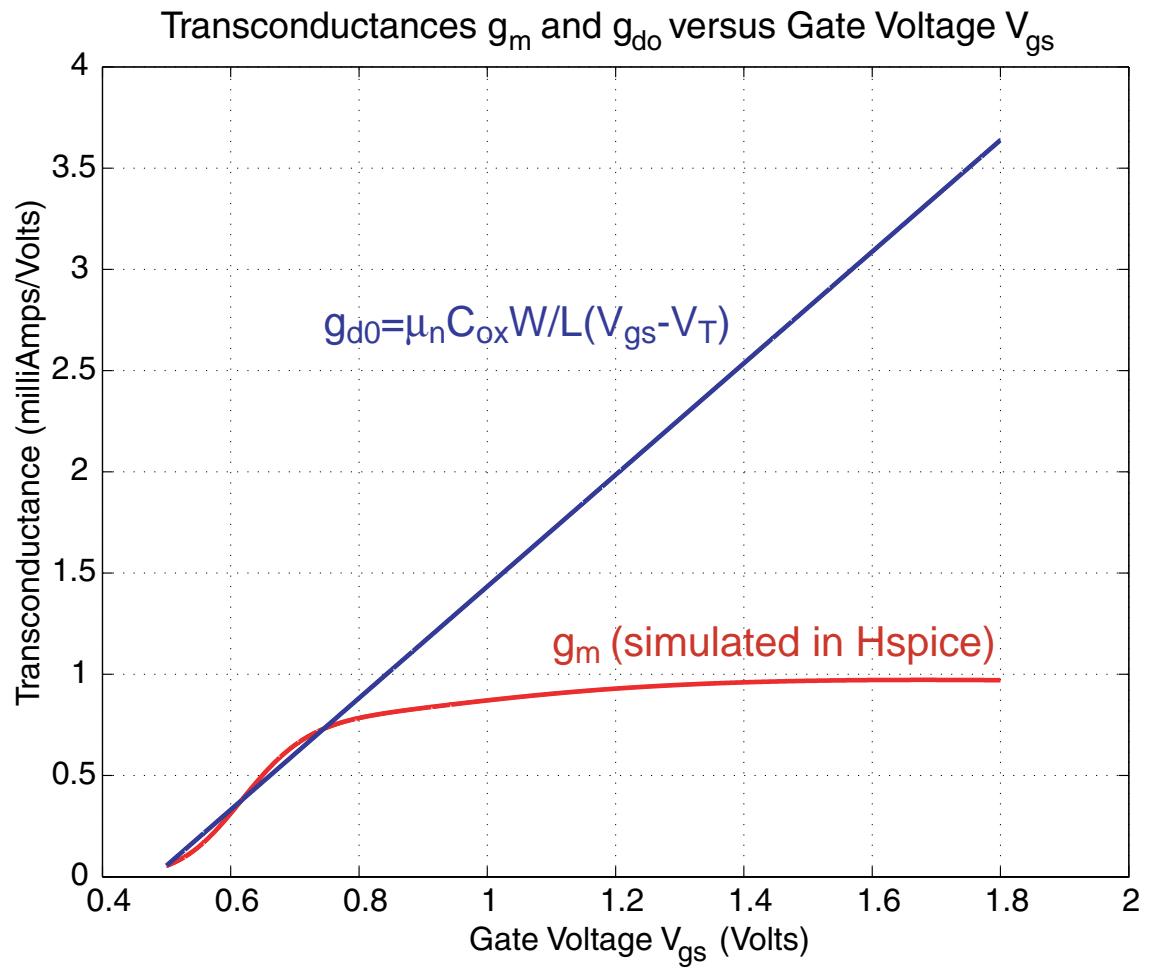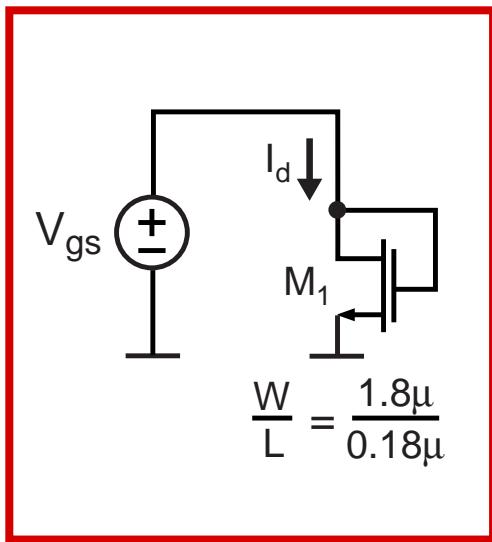Plot of g_m and g_{do} versus V_{gs} for 0.18μ NMOS Device




- For V_{gs} bias voltages around 1.2 V: $\alpha = \frac{g_m}{g_{do}} \approx \frac{1}{2}$

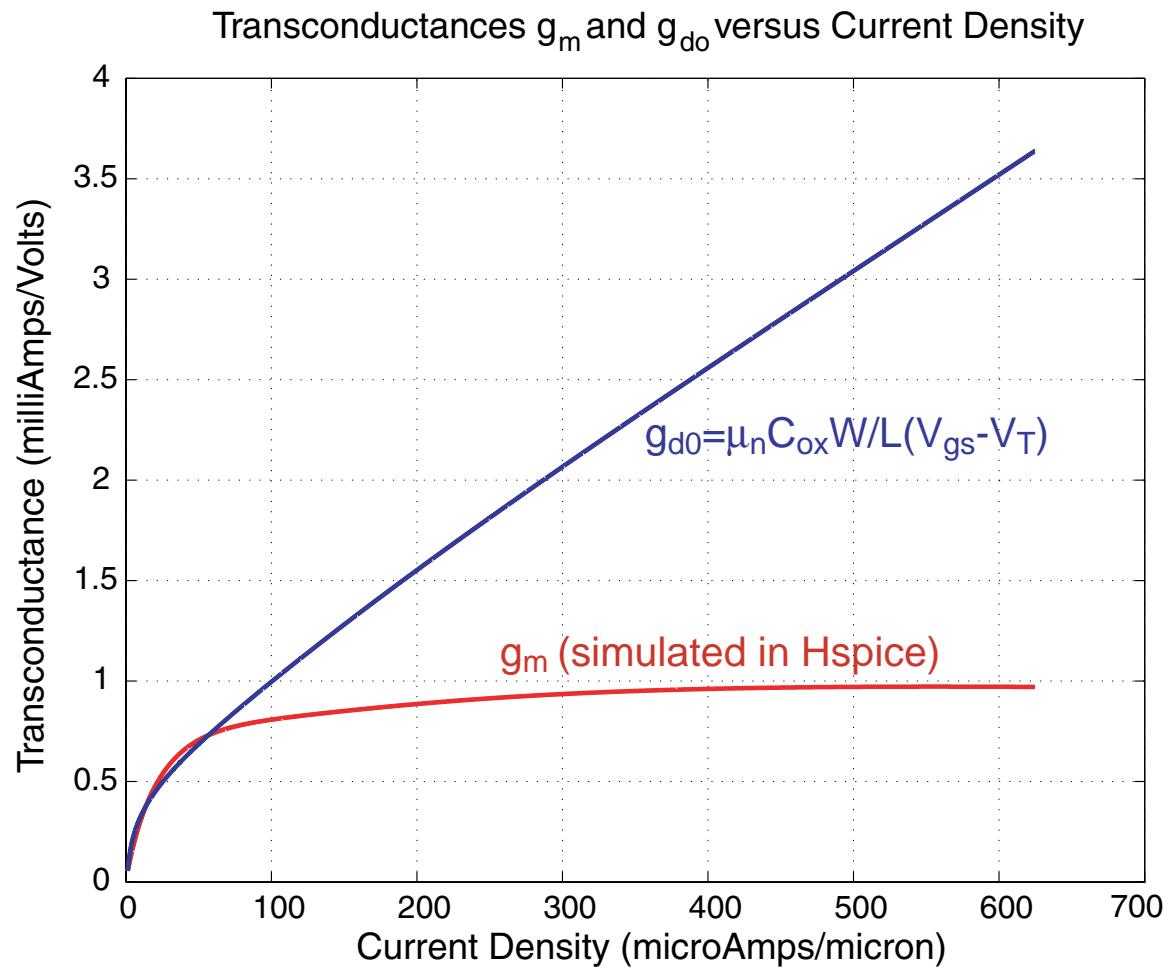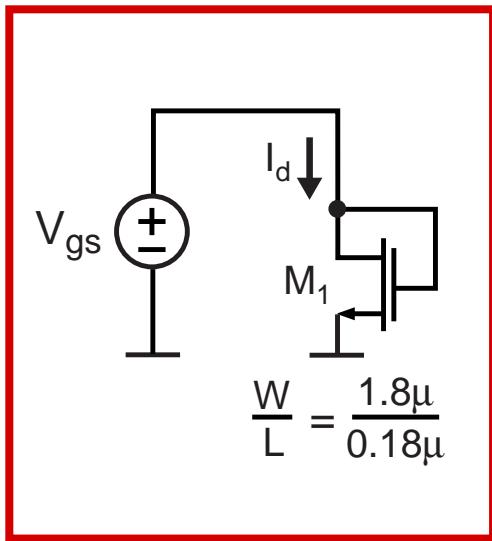Plot of g_m and g_{do} versus I_{dens} for 0.18μ NMOS Device



Noise Sources in a CMOS Amplifier

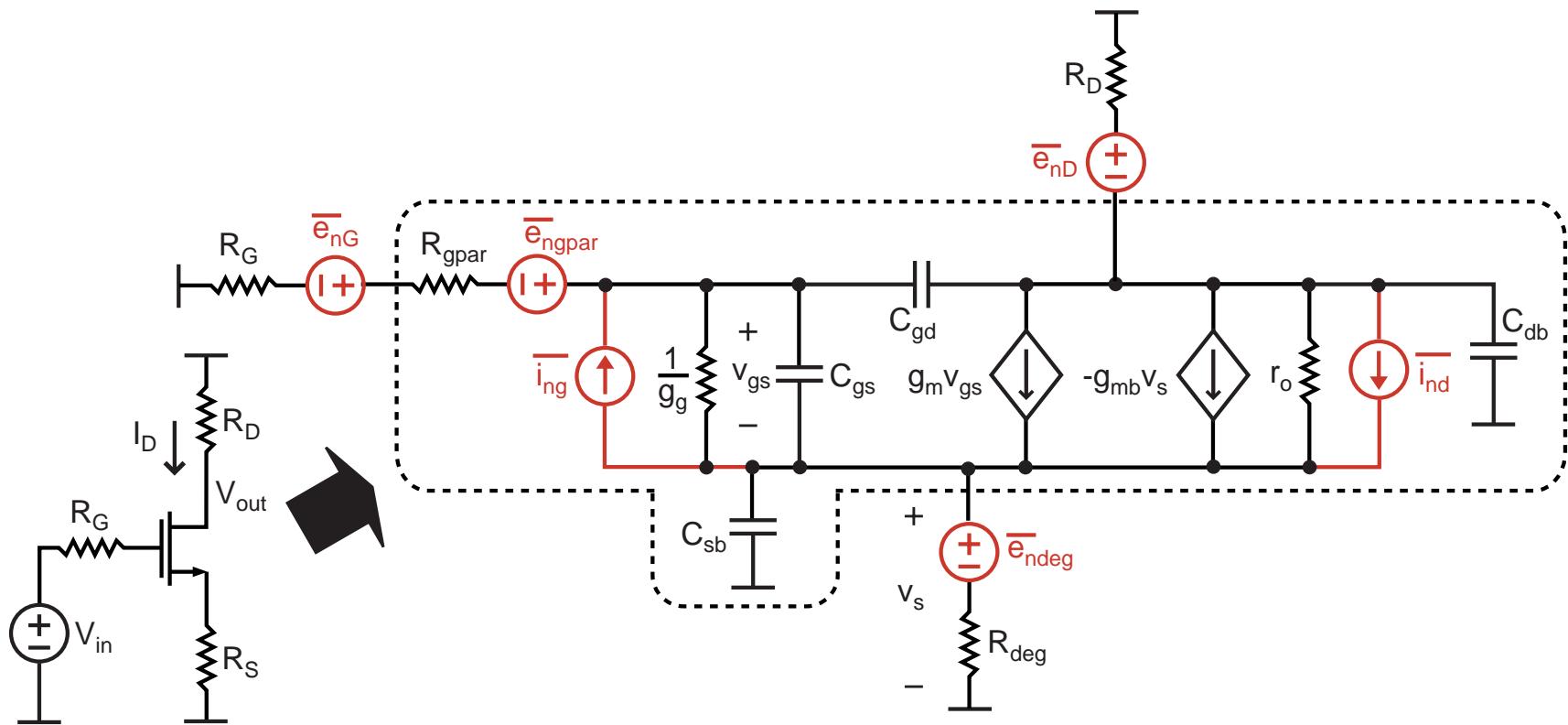

$\overline{e_{nG}}, \overline{e_{nD}}, \overline{e_{ndeg}}$: noise sources of external resistors


$\overline{R_{gpar}}, \overline{e_{ngpar}}$: parasitic gate resistance and its noise

$\overline{i_{ng}}$: induced gate noise,

$\overline{g_g}$: caused by distributed nature of channel $\left(g_g = \frac{w^2 C_{gs}^2}{5 g_{d0}} \right)$

$\overline{i_{nd}}$: drain noise (thermal and 1/f)

Remove Model Components for Simplicity

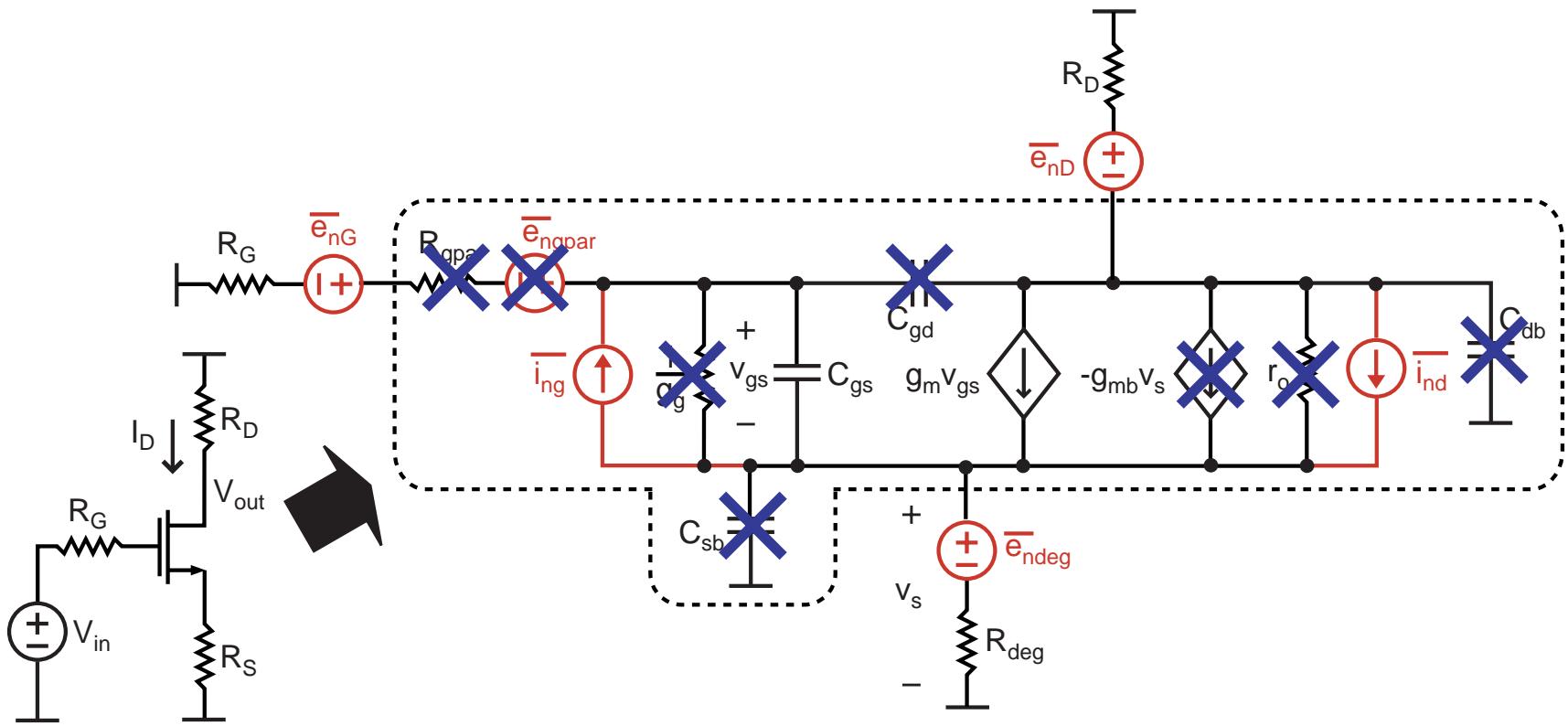

$R_{gpar}, \bar{e}_{ngpar}$: can make negligible with proper layout



g_g : assume to be negligible (for $w \ll w_t$)

$C_{sb}, C_{gd}, C_{db}, g_{mb}$: too painful to include for calculations

r_o : impact is minor since R_D is small (for high bandwidth)

Key Noise Sources for Noise Analysis

$$\overline{e_{nG}^2} = 4kTR_G\Delta f$$

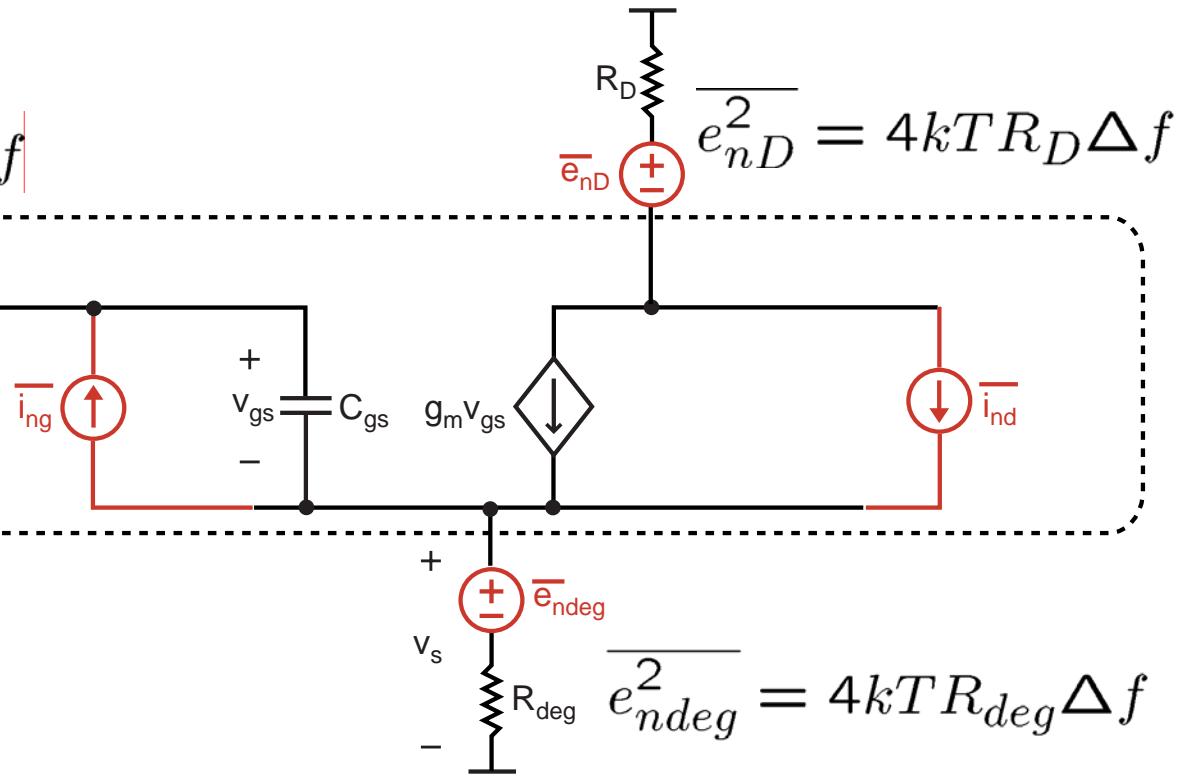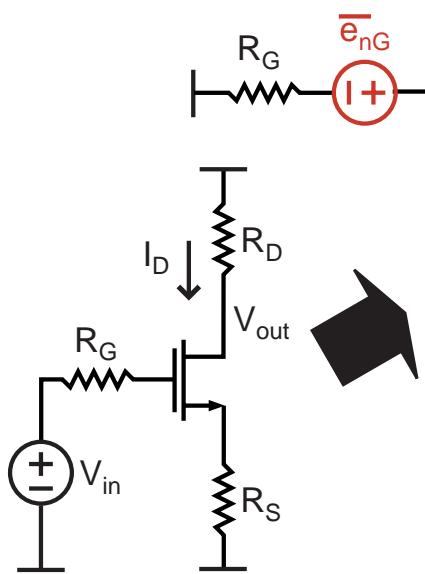

■ Transistor gate noise

$$\overline{i_{ng}^2} = 4kT\delta g_g \Delta f,$$

$$\text{where } g_g = \frac{w^2 C_{gs}^2}{5g_{d0}}$$


■ Transistor drain noise

$$\overline{i_{nd}^2} = 4kT\gamma g_{do} \Delta f + \frac{K_f}{f^n} \Delta f$$

Thermal noise


1/f noise

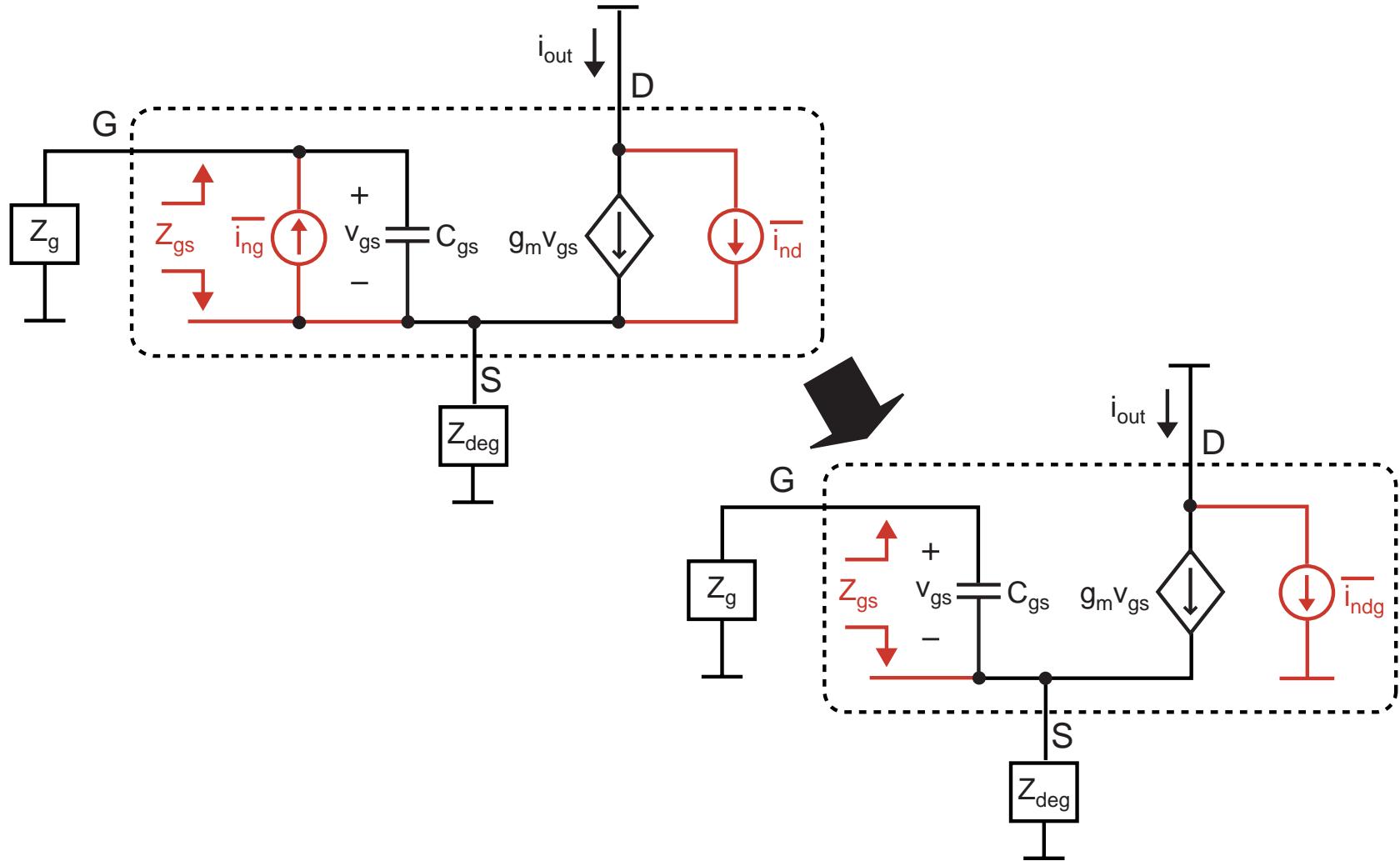Apply Thevenin Techniques to Simplify Noise Analysis




- Assumption: noise independent of load resistor on drain

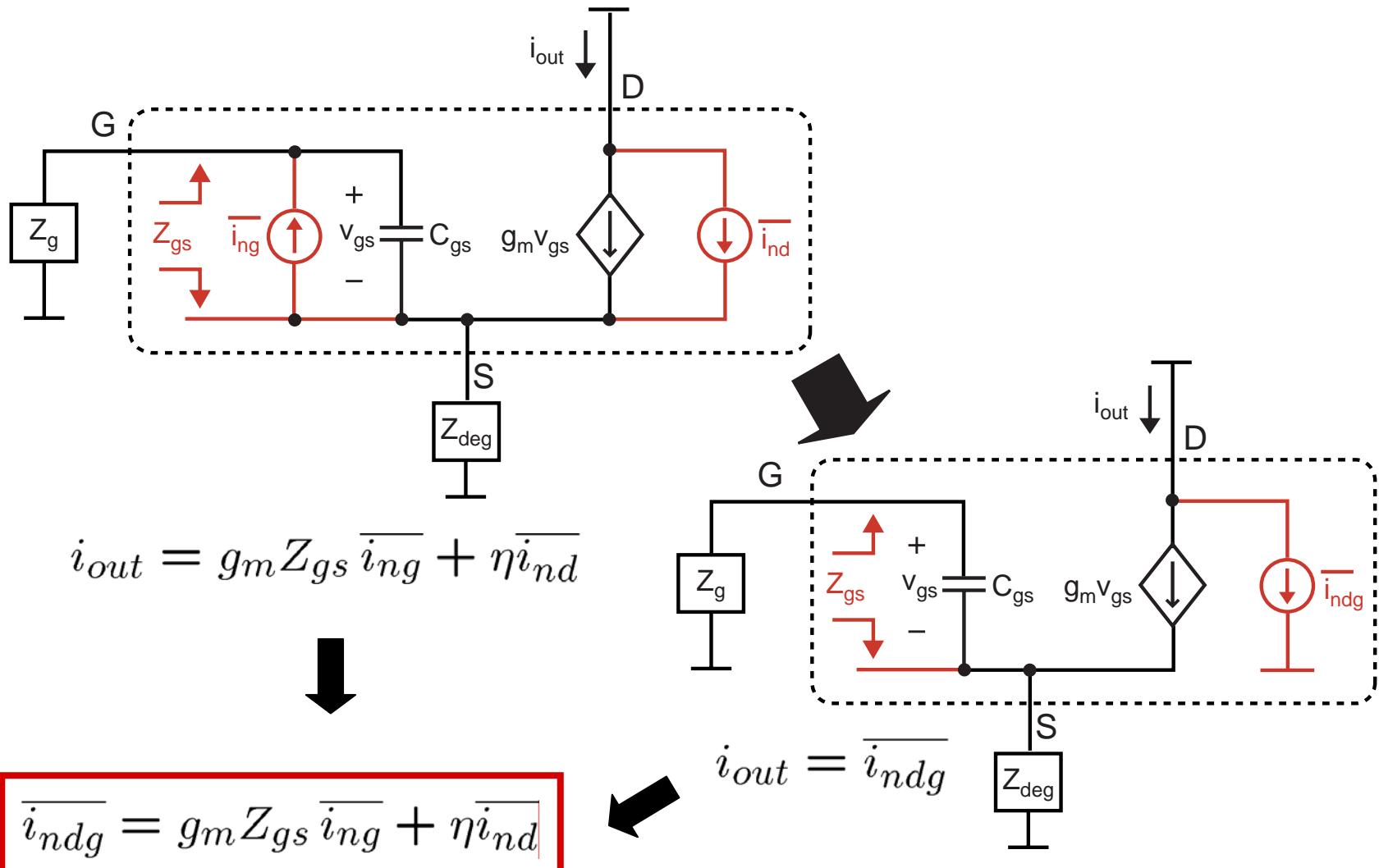Calculation of Equivalent Output Noise for Each Case



Calculation of Z_{gs}

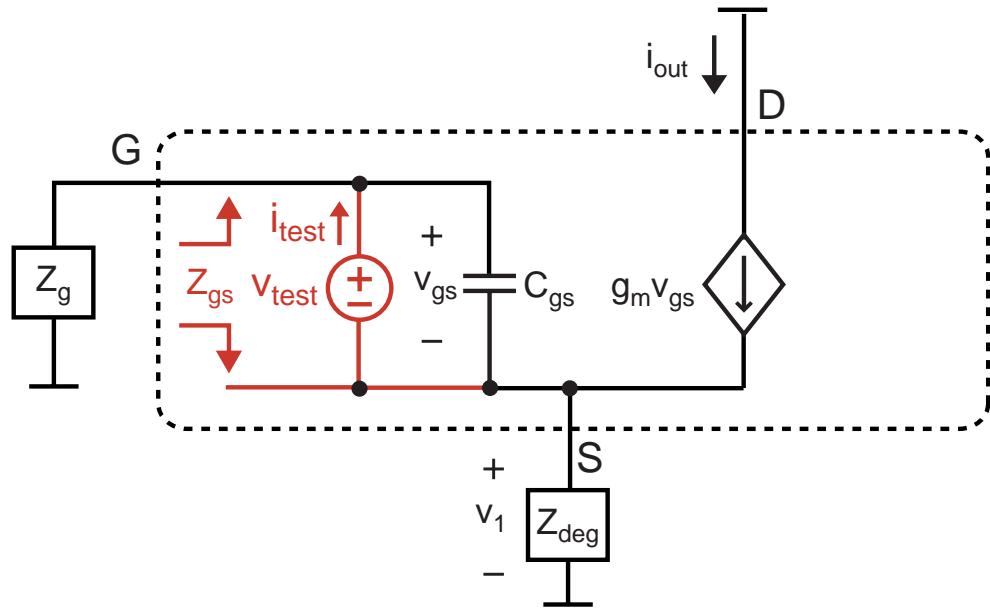

Write KCL equations


$$(1) -i_{test} + \frac{v_{test}}{1/(sC_{gs})} + g_m v_{test} = \frac{v_1}{Z_{deg}}$$

$$(2) \frac{v_{test} + v_1}{Z_g} + \frac{v_1}{Z_{deg}} = g_m v_{test}$$

After much algebra:

$$Z_{gs} = \frac{v_{test}}{i_{test}} = \frac{1}{sC_{gs}} \left| \right| \frac{Z_{deg} + Z_g}{1 + g_m Z_{deg}}$$

Calculation of η

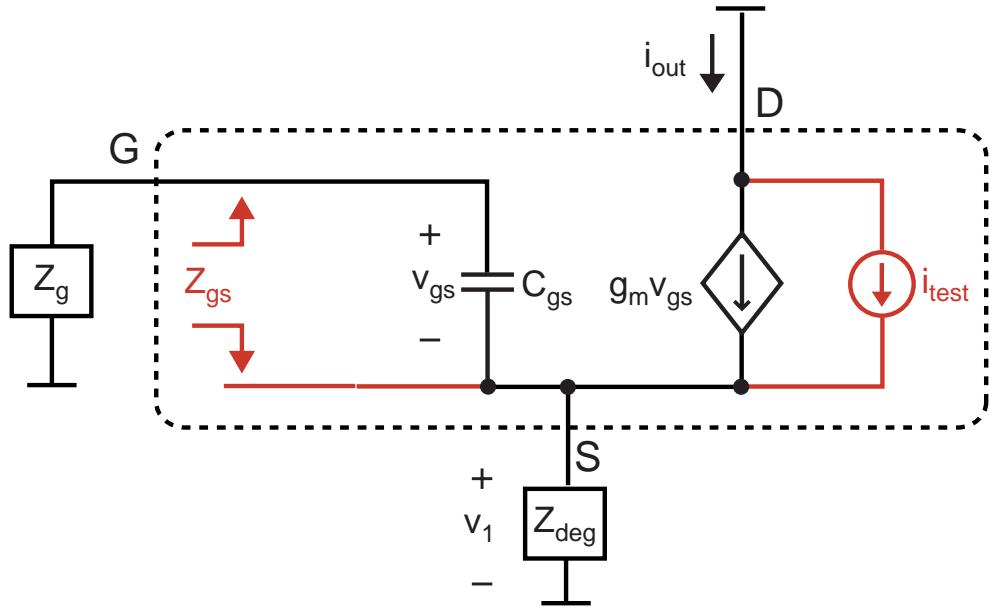

- Determine V_{gs} to find i_{out} in terms of i_{test}


$$(1) i_{out} = i_{test} + g_m v_{gs} \quad (2) v_{gs} = -v_1 \frac{1/(sC_{gs})}{1/(sC_{gs}) + Z_g}$$

$$(3) v_1 = i_{out}(Z_{deg} \parallel (\frac{1}{sC_{gs}} + Z_g))$$

- After much algebra:

$$\eta = \frac{i_{out}}{i_{test}} = \boxed{1 - \left(\frac{g_m Z_{deg}}{Z_{deg} + Z_g} \right) Z_{gs}}$$

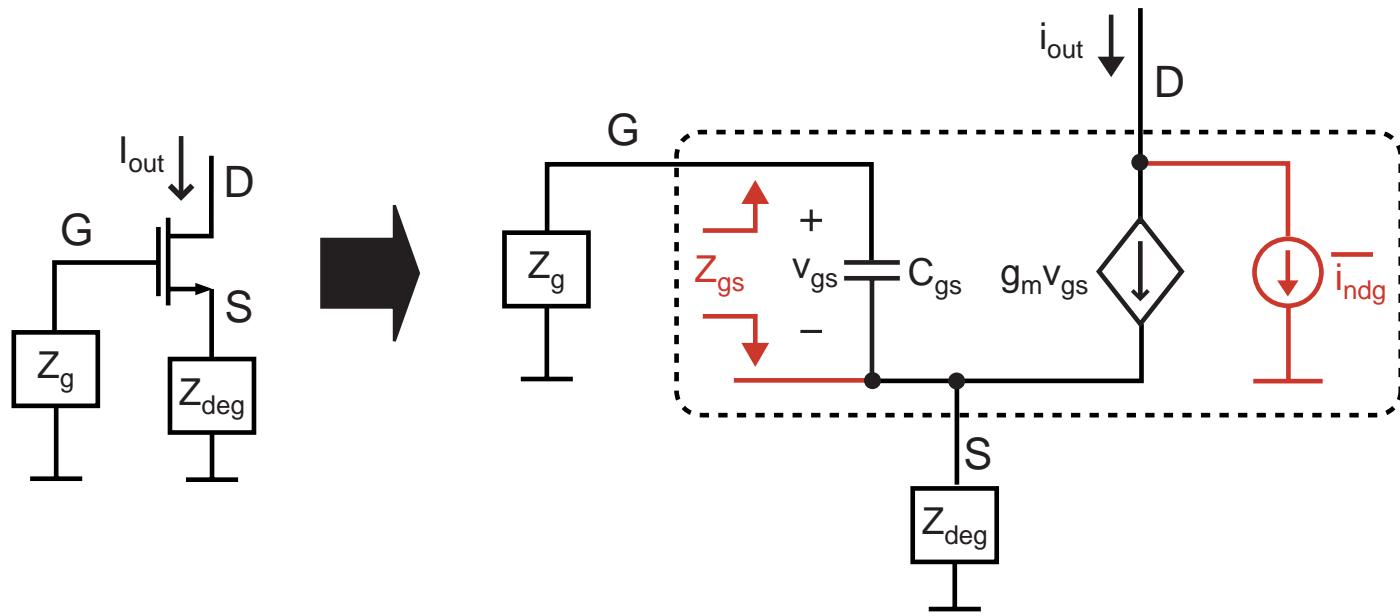Calculation of Output Current Noise Variance (Power)



$$i_{out} = \overline{i_{ndg}} = \eta \overline{i_{nd}} + g_m Z_{gs} \overline{i_{ng}}$$

- To find noise variance:

$$\overline{i_{ndg}^2} = \overline{i_{ndg}^* i_{ndg}} = \overline{(\eta^* i_{nd}^* + g_m Z_{gs}^* i_{ng}^*)(\eta i_{nd} + g_m Z_{gs} i_{ng})}$$

Variance (i.e., Power) Calc. for Output Current Noise

■ Noise variance calculation

$$\begin{aligned}\overline{i_{ndg}^2} &= |\eta|^2 \overline{i_{nd}^* i_{nd}} + \overline{i_{nd}^* i_{ng}} g_m \eta^* Z_{gs} + \overline{i_{nd} i_{ng}^*} (g_m \eta Z_{gs})^* + \overline{i_{ng} i_{ng}^*} |g_m Z_{gs}|^2 \\ &= |\eta|^2 \overline{i_{nd}^2} + 2 \operatorname{Re} \{ \overline{i_{nd}^* i_{ng}} g_m \eta^* Z_{gs} \} + \overline{i_{ng}^2} |g_m Z_{gs}|^2 \\ &= |\eta|^2 \overline{i_{nd}^2} + 2 \operatorname{Re} \{ \frac{\overline{i_{nd}^* i_{ng}}}{\sqrt{\overline{i_{nd}^2} \overline{i_{ng}^2}}} \sqrt{\overline{i_{nd}^2} \overline{i_{ng}^2}} g_m \eta^* Z_{gs} \} + \overline{i_{ng}^2} |g_m Z_{gs}|^2\end{aligned}$$

■ Define correlation coefficient c between i_{ng} and i_{nd}

$$c = \frac{\overline{i_{nd}^* i_{ng}}}{\sqrt{\overline{i_{nd}^2} \overline{i_{ng}^2}}} \Rightarrow \overline{i_{ndg}^2} = |\eta|^2 \overline{i_{nd}^2} + 2 \operatorname{Re} \{ c \sqrt{\overline{i_{nd}^2} \overline{i_{ng}^2}} g_m \eta^* Z_{gs} \} + \overline{i_{ng}^2} |g_m Z_{gs}|^2$$

$$\boxed{\overline{i_{ndg}^2} = \overline{i_{nd}^2} \left(|\eta|^2 + 2 \operatorname{Re} \left\{ c \sqrt{\frac{\overline{i_{ng}^2}}{\overline{i_{nd}^2}}} g_m \eta^* Z_{gs} \right\} + \frac{\overline{i_{ng}^2}}{\overline{i_{nd}^2}} g_m^2 |Z_{gs}|^2 \right)}$$

Parameterized Expression for Output Noise Variance

- Key equation from last slide

$$\overline{i_{ndg}^2} = \overline{i_{nd}^2} \left(|\eta|^2 + 2\operatorname{Re} \left\{ c \sqrt{\frac{\overline{i_{ng}^2}}{\overline{i_{nd}^2}}} g_m \eta^* Z_{gs} \right\} + \frac{\overline{i_{ng}^2}}{\overline{i_{nd}^2}} g_m^2 |Z_{gs}|^2 \right)$$

- Solve for noise ratio


$$\sqrt{\frac{\overline{i_{ng}^2}}{\overline{i_{nd}^2}}} g_m = g_m \sqrt{\frac{4kT\delta(wC_{gs})^2/(5g_{do})}{4kT\gamma g_{do}}} = \frac{g_m}{g_{do}} \sqrt{\frac{\delta}{5\gamma}} (wC_{gs})$$

- Define parameters $Z_{gs w}$ and χ_d

$$Z_{gs w} = wC_{gs} Z_{gs}, \quad \chi_d = \frac{g_m}{g_{do}} \sqrt{\frac{\delta}{5\gamma}}$$

$$\Rightarrow \overline{i_{ndg}^2} = \overline{i_{nd}^2} \left(|\eta|^2 + 2\operatorname{Re} \{ c\chi_d \eta^* Z_{gs w} \} + \chi_d^2 |Z_{gs w}|^2 \right)$$

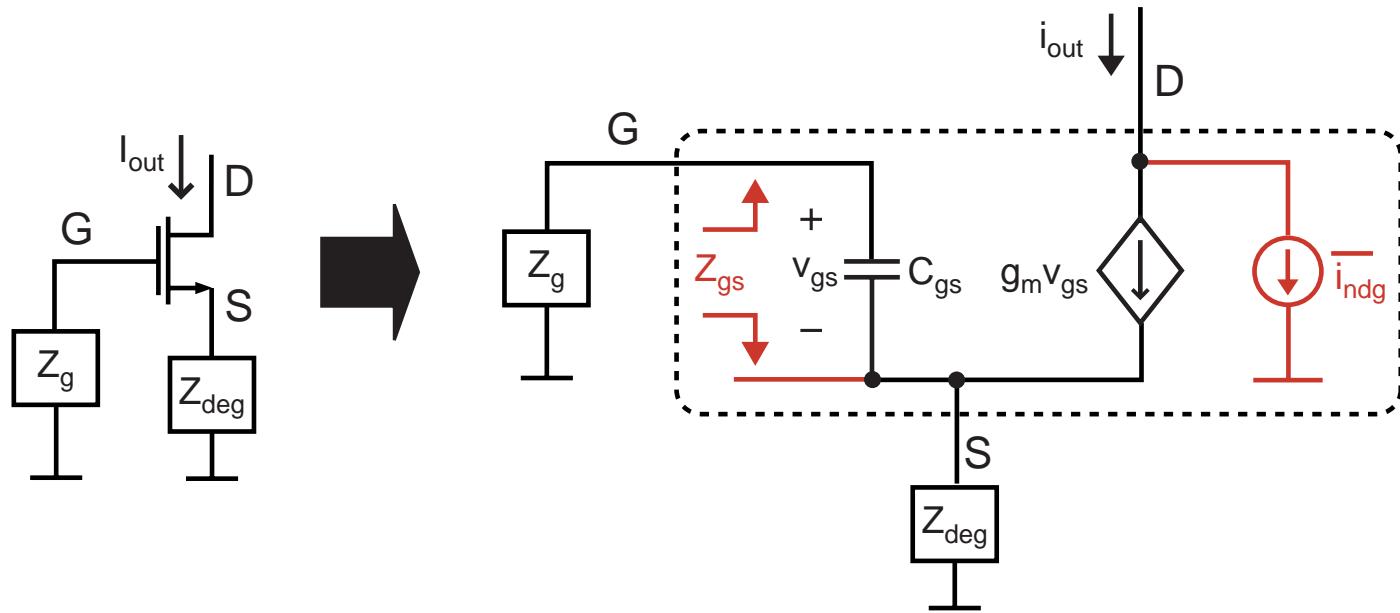Small Signal Model for Noise Calculations




$$\frac{\overline{i_{ndg}^2}}{\Delta f} = \frac{\overline{i_{nd}^2}}{\Delta f} \left(|\eta|^2 + 2\text{Re} \{ c\chi_d \eta^* Z_{gs} \} + \chi_d^2 |Z_{gs}|^2 \right)$$

where: $\frac{\overline{i_{nd}^2}}{\Delta f} = 4kT\gamma g_{do}$, $\chi_d = \frac{g_m}{g_{do}} \sqrt{\frac{\delta}{5\gamma}}$, $Z_{gs} = wC_{gs}Z_{gs}$

$$Z_{gs} = \frac{1}{sC_{gs}} \left| \left| \frac{Z_{deg} + Z_g}{1 + g_m Z_{deg}} \right| \right|$$

$$\eta = 1 - \left(\frac{g_m Z_{deg}}{Z_{deg} + Z_g} \right) Z_{gs}$$

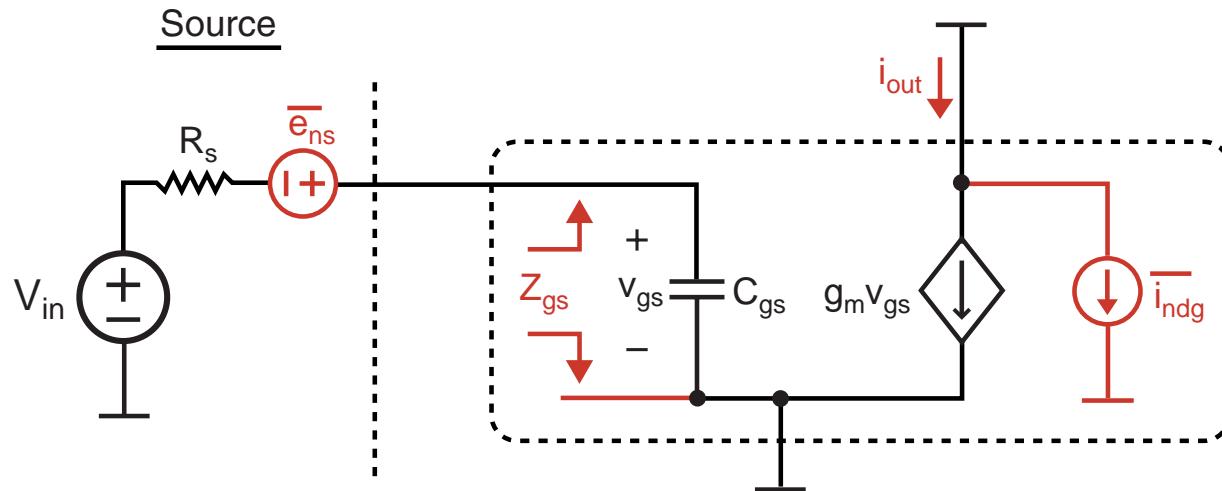Example: Output Current Noise with $Z_s = R_s$, $Z_{deg} = 0$



- Step 1: Determine key noise parameters
 - For 0.18μ CMOS, we will assume the following

$$c = -j0.55, \quad \gamma = 3, \quad \delta = 2\gamma = 6, \quad \frac{g_m}{g_{do}} = \frac{1}{2} \Rightarrow \chi_d = 0.32$$

- Step 2: calculate η and Z_{gsw}

$$\eta = 1,$$

$$Z_{gsw} = wC_{gs} \left(R_s \parallel \frac{1}{jwC_{gs}} \right) = \frac{wC_{gs}R_s}{1 + jwC_{gs}R_s}$$

Calculation of Output Current Noise (continued)

- Step 3: Plug values into the previously derived expression

$$\frac{\overline{i_{ndg}^2}}{\Delta f} = \frac{\overline{i_{nd}^2}}{\Delta f} \left(1 + 2\text{Re} \{ -j|c|\chi_d Z_{gsw} \} + \chi_d^2 |Z_{gsw}|^2 \right)$$

Drain Noise Multiplying Factor

$$Z_{gsw} = wC_{gs} \left(R_s \parallel \frac{1}{jwC_{gs}} \right) = \frac{wC_{gs}R_s}{1 + jwC_{gs}R_s}$$

- For $w \ll 1/(R_s C_{gs})$:

$$Z_{gsw} \approx wC_{gs}R_s \quad \Rightarrow \quad \frac{\overline{i_{ndg}^2}}{\Delta f} \approx \frac{\overline{i_{nd}^2}}{\Delta f} \left(1 + \chi_d^2 (wC_{gs}R_s)^2 \right)$$

Gate noise contribution

Calculation of Output Current Noise (continued)

- Step 3: Plug values into the previously derived expression

$$\frac{\overline{i_{ndg}^2}}{\Delta f} = \frac{\overline{i_{nd}^2}}{\Delta f} \left(1 + 2\text{Re} \{ -j|c|\chi_d Z_{gsw} \} + \chi_d^2 |Z_{gsw}|^2 \right)$$

Drain Noise Multiplying Factor

$$Z_{gsw} = wC_{gs} \left(R_s \left| \frac{1}{jwC_{gs}} \right| \right) = \frac{wC_{gs}R_s}{1 + jwC_{gs}R_s}$$


- For $w \gg 1/(R_s C_{gs})$:

$$Z_{gsw} \approx 1/j \Rightarrow \frac{\overline{i_{ndg}^2}}{\Delta f} = \frac{\overline{i_{nd}^2}}{\Delta f} \left(1 - 2|c|\chi_d + \chi_d^2 \right)$$

Gate noise contribution


Plot of Drain Noise Multiplying Factor (0.18μ NMOS)

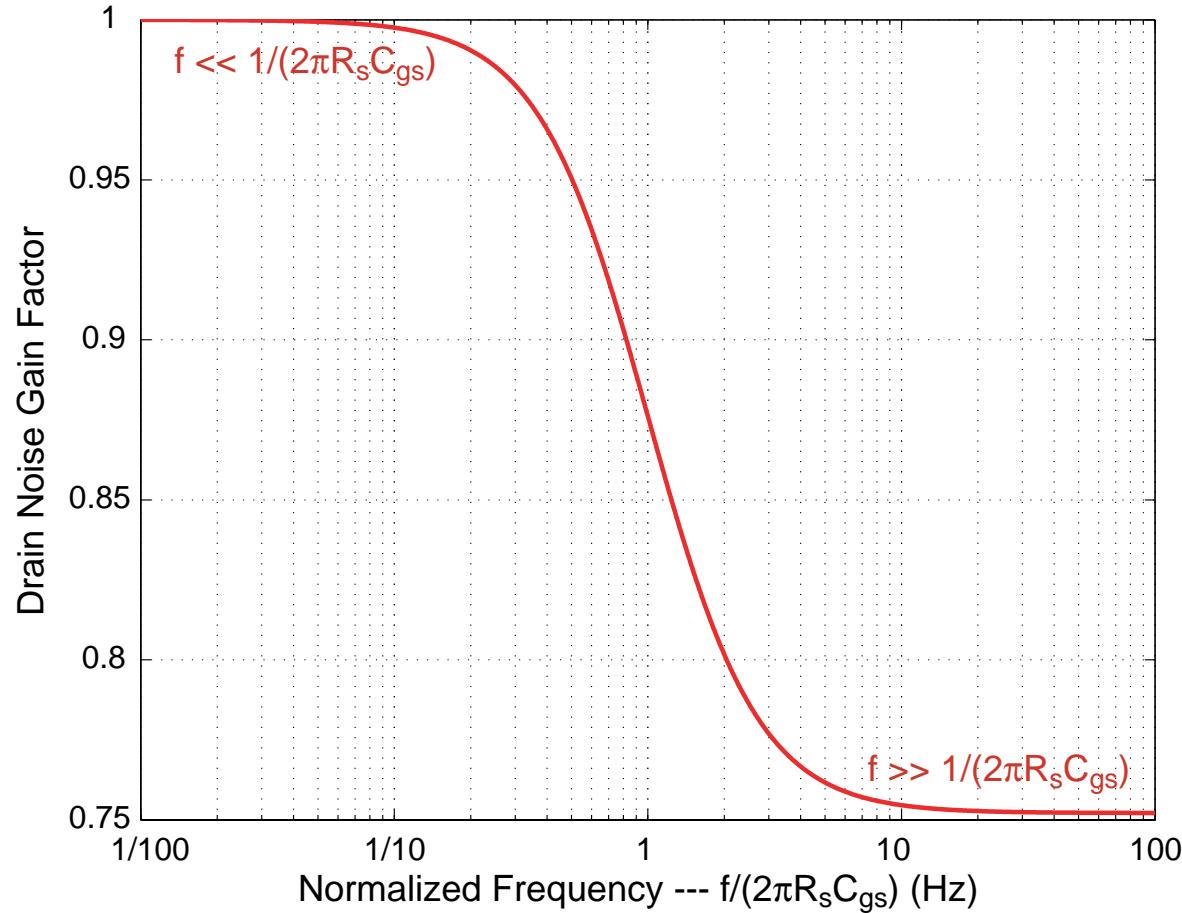Drain Noise Multiplying Factor Versus Frequency for 0.18μ NMOS Device




- Conclusion: gate noise has little effect on common source amp when source impedance is purely resistive!

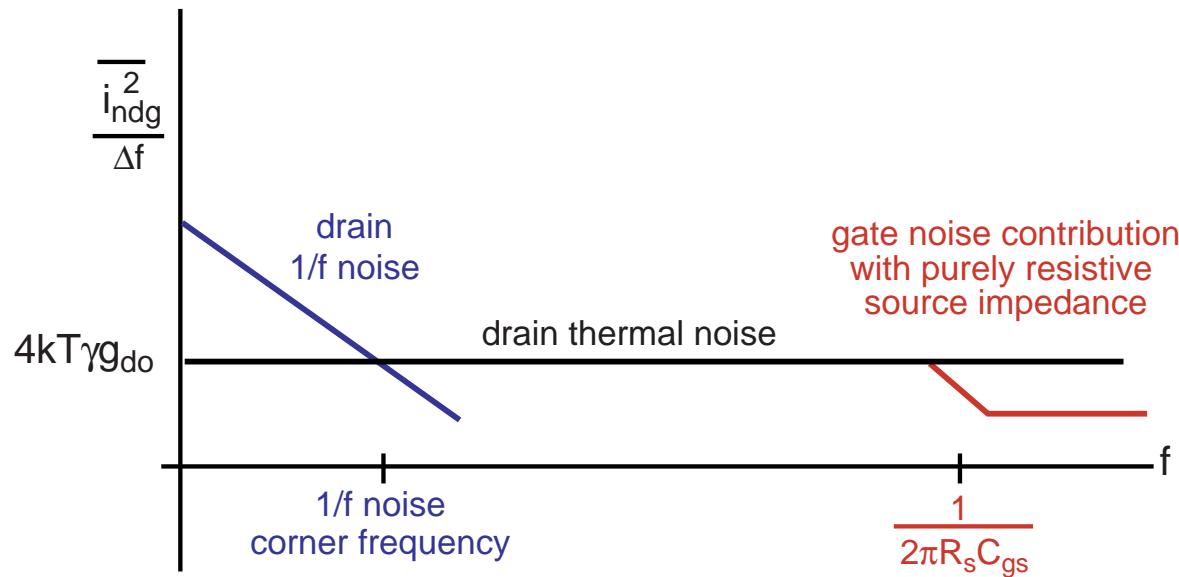Broadband Amplifier Design Considerations for Noise




- Drain thermal noise is the chief issue of concern when designing amplifiers with > 1 GHz bandwidth
 - 1/f noise corner is usually less than 1 MHz
 - Gate noise contribution only has influence at high frequencies
- Noise performance specification is usually given in terms of input referred voltage noise

Narrowband Amplifier Noise Requirements

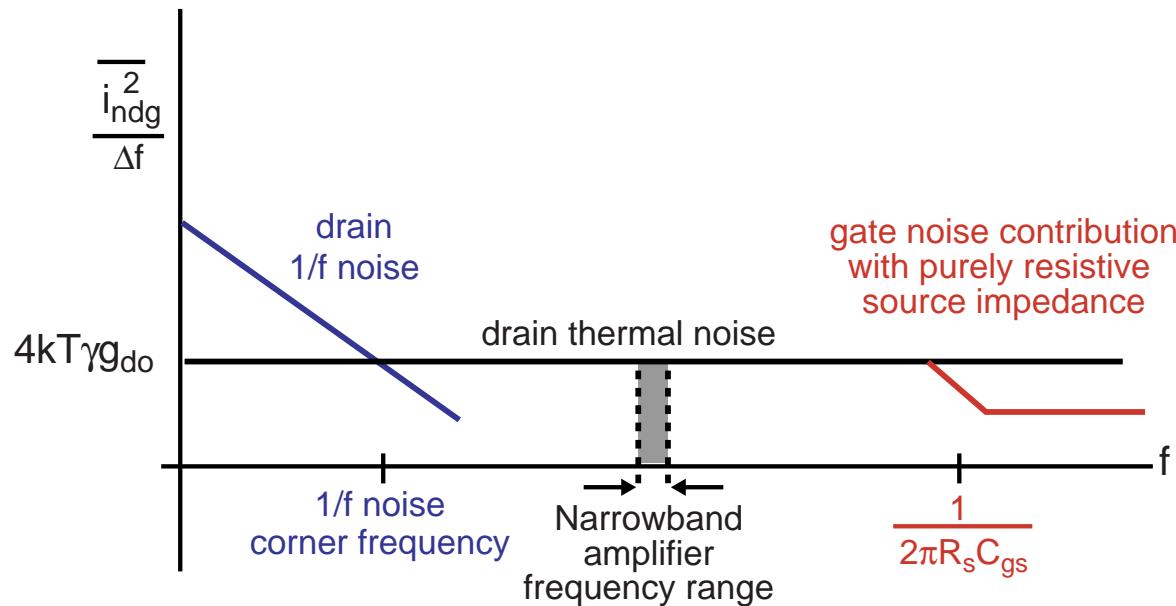

- Here we focus on a narrowband of operation
 - Don't care about noise outside that band since it will be filtered out
- Gate noise is a significant issue here
 - Using reactive elements in the source dramatically impacts the influence of gate noise
- Specification usually given in terms of Noise Figure

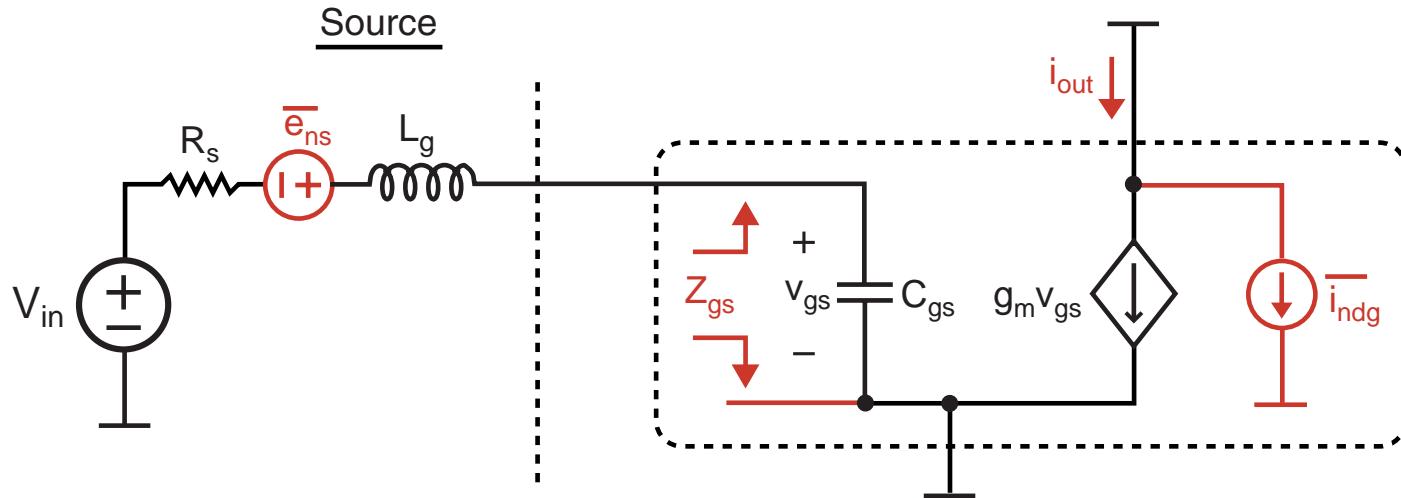The Impact of Gate Noise with $Z_s = R_s + sL_g$




- Step 1: Determine key noise parameters
 - For 0.18μ CMOS, again assume the following

$$c = -j0.55, \quad \gamma = 3, \quad \delta = 2\gamma = 6, \quad \frac{g_m}{g_{do}} = \frac{1}{2} \Rightarrow \chi_d = 0.32$$

- Step 2: Note that $\eta = 1$, calculate Z_{gsw}

$$Z_{gsw} = wC_{gs} \left((R_s + jwL_g) \parallel \frac{1}{jwC_{gs}} \right) = \frac{wC_{gs}(R_s + jwL_g)}{1 - w^2 L_g C_{gs} + jwC_{gs}R_s}$$

Evaluate Z_{gsw} At Resonance

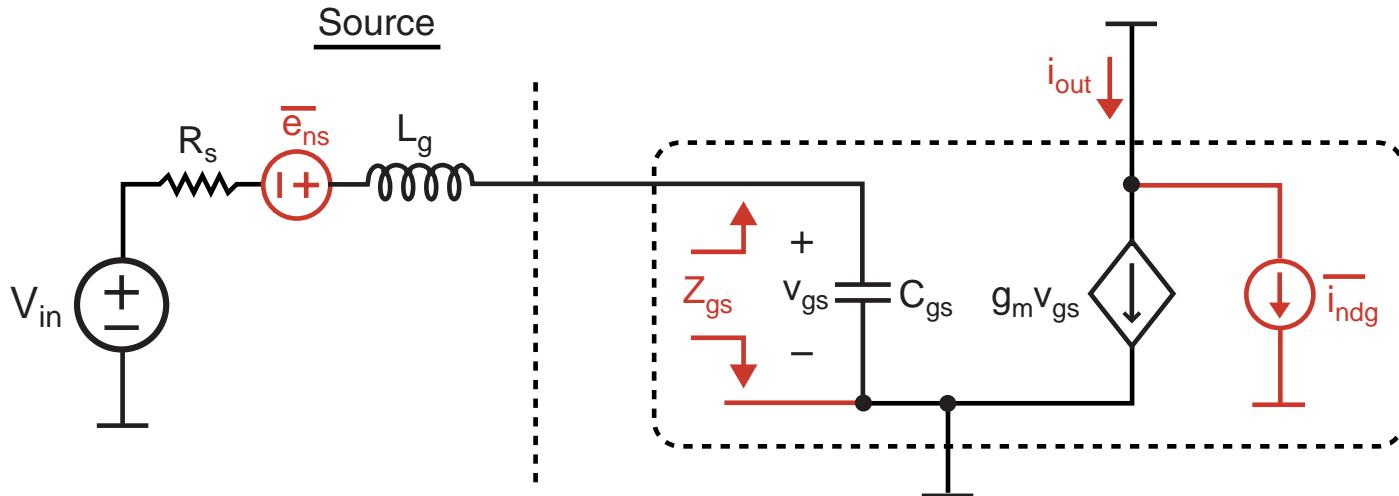

- Set L_g such that it resonates with C_{gs} at the center frequency (w_o) of the narrow band of interest

$$\Rightarrow \frac{1}{\sqrt{L_g C_{gs}}} = w_o$$

Note: $Q = \frac{1}{w_o C_{gs} R_s} = \frac{w_o L_g}{R_s}$

- Calculate Z_{gsw} at frequency w_o

$$Z_{gsw} = \frac{w_o C_{gs} (R_s + j w_o L_g)}{1 - w_o^2 L_g C_{gs} + j w_o C_{gs} R_s} = w_o C_{gs} (Q^2 R_s - j \sqrt{L_g / C_{gs}})$$
$$= Q - j$$

The Impact of Gate Noise with $Z_s = R_s + sL_g$ (Cont.)

- Key noise expression derived earlier

$$\frac{\overline{i_{ndg}^2}}{\Delta f} = \frac{\overline{i_{nd}^2}}{\Delta f} \left(1 + 2\text{Re} \{-j|c|\chi_d Z_{gsw}\} + \chi_d^2 |Z_{gsw}|^2 \right)$$

- Substitute in for Z_{gsw}

$$2\text{Re} \{-j|c|\chi_d Z_{gsw}\} = 2\text{Re} \{-j|c|\chi_d(Q - j)\} = -2|c|\chi_d$$


$$\chi_d^2 |Z_{gsw}|^2 = \chi_d^2 |Q - j|^2 = \chi_d^2 (Q^2 + 1)$$

$$\Rightarrow \frac{\overline{i_{ndg}^2}}{\Delta f} = \frac{\overline{i_{nd}^2}}{\Delta f} \left(1 - 2|c|\chi_d + \chi_d^2 (Q^2 + 1) \right)$$

Gate noise contribution

- Gate noise contribution is a function of Q!
 - Rises monotonically with Q

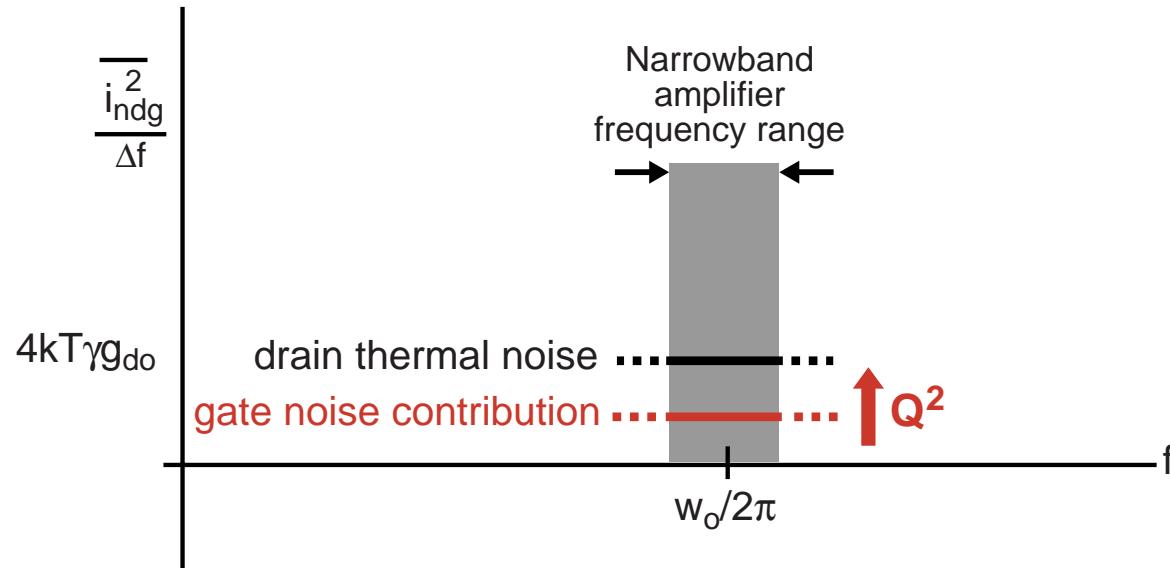At What Value of Q Does Gate Noise Exceed Drain Noise?




- Determine crossover point for Q value

$$\frac{\overline{i_{ndg}^2}}{\Delta f} = \frac{\overline{i_{nd}^2}}{\Delta f} (1 - 2|c|\chi_d + \chi_d^2(Q^2 + 1)) = \frac{\overline{i_{nd}^2}}{\Delta f} 1$$

$$\Rightarrow Q = \sqrt{1/\chi_d^2 - 1 + 2|c|/\chi_d} \quad (= 3.5 \text{ for } 0.18\mu \text{ specs})$$

- Critical Q value for crossover is primarily set by process

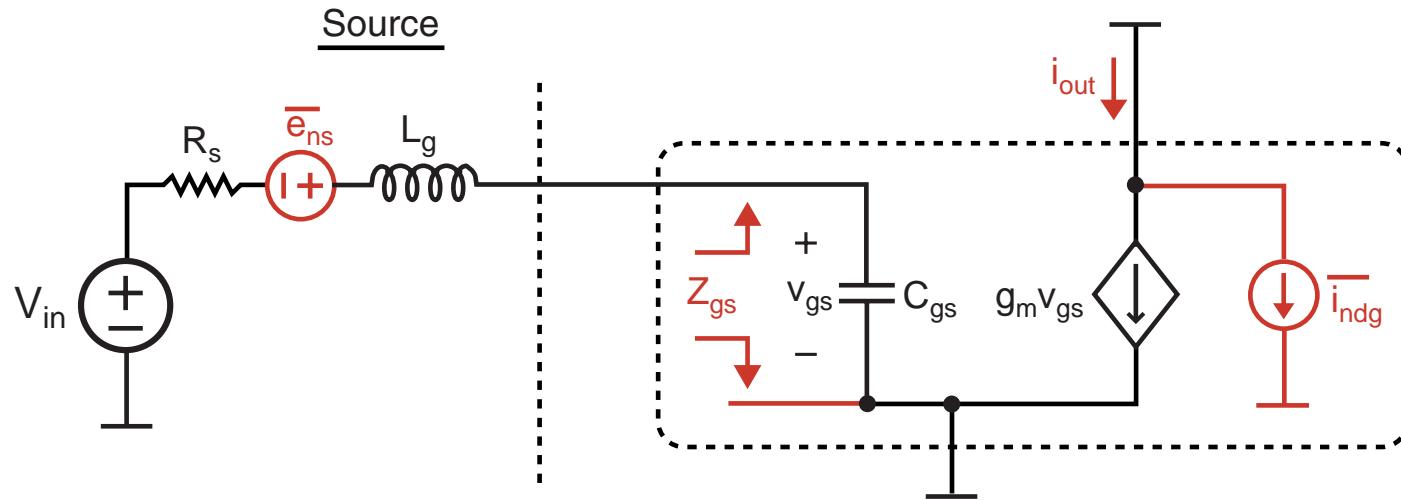Calculation of the Signal Spectrum at the Output



- First calculate relationship between v_{in} and i_{out}

$$i_{out,sig} = g_m v_{gs} = g_m \frac{1}{1 - w^2 L_g C_{gs} + j w R_s C_{gs}} V_{in}$$


- At resonance:

$$i_{out,sig} = g_m v_{gs} = g_m \frac{1}{j w_o R_s C_{gs}} v_{in} = g_m (-j Q) v_{in}$$

- Spectral density of signal at output at resonant frequency

$$S_{iout,sig}(f) = |g_m(-jQ)|^2 S_{in}(f) = (g_m Q)^2 S_{in}(f)$$

Impact of Q on SNR (Ignoring R_s Noise)

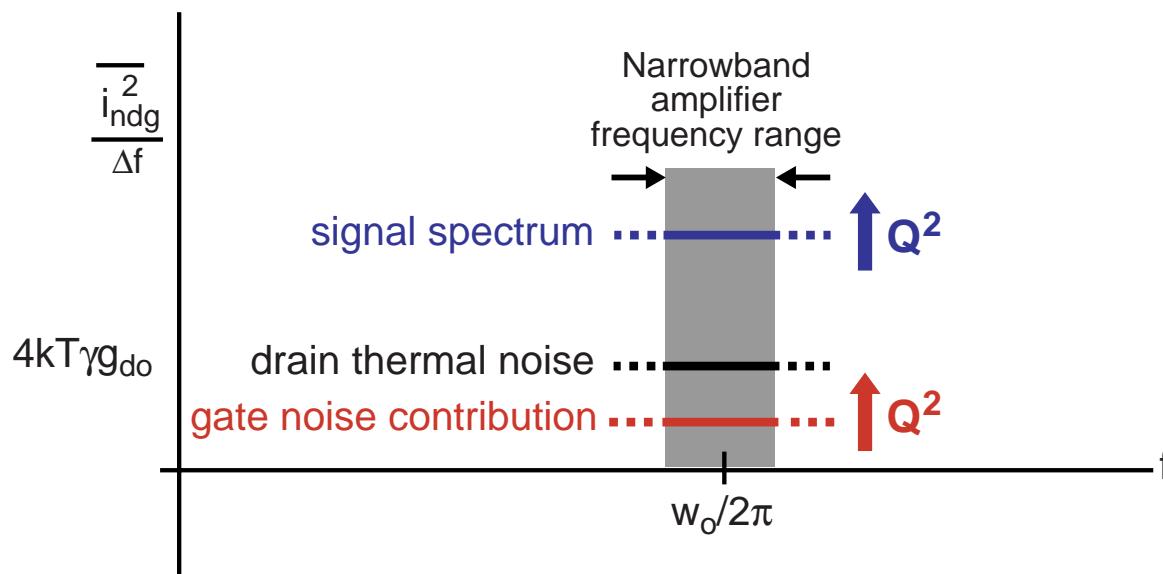


- **SNR (assume constant spectra, ignore noise from R_s):**

$$SNR_{out} = \frac{S_{iout,sig}(f)}{S_{iout,noise}(f)} \approx \frac{(g_m Q)^2 S_{in}(f)}{\bar{i_{ndg}^2}/\Delta f}$$

- **For small Q such that gate noise < drain noise**
 - SNR_{out} improves dramatically as Q is increased
- **For large Q such that gate noise > drain noise**
 - SNR_{out} improves very little as Q is increased

Noise Factor and Noise Figure

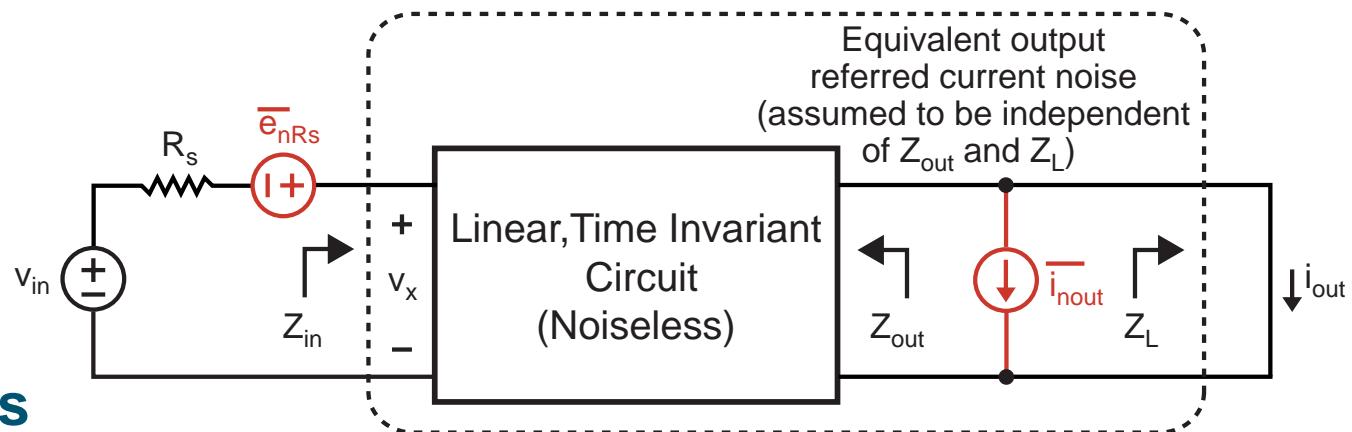

■ Definitions

$$\text{Noise Factor } = F = \frac{SNR_{in}}{SNR_{out}}$$


$$\text{Noise Figure} = 10 \log(\text{Noise Factor})$$

■ Calculation of SNR_{in} and SNR_{out}

$$SNR_{in} = \frac{|\alpha|^2 v_{in}^2}{|\alpha|^2 e_{nRs}^2} = \frac{v_{in}^2}{e_{nRs}^2} \quad \text{where } \alpha = \frac{Z_{in}}{R_s + Z_{in}}$$

$$SNR_{out} = \frac{|\alpha|^2 |G_m|^2 v_{in}^2}{|\alpha|^2 |G_m|^2 e_{nRs}^2 + i_{nout}^2} \quad \text{where } G_m = \frac{i_{out}}{v_x}$$

Calculate Noise Factor (Part 1)

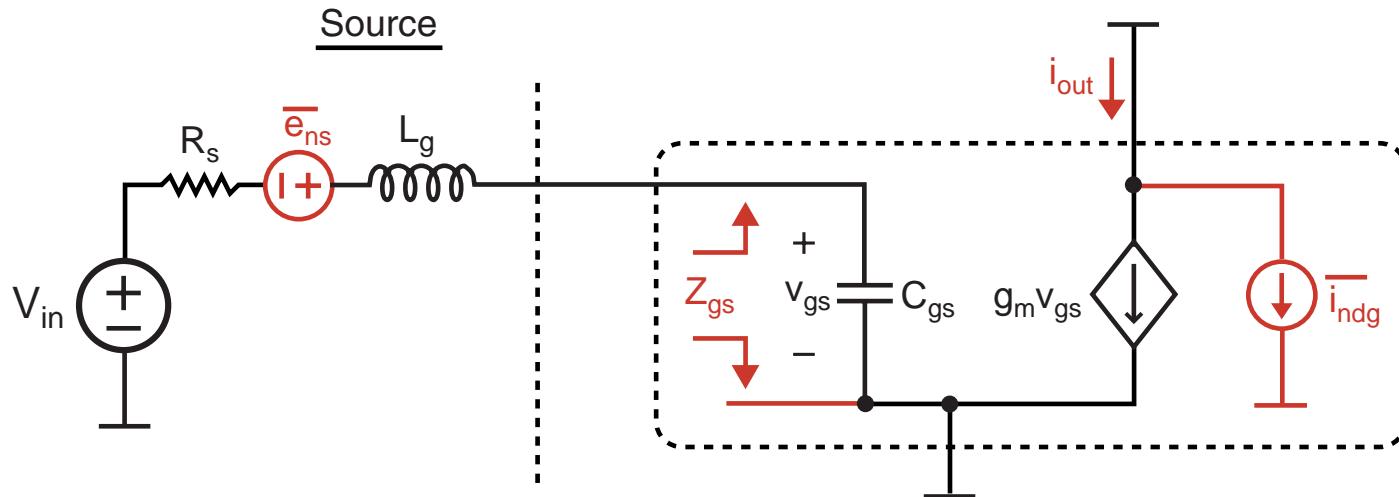

- First calculate SNR_{out} (must include R_s noise for this)
 - R_s noise calculation (same as for V_{in})

$$i_{out,Rs} = g_m(-jQ) \overline{e_{ns}} \Rightarrow S_{iout,Rs}(f) = (g_m Q)^2 4kT R_s$$

- SNR_{out} : $\Rightarrow SNR_{out} = \frac{(g_m Q)^2 S_{in}(f)}{\overline{i_{ndg}^2}/\Delta f + (g_m Q)^2 4kT R_s}$

- Then calculate SNR_{in} :

$$SNR_{in} = \frac{S_{in}(f)}{\overline{e_{ns}^2}/\Delta f} = \frac{S_{in}(f)}{4kT R_s}$$

Calculate Noise Factor (Part 2)

$$SNR_{out} = \frac{|g_m Q|^2 S_{in}(f)}{\overline{i_{ndg}^2}/\Delta f + (g_m Q)^2 4kTR_s} \quad SNR_{in} = \frac{S_{in}(f)}{\overline{e_{ns}^2}/\Delta f} = \frac{S_{in}(f)}{4kTR_s}$$

- Noise Factor calculation:

$$\begin{aligned} \text{Noise Factor} &= \frac{SNR_{in}}{SNR_{out}} = \frac{\overline{i_{ndg}^2}/\Delta f + |g_m Q|^2 4kTR_s}{(g_m Q)^2 4kTR_s} \\ &= 1 + \frac{\overline{i_{ndg}^2}/\Delta f}{(g_m Q)^2 4kTR_s} \end{aligned}$$

- From previous analysis

$$\overline{i_{ndg}^2}/\Delta f = 4kT\gamma g_{do} \left(1 - 2|c|\chi_d + (Q^2 + 1)\chi_d^2 \right)$$

$$\Rightarrow \text{Noise Factor} = 1 + \frac{\gamma g_{do} \left(1 - 2|c|\chi_d + (Q^2 + 1)\chi_d^2 \right)}{(g_m Q)^2 R_s}$$

Calculate Noise Factor (Part 3)

$$\text{Noise Factor} = 1 + \frac{\gamma g_{do} (1 - 2|c|\chi_d + (Q^2 + 1)\chi_d^2)}{(g_m Q)^2 R_s}$$

■ Modify denominator using expressions for Q and w_t

$$Q = \frac{1}{w_o R_s C_{gs}}, \quad w_t \approx \frac{g_m}{C_{gs}}$$

$$\Rightarrow (g_m Q)^2 R_s = g_m^2 Q \frac{R_s}{w_o R_s C_{gs}} = g_m Q \frac{g_m}{C_{gs} w_o} \frac{1}{w_o} = g_m Q \frac{w_t}{w_o}$$

■ Resulting expression for noise factor:

$$\text{Noise Factor} = 1 + \left(\frac{w_o}{w_t} \right) \gamma \left(\frac{g_{do}}{g_m} \right) \frac{1}{Q} (1 - 2|c|\chi_d + (Q^2 + 1)\chi_d^2)$$

Noise Factor scaling coefficient

- Noise factor primarily depends on Q, w_o/w_t , and process specs

Minimum Noise Factor


$$\text{Noise Factor} = \frac{1 + \left(\frac{w_o}{w_t}\right) \gamma \left(\frac{g_{do}}{g_m}\right) \frac{1}{Q} (1 - 2|c|\chi_d + (Q^2 + 1)\chi_d^2)}{\text{Noise Factor scaling coefficient}}$$

- We see that the noise factor will be minimized for some value of Q
 - Could solve analytically by differentiating with respect to Q and solving for peak value (i.e. where deriv. = 0)
- In Tom Lee's book (pp 272-277), the minimum noise factor for the MOS common source amplifier (i.e. no degeneration) is found to be:

$$\text{Min Noise Factor} = \frac{1 + \left(\frac{w_o}{w_t}\right) \frac{2}{\sqrt{5}} \sqrt{\gamma \delta (1 - |c|^2)}}{\text{Noise Factor scaling coefficient}}$$

- How do these compare?

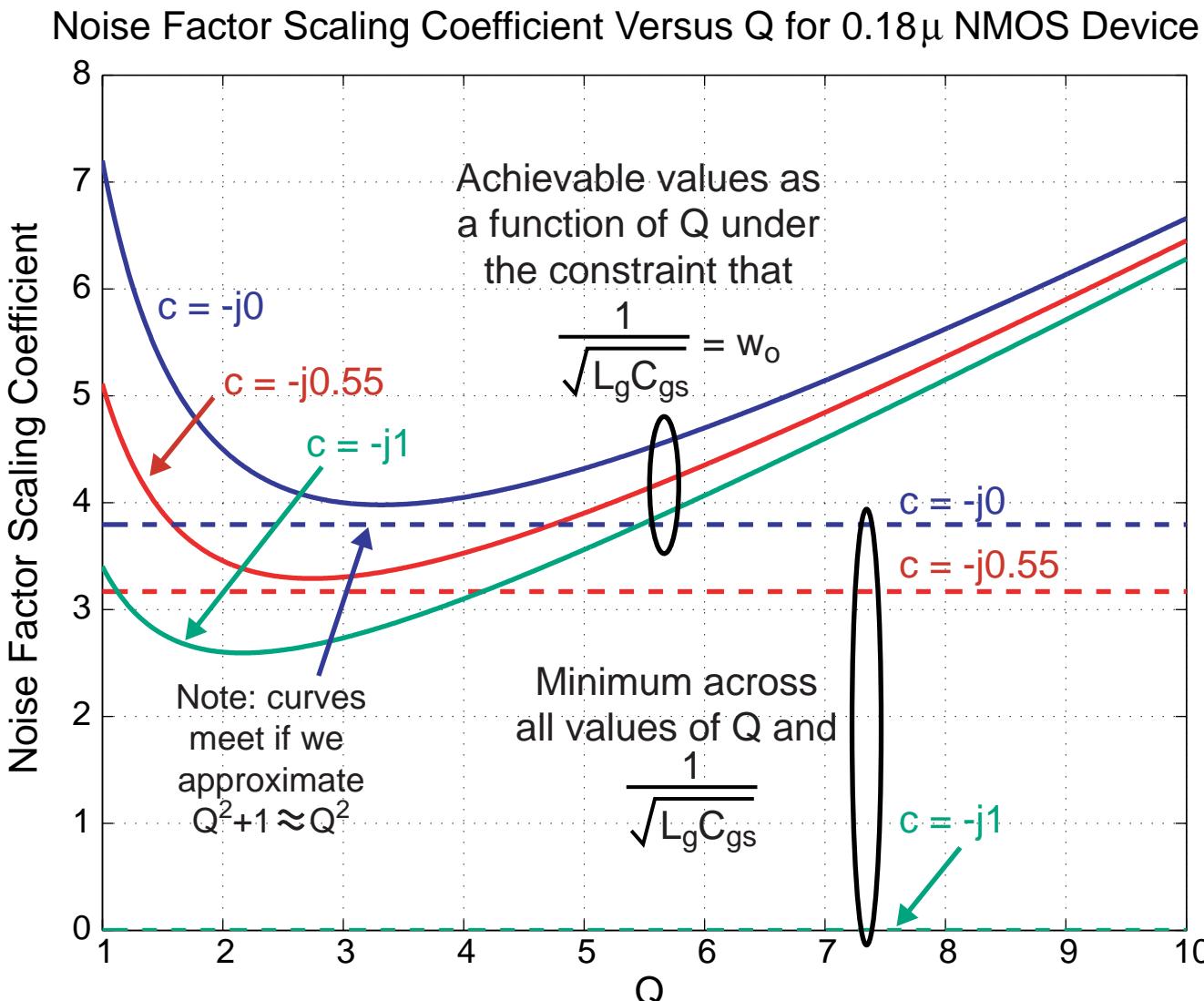Plot of Minimum Noise Factor and Noise Factor Vs. Q



Achieving Minimum Noise Factor

- **For common source amplifier without degeneration**
 - Minimum noise factor can only be achieved at resonance if gate noise is uncorrelated to drain noise (i.e., if $c = 0$) – we'll see this next lecture
 - We typically must operate slightly away from resonance in practice to achieve minimum noise factor since c will be nonzero
- **How do we determine the optimum source impedance to minimize noise figure in classical analysis?**
 - Next lecture!