




6.776

High Speed Communication Circuits and Systems
Lecture 12
Low Noise Amplifiers

Massachusetts Institute of Technology
March 15, 2005


Copyright © 2005 by Hae-Seung Lee and Michael H.
Perrott

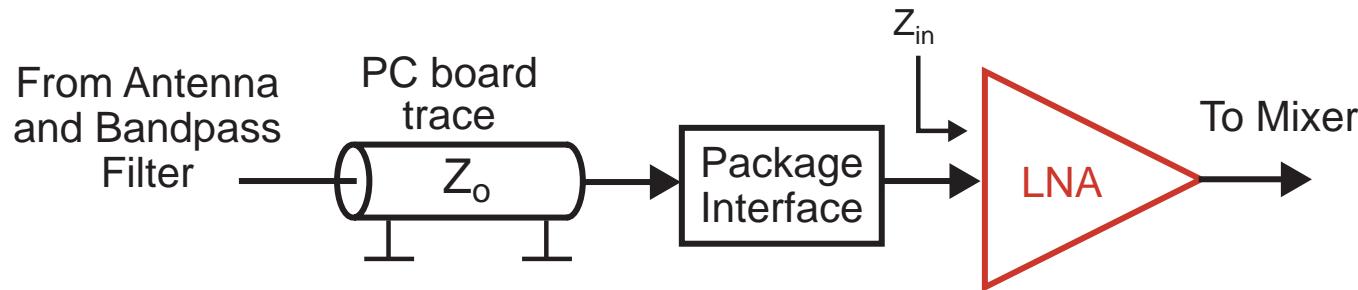Narrowband LNA Design for Wireless Systems



- **Design Issues**
 - Noise Figure – impacts receiver sensitivity
 - Linearity (IIP3) – impacts receiver blocking performance
 - Gain – high gain reduces impact of noise from components that follow the LNA (such as the mixer)
 - Power match – want $Z_{in} = Z_o$ (usually = 50 Ohms)
 - Power – want low power dissipation
 - Bandwidth – need to pass the entire RF band for the intended radio application (i.e., all of the relevant channels)
 - Sensitivity to process/temp variations – need to make it manufacturable in high volume


Our Focus in This Lecture

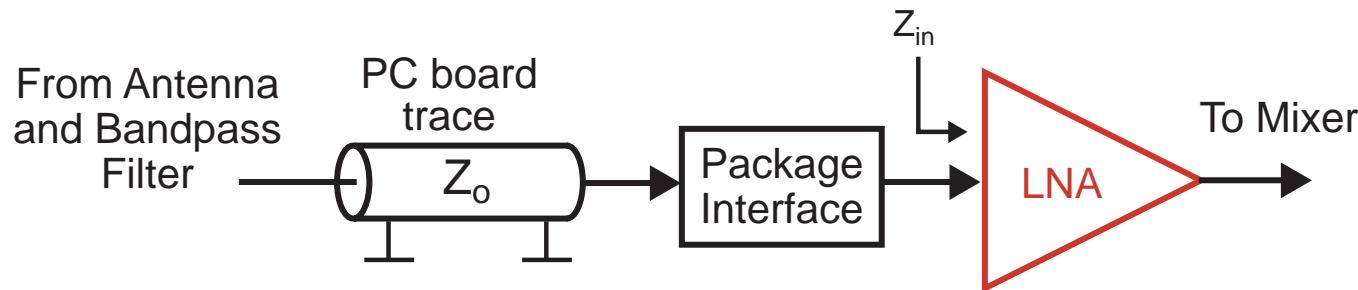

- Designing for low Noise Figure
- Achieving a good power match
- Hints at getting good IIP3
- Impact of power dissipation on design
- Tradeoff in gain versus bandwidth

Direct Input Termination of CS Amplifier

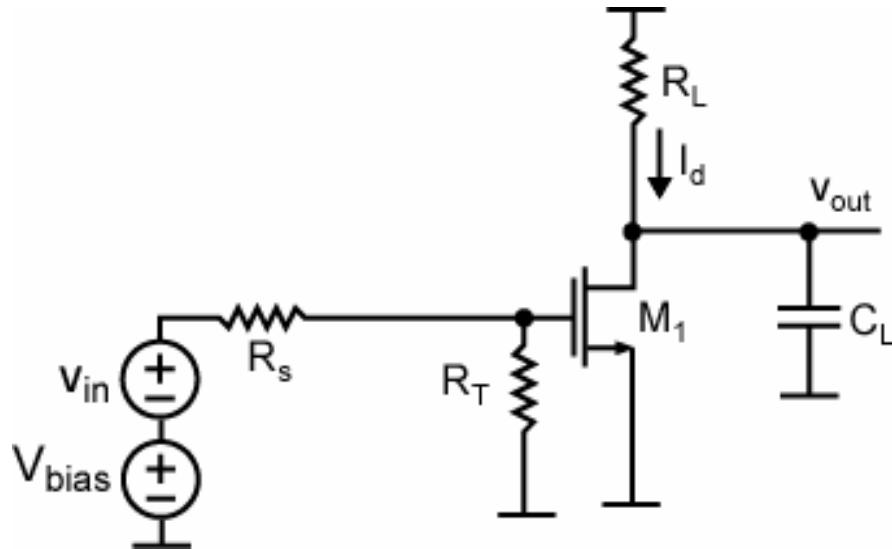- For power match, terminate the input of CS amplifier



$$R_T = R_s = R$$

- Voltage gain is halved
- Termination resistor adds thermal noise
- More appropriate for broadband than narrowband (maybe)

Noise Factor (Low Frequency)

- Noise factor at low frequencies (thus ignoring gate current noise) looking at short-circuit output current

$$\overline{i_{n1}^2} = \frac{1}{4} g_m^2 4kT R \Delta f = kT g_m (g_m R) \Delta f$$


$$\overline{i_{n2}^2} = 2kT g_m (g_m R) \Delta f + 4kT \gamma g_{do} \Delta f$$

$$\begin{aligned} F &= \frac{2kT g_m (g_m R) \Delta f + 4kT \gamma g_{do} \Delta f}{kT g_m (g_m R) \Delta f} \\ &= 2 + 4 \frac{\gamma g_{do}}{g_m} \cdot \frac{1}{g_m R} \\ &= 2 + 4 \frac{\gamma}{\alpha} \cdot \frac{1}{g_m R} \end{aligned}$$

- Noise factor too high even at low frequencies.
- Generally not an acceptable circuit for LNA

Common-Gate Amplifier

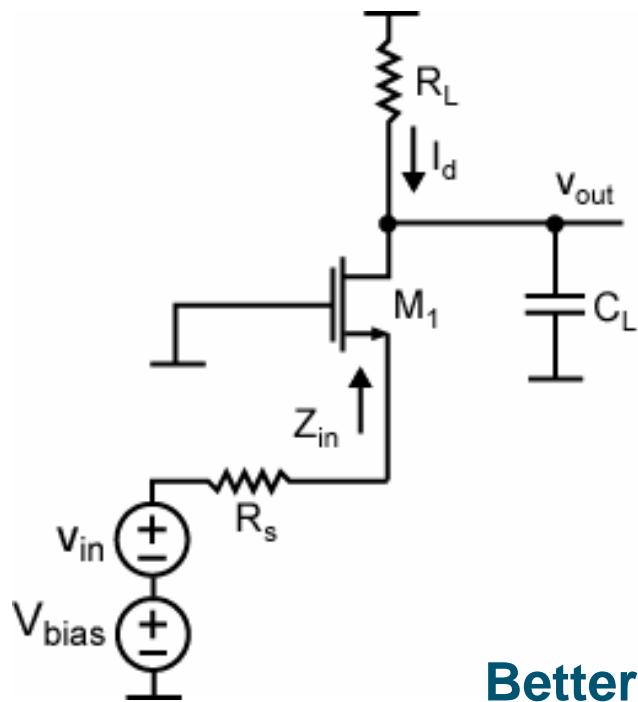Offers the possibility of power match without an explicit termination resistor



For power match, make

$$Z_{in} = \frac{1}{g_m} = R_s$$


At low frequencies, it can be shown

$$F = 1 + \frac{\gamma}{\alpha} \cdot \frac{1}{g_m R_s} = 1 + \frac{\gamma}{\alpha}$$

Better than the CS, but noise factor degrades significantly at high frequencies

Noise Factor Analysis of CG Amp (Low Freq.)

■ Equivalent Circuit

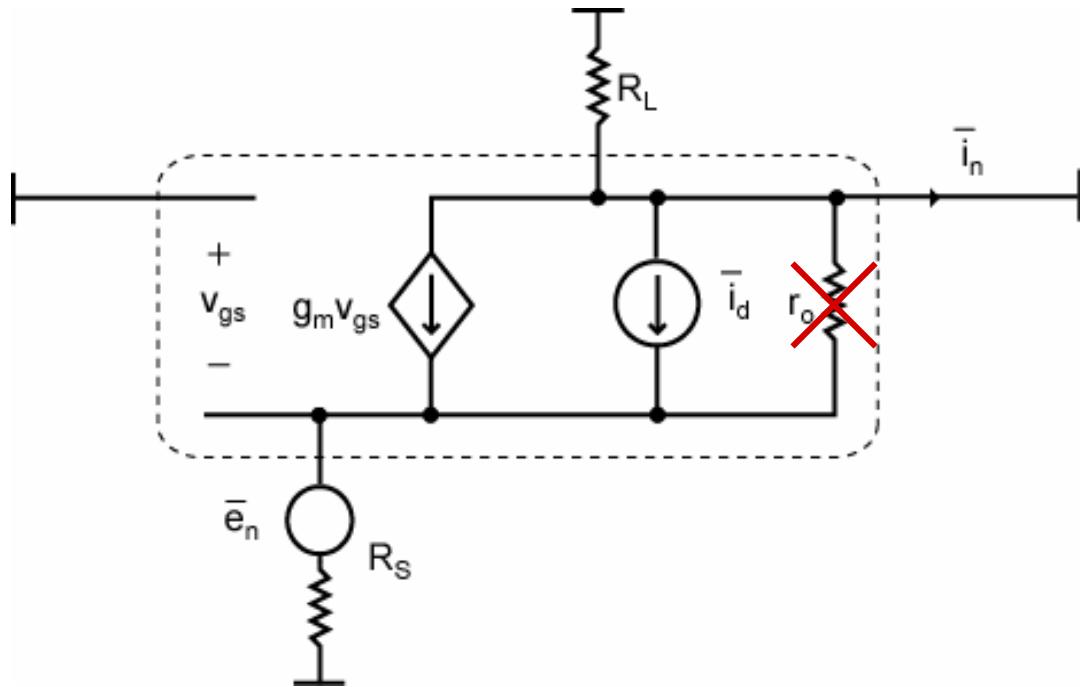

Noise Factor Calculation

- Noise factor at low frequencies (thus ignoring gate current noise) looking at short-circuit output current
First calculate the output noise due to the source resistance only (e_n) using voltage divider:

$$\begin{aligned}\overline{i_{n1}^2} &= \frac{\left(\frac{1}{g_m}\right)^2}{\left(R_s + \frac{1}{g_m}\right)^2} g_m^2 4kT R_s \Delta f \\ &= \frac{g_m^2}{(1 + g_m R_s)^2} 4kT R_s \Delta f\end{aligned}$$

The next step is finding the total output noise due to e_n and i_d . We can use superposition as before.

Noise Factor Calculation, Continued

First, let's compute output noise due to i_d only. We'll need to use the instantaneous value of i_d for now:

$$v_{gs} = -(i_d + g_m v_{gs}) R_s$$


$$g_m v_{gs} = -\frac{g_m R_s}{1 + g_m R_s} i_d$$

The instantaneous value of the output noise due to i_d

$$i_n(i_d) = i_d + g_m v_{gs} = \frac{1}{1 + g_m R_s} i_d$$

The mean-square value of the output noise due to i_d
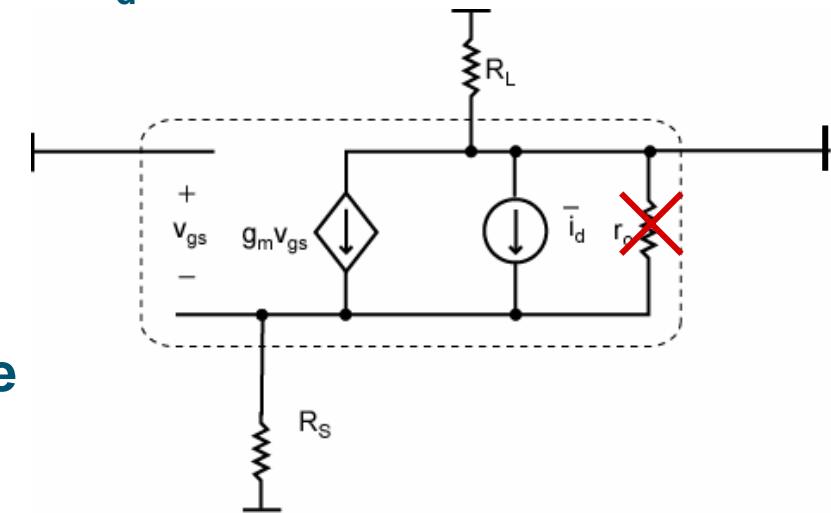
$$\overline{i_n(i_d)^2} = \frac{1}{(1 + g_m R_s)^2} 4kT\gamma g_{do}\Delta f$$



Noise Factor of CG Amplifier

$$\overline{i_{n2}^2} = \overline{i_{n1}^2} + \overline{i_n(i_d)^2}$$

$$F = \frac{\overline{i_{n2}^2}}{\overline{i_{n1}^2}} = \frac{\overline{i_{n1}^2} + \overline{i_n(i_d)^2}}{\overline{i_{n1}^2}}$$


$$F = 1 + \frac{\gamma}{\alpha} \cdot \frac{1}{g_m R_s}$$

For power match, $1/g_m = R_s$

$$F = 1 + \frac{\gamma}{\alpha}$$


This may be o.k. for broadband amplifiers. For narrowband amplifiers, we can improve the noise factor considerably while maintaining power match: inductors!

Inductor Degenerated CS Amp

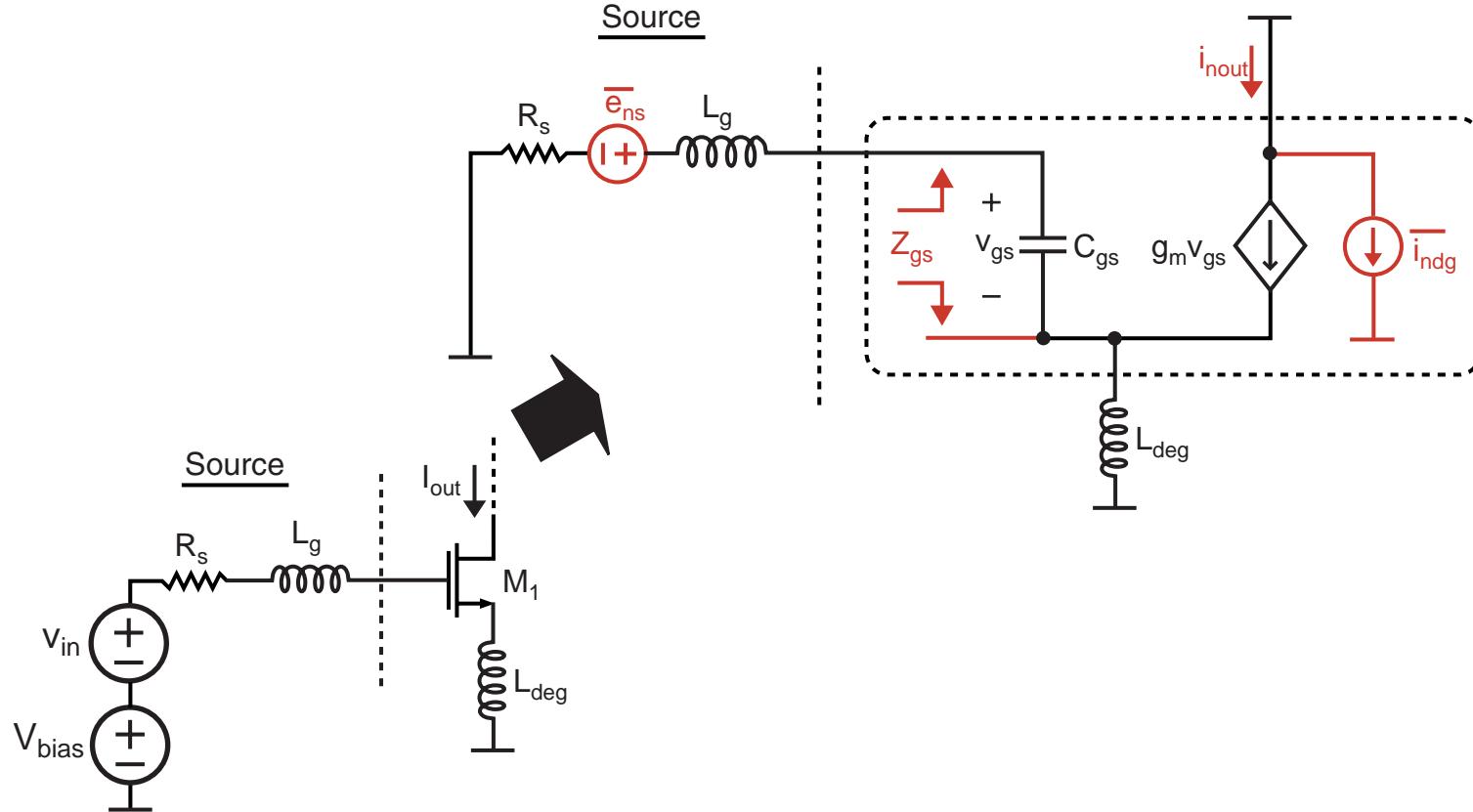

- Same as amp in Lecture 10 except for inductor degeneration
 - Note that noise analysis in Tom Lee's book does not include inductor degeneration (i.e., Table 12.1 (11.1))

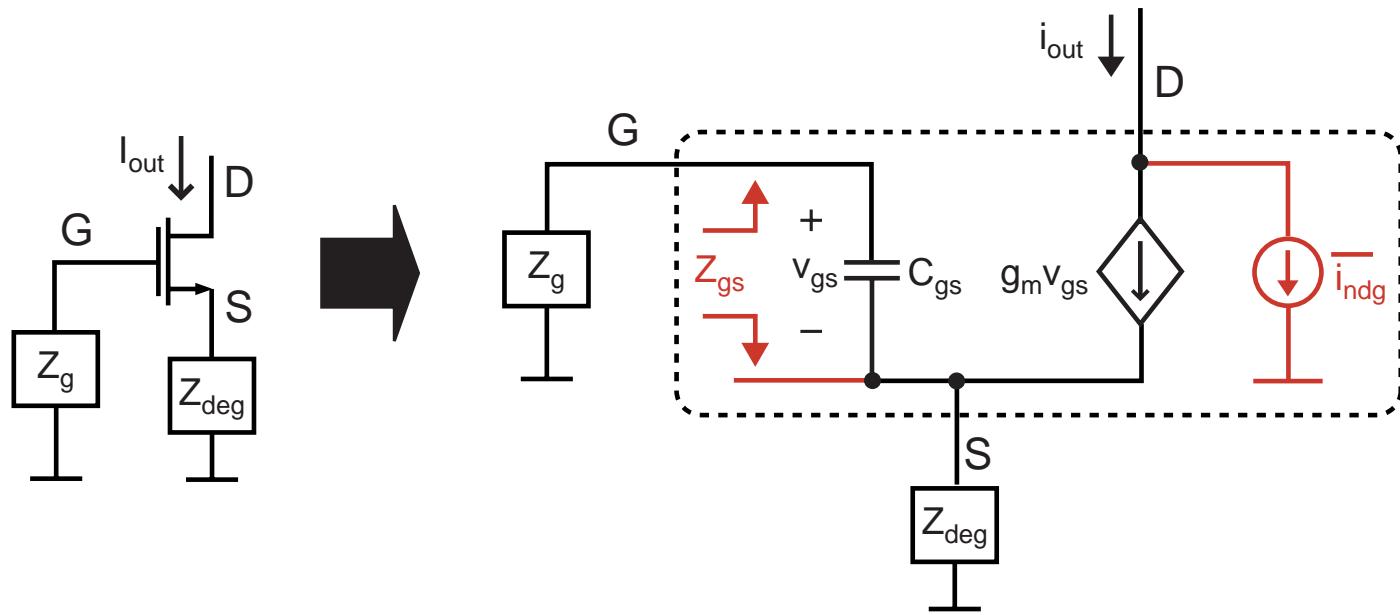Recall Small Signal Model for Noise Calculations




$$\frac{\overline{i_{ndg}^2}}{\Delta f} = \frac{\overline{i_{nd}^2}}{\Delta f} \left(|\eta|^2 + 2\text{Re} \{ c\chi_d \eta^* Z_{gsw} \} + \chi_d^2 |Z_{gsw}|^2 \right)$$

where: $\frac{\overline{i_{nd}^2}}{\Delta f} = 4kT\gamma g_{do}$, $\chi_d = \frac{g_m}{g_{do}} \sqrt{\frac{\delta}{5\gamma}}$, $Z_{gsw} = wC_{gs}Z_{gs}$

$$Z_{gs} = \frac{1}{jwC_{gs}} \parallel \frac{Z_{deg} + Z_g}{1 + g_m Z_{deg}}$$

$$\eta = 1 - \left(\frac{g_m Z_{deg}}{Z_{deg} + Z_g} \right) Z_{gs}$$

Key Assumption: Design for Power Match

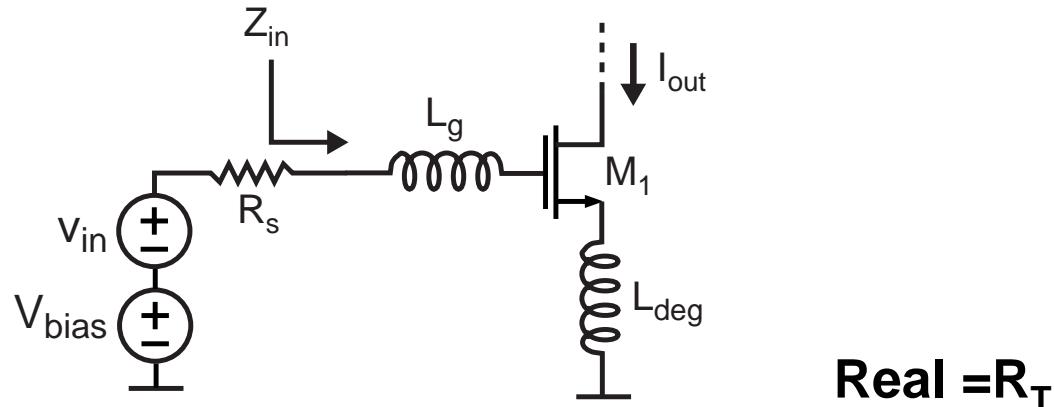

- Input impedance (from Lec 9)


$$Z_{in}(s) = \frac{1}{sC_{gs}} + s(L_{deg} + L_g) + \frac{g_m}{C_{gs}}L_{deg}$$

- Set to achieve pure resistance = R_s at frequency ω_o

$$\Rightarrow \frac{1}{\sqrt{(L_g + L_{deg})C_{gs}}} = \omega_o, \quad R_T = \frac{g_m}{C_{gs}}L_{deg} = R_s$$

Adding L_g gives additional degree of freedom to set ω_o and R_T independently

Key Assumption: Design for Power Match

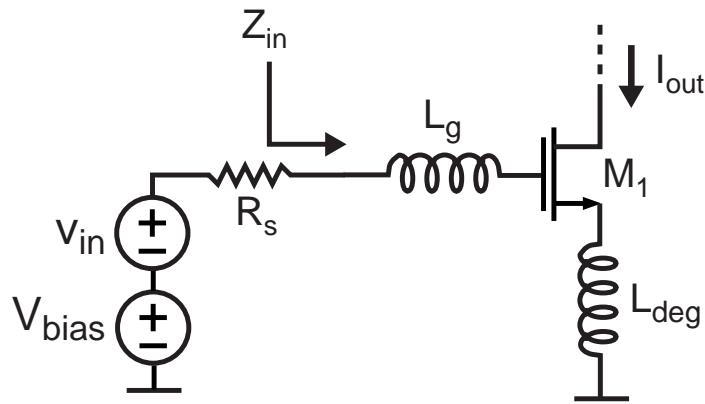


- The total impedance of the RLC circuit (including the source resistance)

$$Z(s) = \frac{1}{sC_{gs}} + s(L_{deg} + L_g) + \frac{g_m}{C_{gs}}L_{deg} + R_s$$

Thus Q is then

$$Q = \frac{1}{w_o C_{gs} 2R_s} = \frac{w_o (L_g + L_{deg})}{2R_s}$$

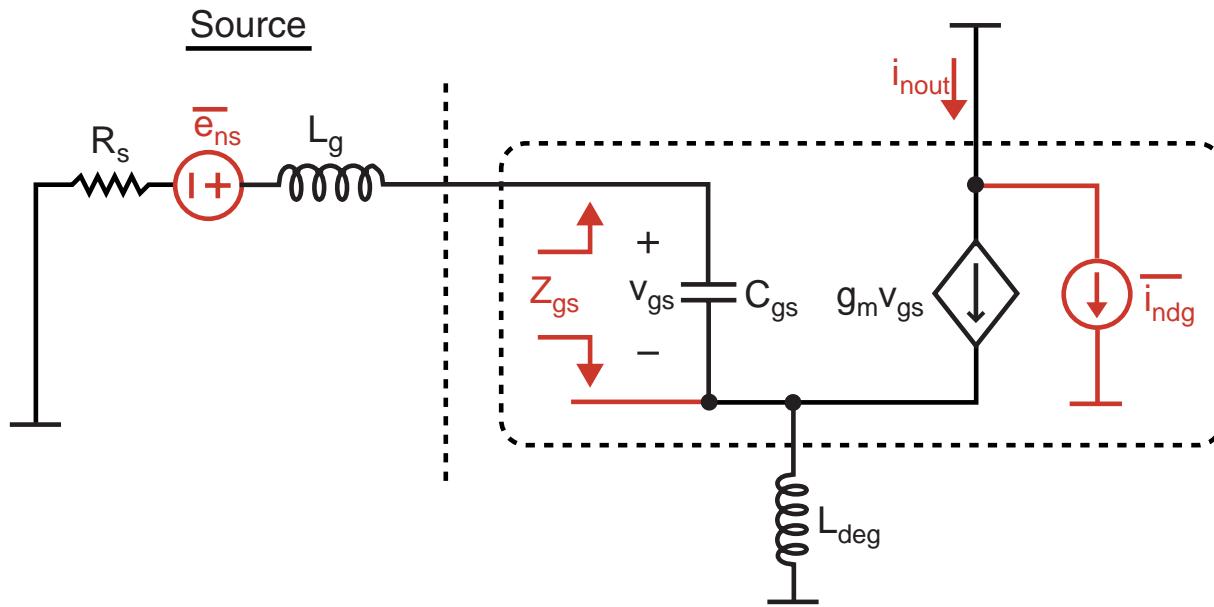Process and Topology Parameters for Noise Calculation




- Process parameters
 - For 0.18μ CMOS, we will assume the following

$$c = -j0.55, \quad \gamma = 3, \quad \delta = 2\gamma = 6, \quad \frac{g_m}{g_{do}} = \frac{1}{2} \Rightarrow \chi_d = 0.32$$

- Circuit topology parameters Z_g and Z_{deg}


$$Z_g = R_s + jwL_g, \quad Z_{deg} = jwL_{deg}$$

Calculation of Z_{gs}

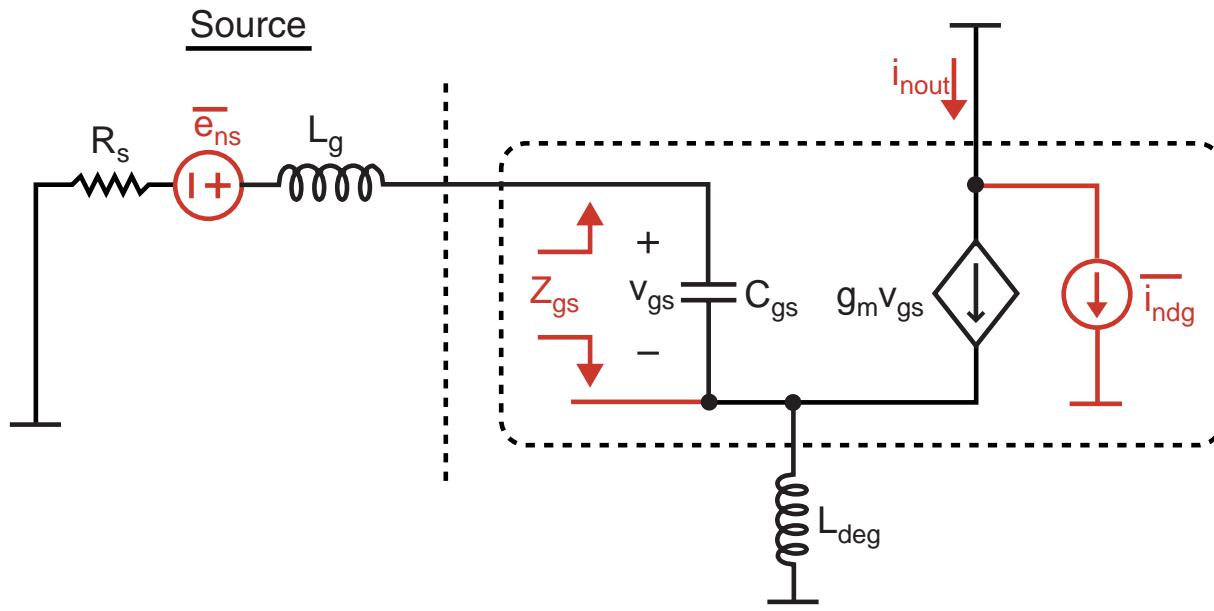

$$\begin{aligned}
 Z_{gs} &= \frac{1}{jwC_{gs}} \left| \left| \frac{Z_{deg} + Z_g}{1 + g_m Z_{deg}} \right| \right| \frac{1}{jw_o C_{gs}} \left| \left| \frac{jw_o(L_{deg} + L_g) + R_s}{1 + g_m j w_o L_{deg}} \right. \right. \\
 &= \frac{jw_o(L_{deg} + L_g) + R_s}{1 - w_o^2 C_{gs}(L_{deg} + L_s) + jw_o(g_m L_{deg} + R_s C_{gs})} \\
 &= \boxed{\frac{jw_o(L_{deg} + L_g) + R_s}{jw_o(g_m L_{deg} + R_s C_{gs})}}
 \end{aligned}$$

Calculation of η

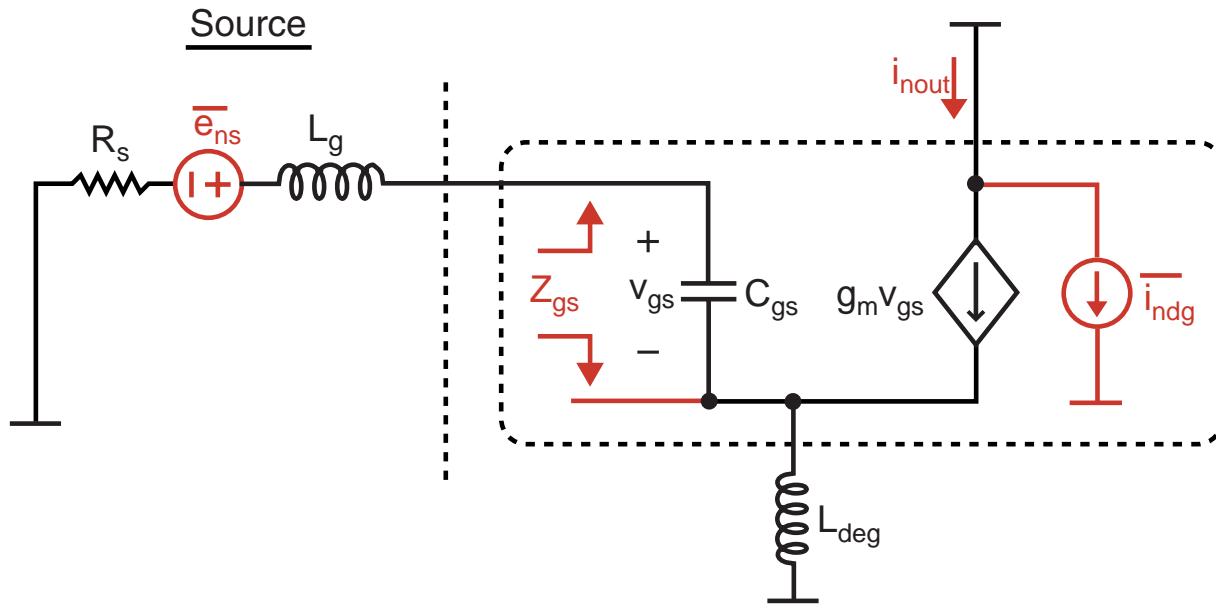

$$\begin{aligned}
 \eta &= 1 - \left(\frac{g_m Z_{deg}}{Z_{deg} + Z_g} \right) Z_{gs} = 1 - \frac{g_m j w_o L_{deg}}{j w_o (L_{deg} + L_g) + R_s} Z_{gs} \\
 &= 1 - \frac{g_m j w_o L_{deg}}{j w_o (g_m L_{deg} + R_s C_{gs})} = 1 - \frac{(g_m / C_{gs}) L_{deg}}{(g_m / C_{gs}) L_{deg} + R_s} \\
 &= 1 - \frac{R_s}{R_s + R_s} = \boxed{\frac{1}{2}}
 \end{aligned}$$

Calculation of Z_{gsw}

- **By definition**

$$Z_{gsw} = w_o C_{gs} Z_{gs} \quad \left(Q = \frac{1}{w_o C_{gs} 2 R_s} = \frac{w_o (L_g + L_{deg})}{2 R_s} \right)$$

- **Calculation**

$$\begin{aligned} Z_{gsw} &= w_o C_{gs} \frac{j w_o (L_{deg} + L_g) + R_s}{j w_o (g_m L_{deg} + R_s C_{gs})} \\ &= \frac{j w_o^2 C_{gs} (L_{deg} + L_g) + w_o C_{gs} R_s}{j w_o (g_m L_{deg} + R_s C_{gs})} \\ &= \frac{j 1 + 1/(2Q)}{j w_o (g_m L_{deg} + R_s C_{gs})} \\ &= \frac{j 1 + 1/(2Q)}{j w_o C_{gs} ((g_m / C_{gs}) L_{deg} + R_s)} \\ &= \frac{j 1 + 1/(2Q)}{j w_o C_{gs} (R_s + R_s)} = \frac{j 1 + 1/(2Q)}{j 1 / Q} = \end{aligned}$$

$$\boxed{\frac{1}{2}(2Q - j)}$$

Calculation of Output Current Noise

- Step 3: Plug in values to noise expression for i_{ndg}


$$\frac{\overline{i_{ndg}^2}}{\Delta f} = \frac{\overline{i_{nd}^2}}{\Delta f} \left(|\eta|^2 + 2\operatorname{Re} \{-j|c|\chi_d \eta^* Z_{gsw}\} + \chi_d^2 |Z_{gsw}|^2 \right)$$

$$\text{where } \eta = \frac{1}{2}, \quad Z_{gsw} = \frac{1}{2}(2Q - j)$$

$$\Rightarrow \frac{\overline{i_{ndg}^2}}{\Delta f} = \frac{\overline{i_{nd}^2}}{\Delta f} \left(\frac{1}{4} + 2\operatorname{Re} \left\{ -j|c|\chi_d \frac{1}{4}(2Q - j) \right\} + \chi_d^2 \frac{1}{4} |2Q - j|^2 \right)$$

$$= \frac{\overline{i_{nd}^2}}{\Delta f} \frac{1}{4} \left(1 - 2|c|\chi_d + \chi_d^2 (4Q^2 + 1) \right)$$

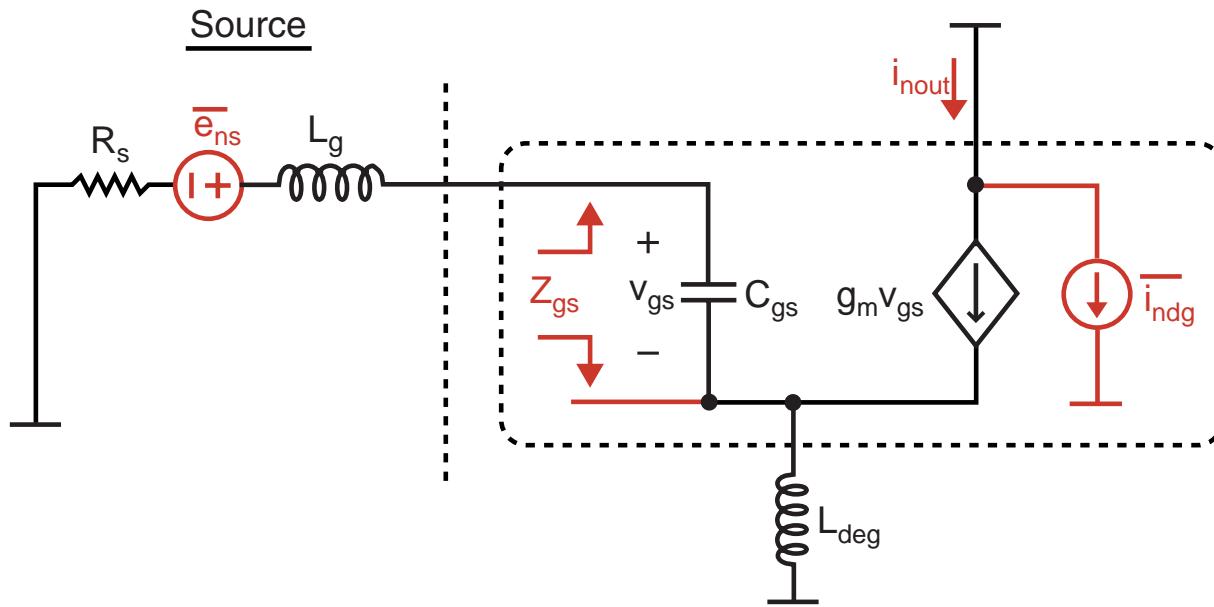Compare Noise With and Without Inductor Degeneration




- From Lecture 10, we derived for $L_{deg} = 0$, $\omega_o^2 = 1/(L_g C_{gs})$

$$\frac{\overline{i_{ndg}^2}}{\Delta f} = \frac{\overline{i_{nd}^2}}{\Delta f} \left(1 - 2|c|\chi_d + \chi_d^2(Q^2 + 1) \right)$$

- We now have for $(g_m/C_{gs})L_{deg} = R_s$, $\omega_o^2 = 1/((L_g + L_{deg})C_{gs})$

$$\frac{\overline{i_{ndg}^2}}{\Delta f} = \frac{\overline{i_{nd}^2}}{\Delta f} \frac{1}{4} \left(1 - 2|c|\chi_d + \chi_d^2(4Q^2 + 1) \right)$$

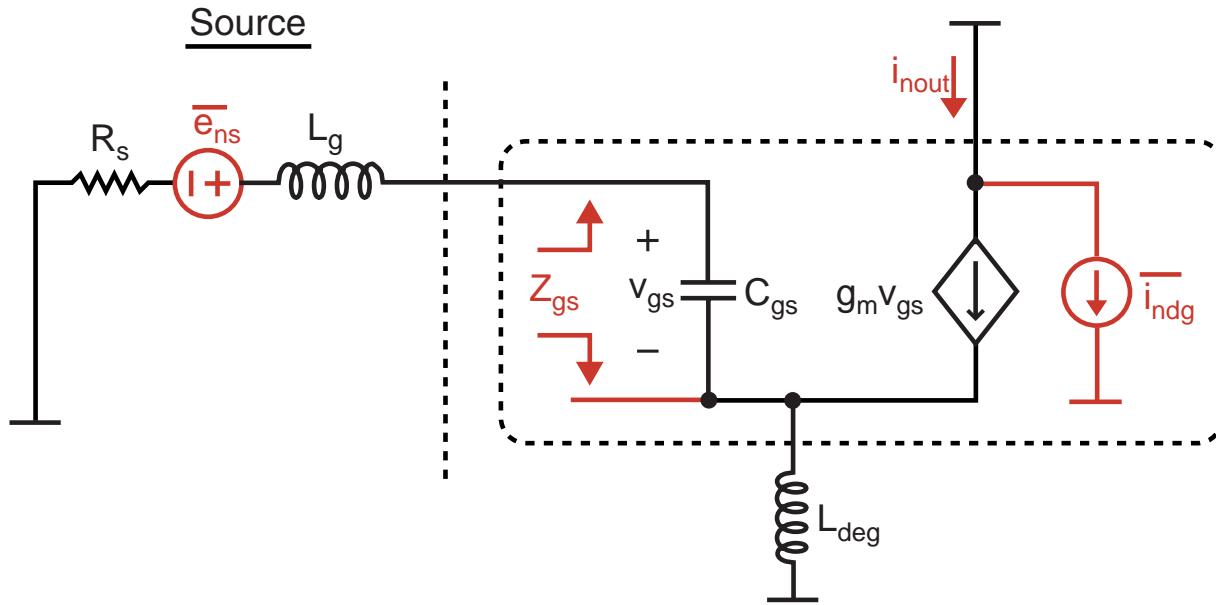Derive Noise Factor for Inductor Degenerated Amp




- Recall the alternate expression for Noise Factor derived in Lecture 11

$$F = \frac{\text{total output noise power}}{\text{output noise due to input source}} = \frac{i_{nout(tot)}^2}{i_{nout(in)}^2}$$

- We now know the output noise due to the transistor noise
 - We need to determine the output noise due to the source resistance

Output Noise Due to Source Resistance

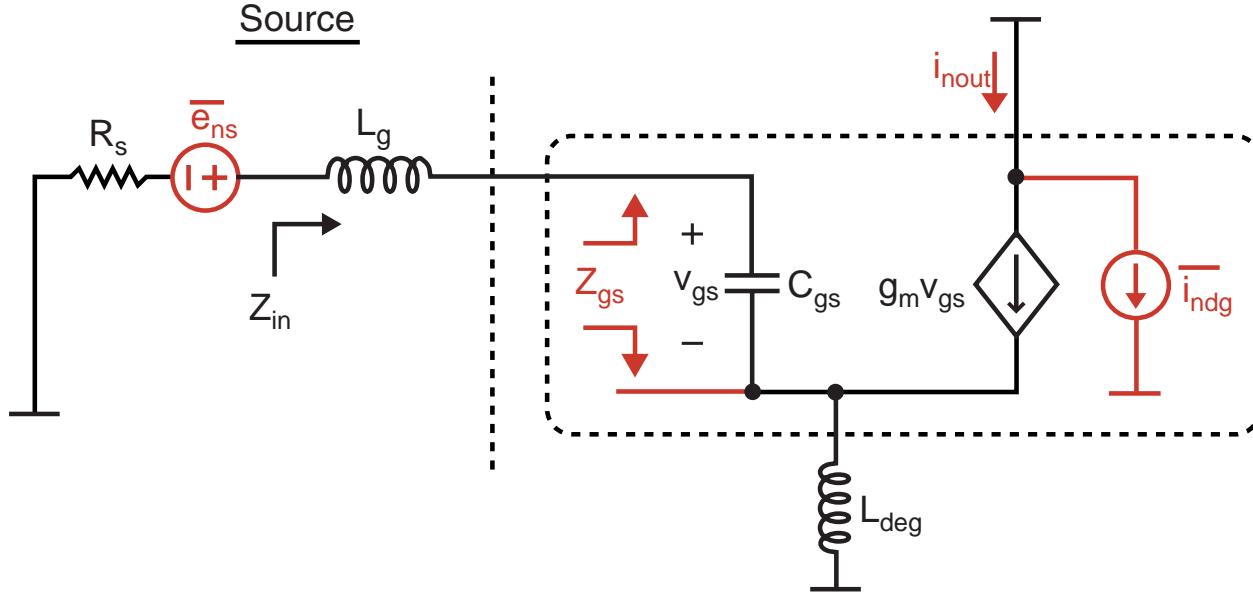

$$Z_{in} = \frac{1}{jw_o C_{gs}} + jw_o(L_{deg} + L_g) + \frac{g_m}{C_{gs}}L_{deg} = R_s$$

$$\Rightarrow v_{gs} = \frac{\overline{e_{ns}}}{R_s + Z_{in}} \left(\frac{1}{jw_o C_{gs}} \right) = \frac{\overline{e_{ns}}}{2R_s} \left(\frac{1}{jw_o C_{gs}} \right) = \left(\frac{Q}{j} \right) \overline{e_{ns}}$$


$$\Rightarrow i_{nout} = g_m \left(\frac{Q}{j} \right) \overline{e_{ns}}$$

$$\Rightarrow \overline{i_{nout}^2} = (g_m Q)^2 \overline{e_{ns}^2}$$


Noise Factor for Inductor Degenerated Amplifier

$$\begin{aligned}\text{Noise Factor} &= \frac{(g_m Q)^2 \overline{e_{ns}^2} + \overline{i_{ndg}^2} / \Delta f}{(g_m Q)^2 \overline{e_{ns}^2}} = 1 + \frac{\overline{i_{ndg}^2} / \Delta f}{(g_m Q)^2 \overline{e_{ns}^2}} \\ &= 1 + \frac{4kT\gamma g_{do}(1/4)(1 - 2|c|\chi_d + \chi_d^2(4Q^2 + 1))}{(g_m Q)^2 4kT R_s} \\ &= 1 + \left(\frac{1}{g_m Q R_s} \right) \gamma \left(\frac{g_{do}}{g_m} \right) \frac{1}{4Q} (1 - 2|c|\chi_d + (4Q^2 + 1)\chi_d^2) \\ &= 1 + \left(\frac{2w_o R_s C_{gs}}{g_m R_s} \right) \gamma \left(\frac{g_{do}}{g_m} \right) \frac{1}{4Q} (1 - 2|c|\chi_d + (4Q^2 + 1)\chi_d^2) \\ &= 1 + \left(\frac{w_o}{w_t} \right) \gamma \left(\frac{g_{do}}{g_m} \right) \frac{1}{2Q} (1 - 2|c|\chi_d + (4Q^2 + 1)\chi_d^2)\end{aligned}$$

Noise Factor scaling coefficient

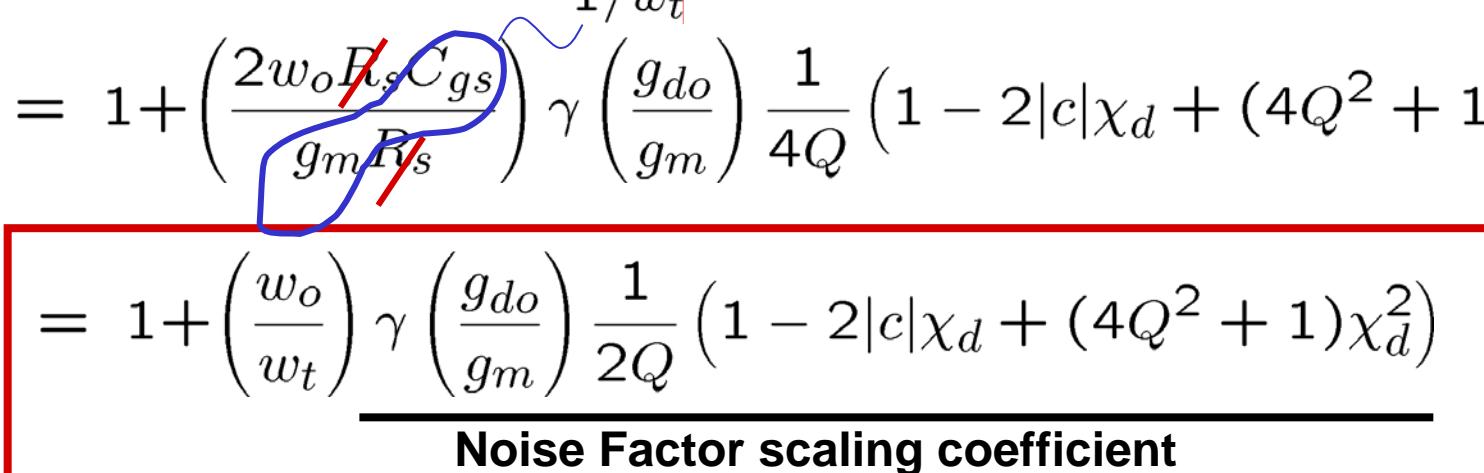

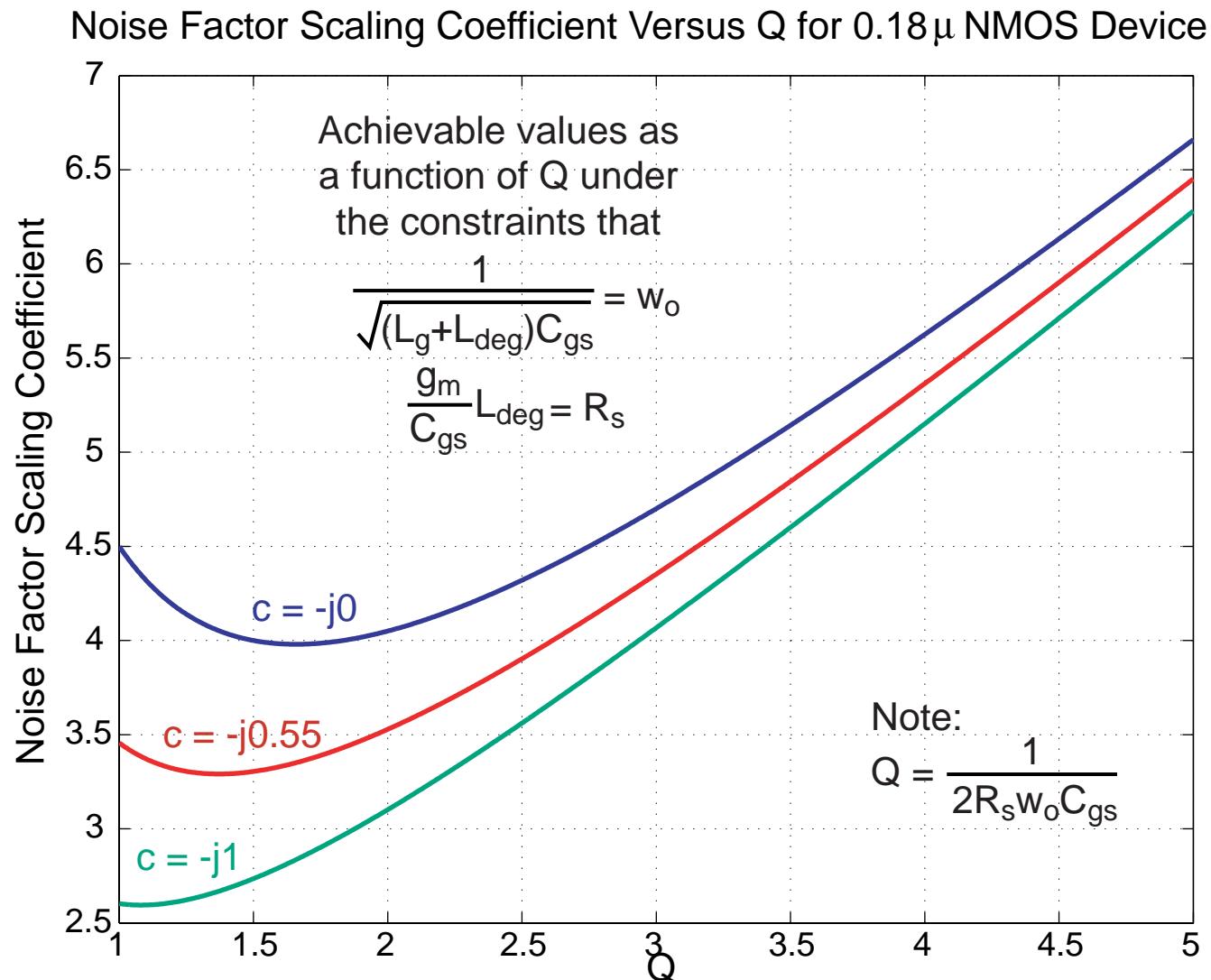Noise Factor Scaling Coefficient Versus Q



Noise Factor Comparison


- Inductor Degenerated CS

$$\text{Noise Factor} = \frac{1 + \left(\frac{w_o}{w_t}\right) \gamma \left(\frac{g_{do}}{g_m}\right) \frac{1}{2Q} (1 - 2|c|\chi_d + (4Q^2 + 1)\chi_d^2)}{\text{Noise Factor scaling coefficient}}$$


- Non degenerated (From Lecture 10)

$$\text{Noise Factor} = \frac{1 + \left(\frac{w_o}{w_t}\right) \gamma \left(\frac{g_{do}}{g_m}\right) \frac{1}{Q} (1 - 2|c|\chi_d + (Q^2 + 1)\chi_d^2)}{\text{Noise Factor scaling coefficient}}$$

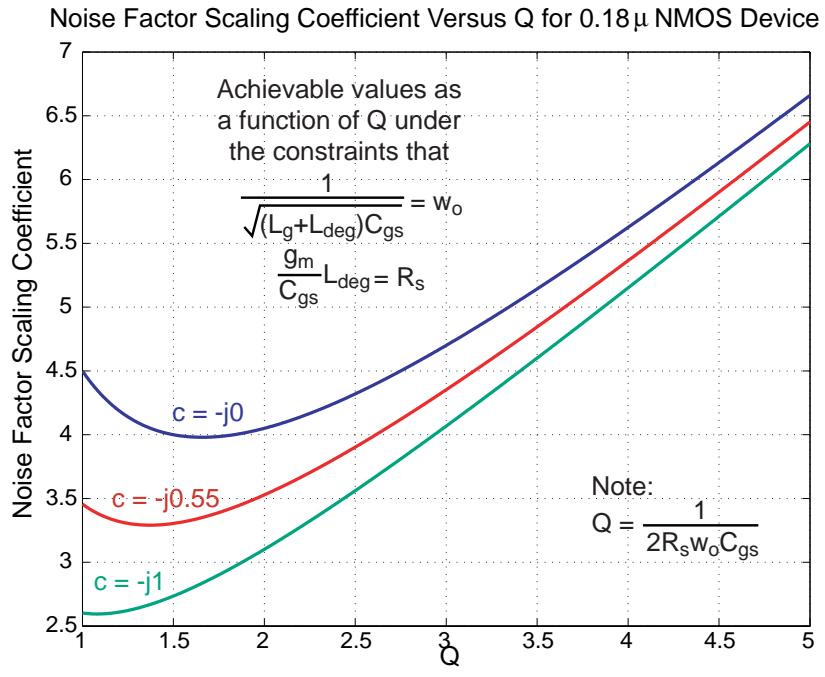Noise Factor Scaling Coefficient Comparison



With degeneration

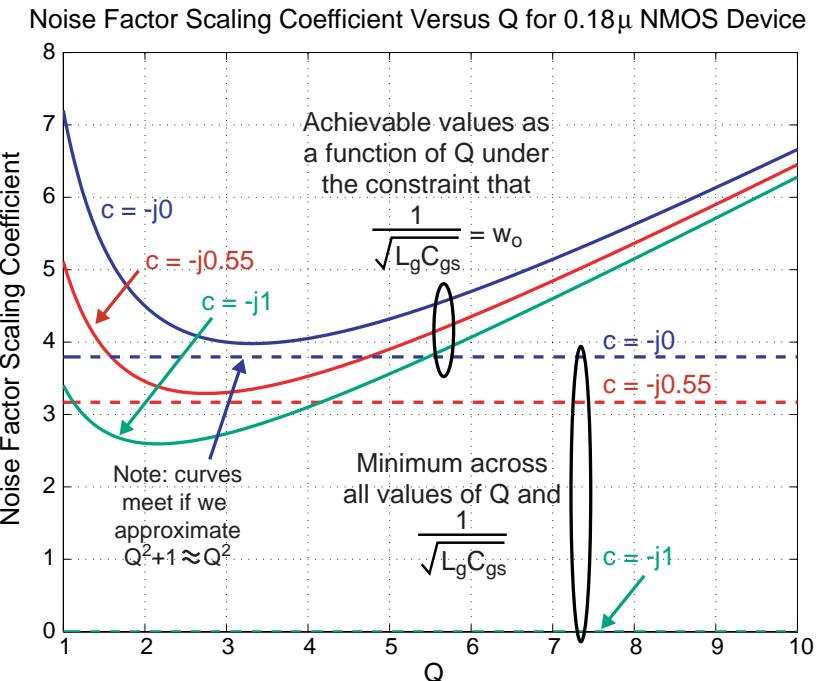

Without degeneration

Achievable Noise Figure in 0.18μ with Power Match

- Suppose we desire to build a narrowband LNA with center frequency of 1.8 GHz in 0.18μ CMOS ($c=-j0.55$)
 - From Hspice – at $V_{gs} = 1$ V with NMOS ($W=1.8\mu$, $L=0.18\mu$)
 - measured $g_m = 871 \mu S$, $C_{gs} = 2.9 fF$

$$\Rightarrow w_t \approx \frac{g_m}{C_{gs}} = \frac{871 \times 10^{-6}}{2.9 \times 10^{-15}} = 2\pi(47.8GHz)$$

$$\Rightarrow \frac{w_o}{w_t} = \frac{2\pi 1.8e9}{2\pi 47.8e9} \approx \frac{1}{26.6}$$

- Looking at previous curve, with $Q \approx 1.4$ we achieve a Noise Factor scaling coefficient ≈ 3.25

$$\Rightarrow \text{Noise Factor} \approx 1 + \frac{1}{26.6} 3.25 \approx 1.12$$

$$\Rightarrow \text{Noise Figure} = 10 \log(1.13) \approx 0.49 dB$$

Component Values for Minimum NF with Power Match

- Assume $R_s = 50$ Ohms, $Q = 1.4$, $f_o = 1.8$ GHz, $f_t = 47.8$ GHz

- C_{gs} calculated as

$$Q = \frac{1}{2R_s w_o C_{gs}}$$

$$\Rightarrow C_{gs} = \frac{1}{2R_s w_o Q} = \frac{1}{2(50)2\pi1.8e9(1.4)} = 631fF$$

- L_{deg} calculated as



$$\frac{g_m}{C_{gs}} L_{deg} = R_s \Rightarrow L_{deg} = \frac{R_s}{w_t} = \frac{50}{2\pi47.8e9} = 0.17nH$$

- L_g calculated as

$$\frac{1}{\sqrt{(L_g + L_{deg})C_{gs}}} = w_o \Rightarrow L_g = \frac{1}{w_o^2 C_{gs}} - L_{deg}$$

$$\Rightarrow L_g = \frac{1}{(2\pi1.8e9)^2 631e-15} - 0.17e-9 = 12.2nH$$

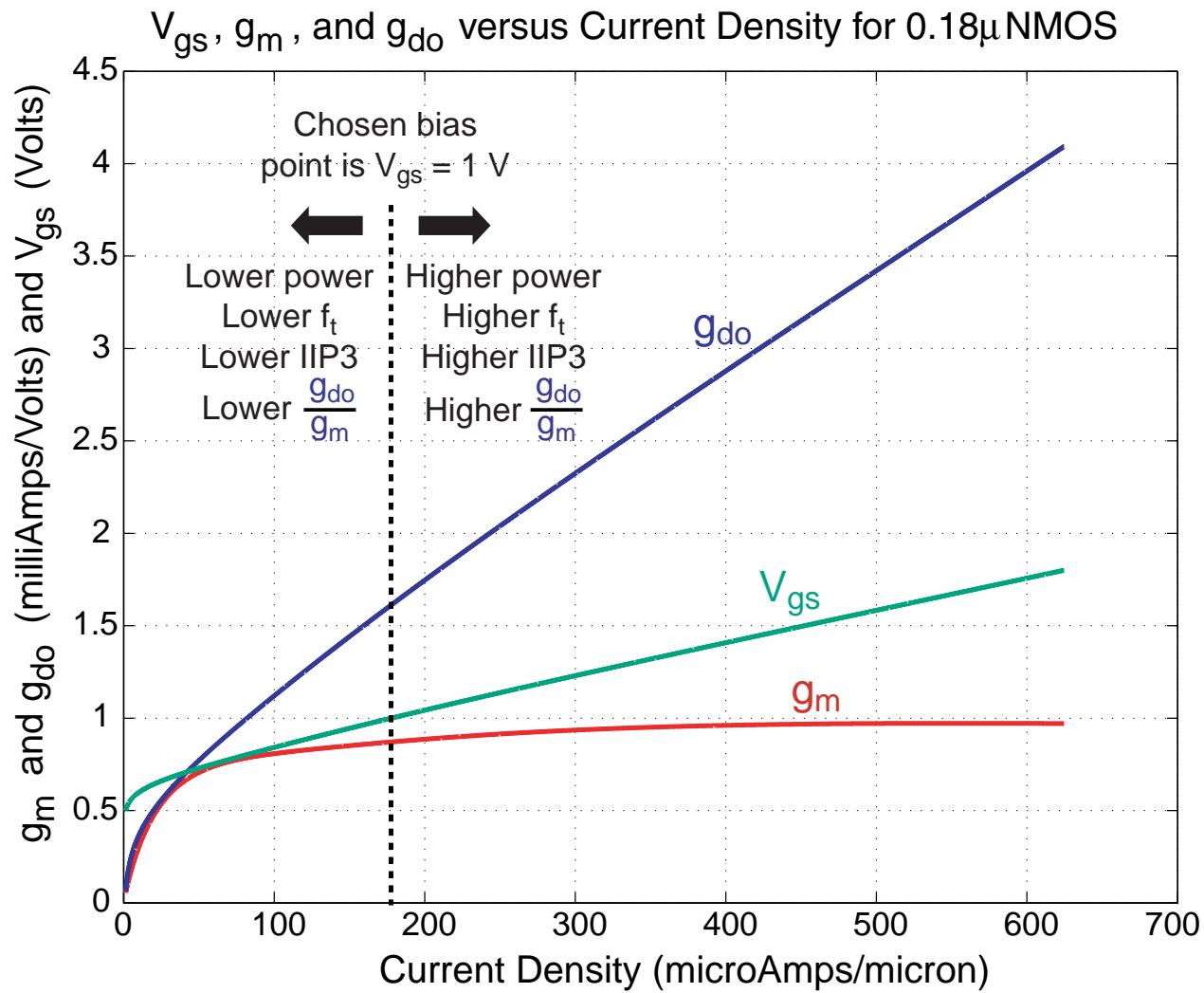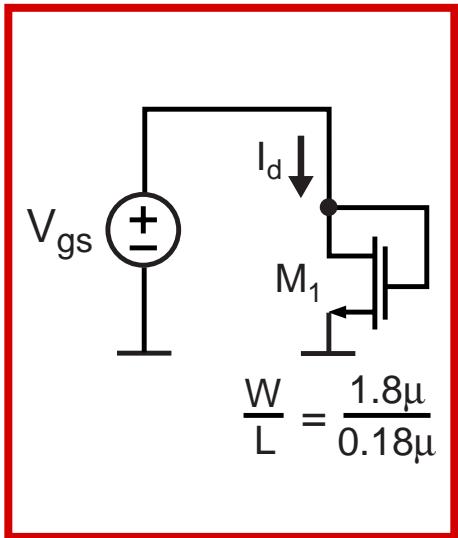Have We Chosen a Good Bias Point? ($V_{gs} = 1V$)



- Note: IIP3 is also a function of Q

Calculation of Bias Current for Example Design

- Calculate current density from previous plot

$$V_{gs} = 1V \Rightarrow I_{dens} \approx 175\mu A/\mu m$$

- Calculate W from HSpice simulation (assume L=0.18 μm)

$$C_{gs} = 2.9fF \text{ for } W = 1.8\mu m \Rightarrow W = \frac{631fF}{2.9fF} 1.8\mu m \approx 392\mu m$$

- Could also compute this based on C_{ox} value
- Calculate bias current

$$I_{bias} = I_{den}W = (175\mu A/\mu m)(392\mu m) \approx 69mA$$

- Problem: this is not low power!!