



6.776

High Speed Communication Circuits

Lecture 4

S-Parameters and Impedance Transformers


Massachusetts Institute of Technology

February 10, 2005

Copyright © 2005 by Hae-Seung Lee and Michael H.
Perrott


What Happens When the Wave Hits a Boundary?

- Reflections can occur

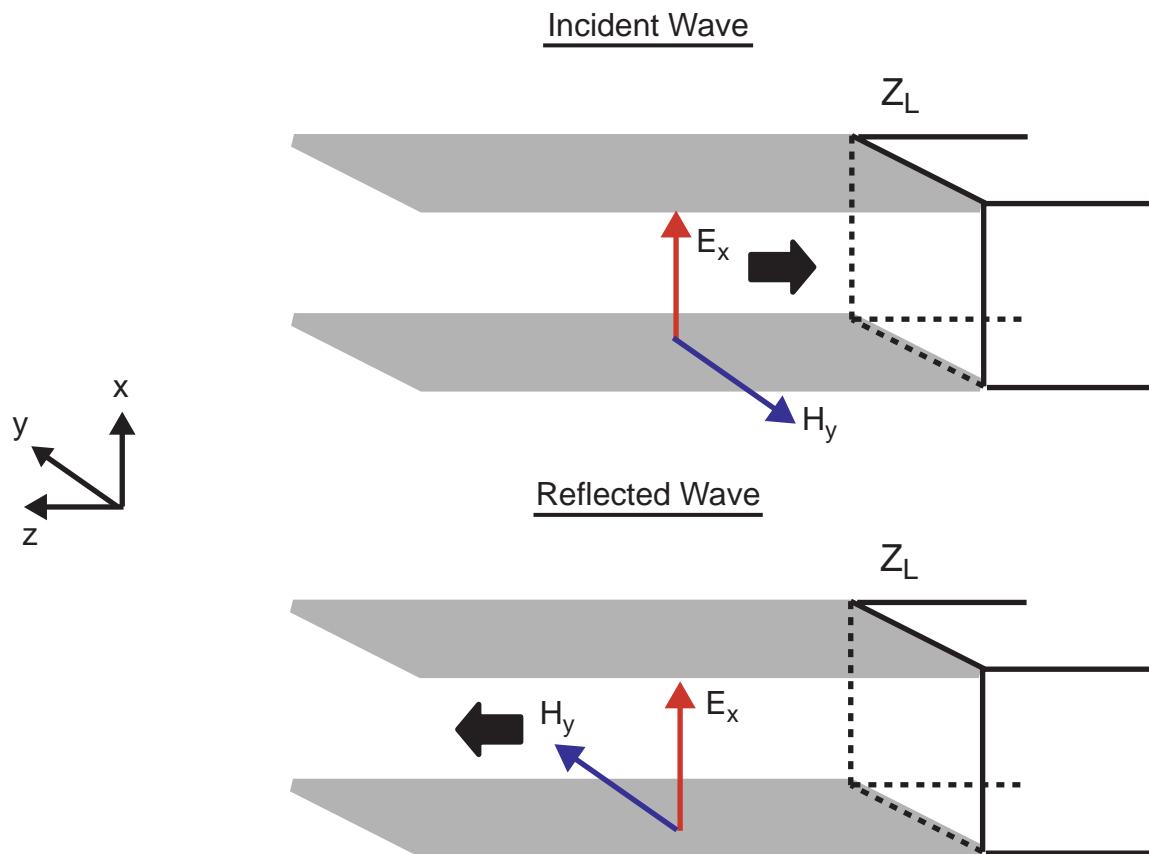


What Happens When the Wave Hits a Boundary?

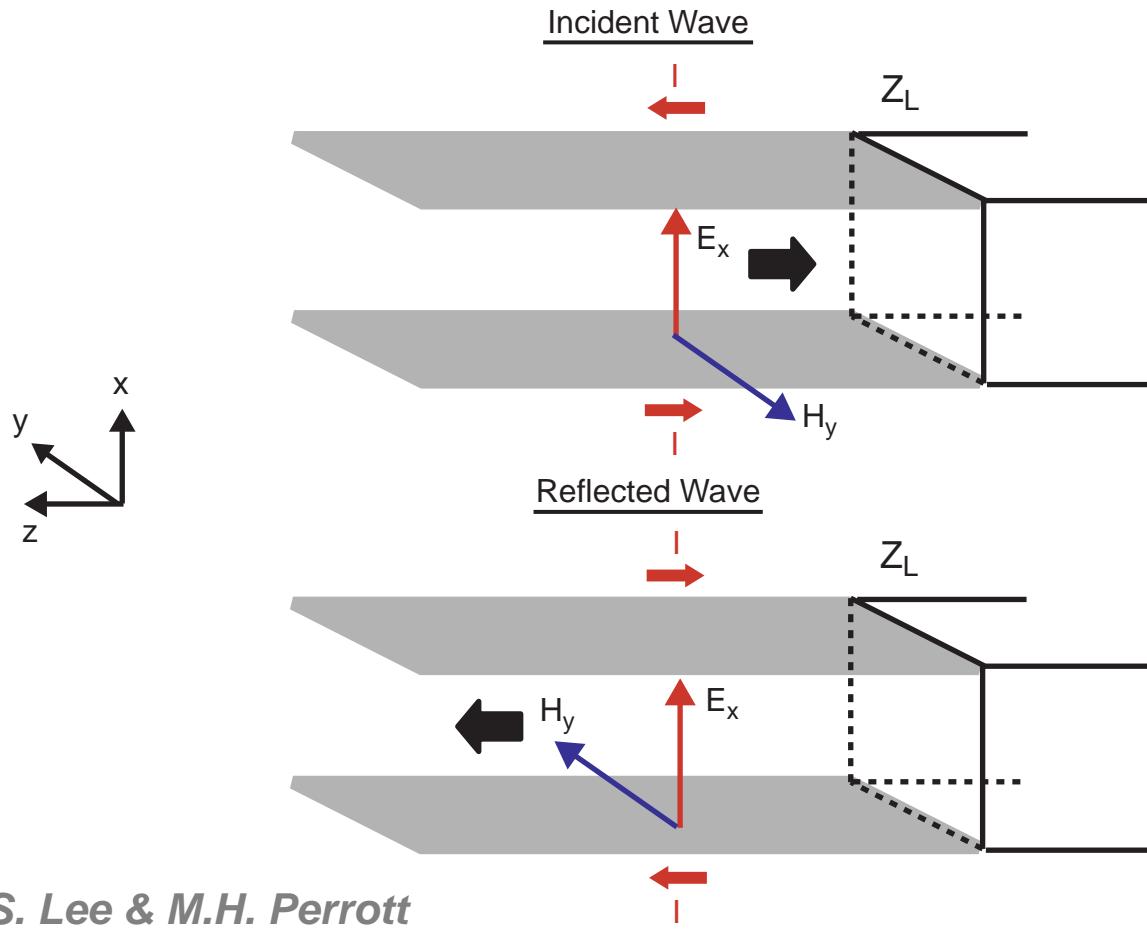- At boundary
 - Orientation of H-field flips with respect to E-field
 - Current reverses direction with respect to voltage



What Happens At The Load Location?

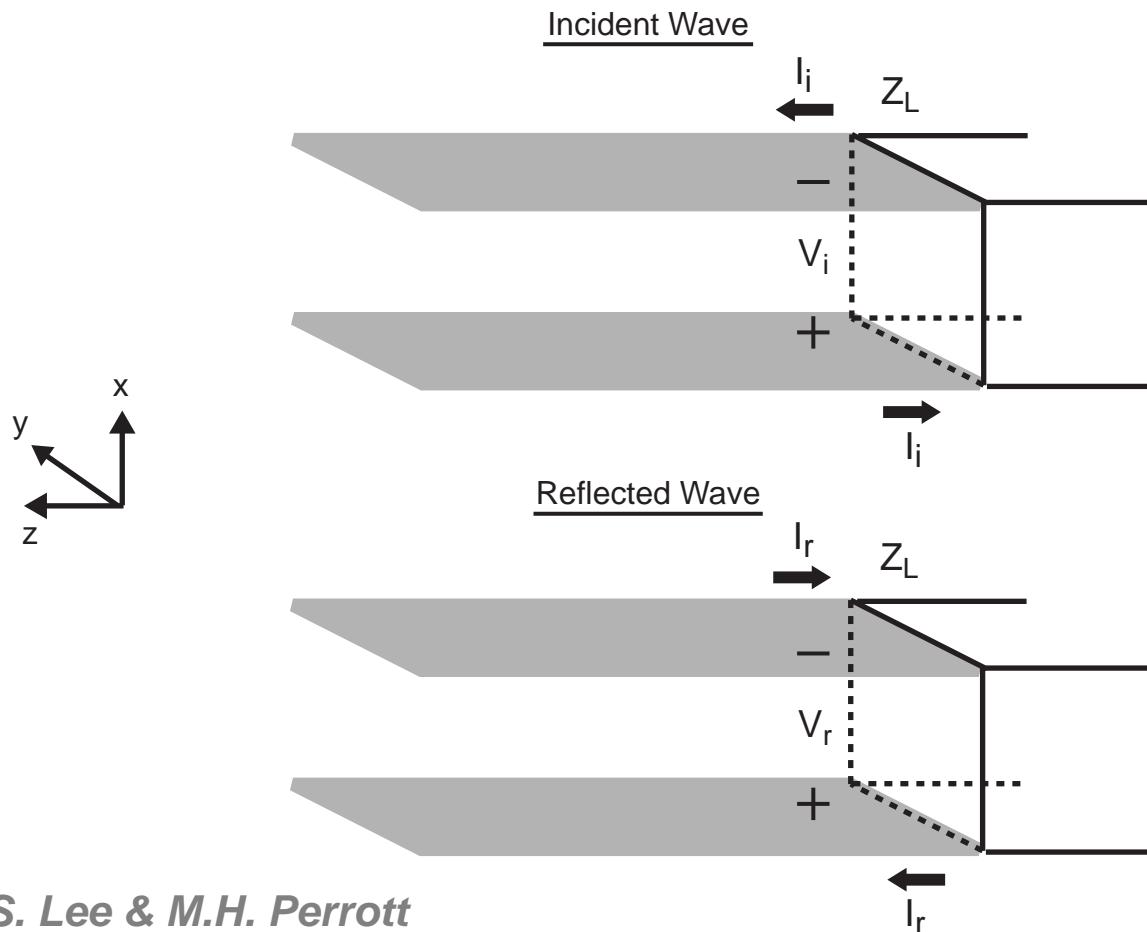- Voltage and currents at load are ratioed according to the load impedance



Voltage at Load

$$V_i + V_r$$

Current at Load

$$I_i - I_r$$

Ratio at Load

$$\frac{V_i + V_r}{I_i - I_r} = Z_L$$

Relate to Characteristic Impedance

- From previous slide

$$\frac{V_i + V_r}{I_i - I_r} = \frac{V_i}{I_i} \left(\frac{1 + V_r/V_i}{1 - I_r/I_i} \right) = Z_L$$

- Voltage and current ratio in transmission line set by its characteristic impedance

$$\frac{V_i}{I_i} = \frac{V_r}{I_r} = Z_o \quad \Rightarrow \quad \frac{I_r}{I_i} = \frac{V_r}{V_i}$$

- Substituting:

$$Z_o \left(\frac{1 + V_r/V_i}{1 - V_r/V_i} \right) = Z_L$$

Define Reflection Coefficient

- **Definition:** $\Gamma_L = \frac{V_r}{V_i}$
 - No reflection if $\Gamma_L = 0$
- Relation to load and characteristic impedances

$$Z_o \left(\frac{1 + \Gamma_L}{1 - \Gamma_L} \right) = Z_L$$


- Alternate expression

$$\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o}$$

- No reflection if $Z_L = Z_o$


Parameterization of High Speed Circuits/Passives

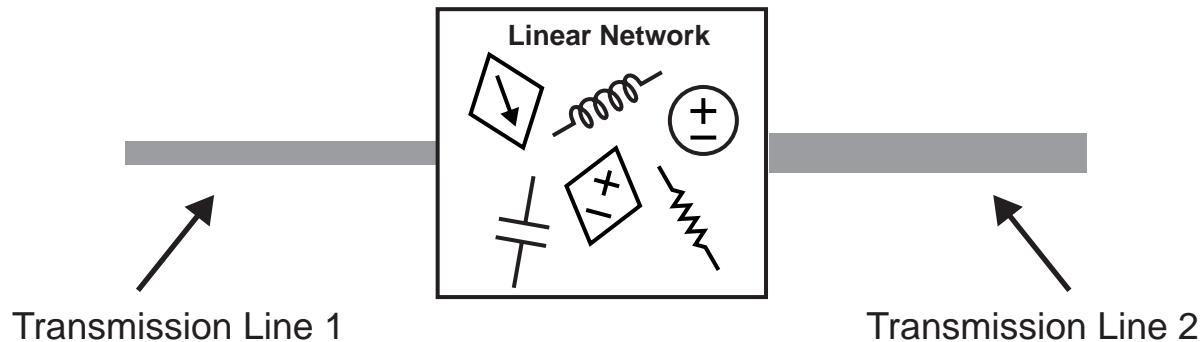- Circuits or passive structures are often connected to transmission lines at high frequencies
 - How do you describe their behavior?




Calculate Response to Input Voltage Sources

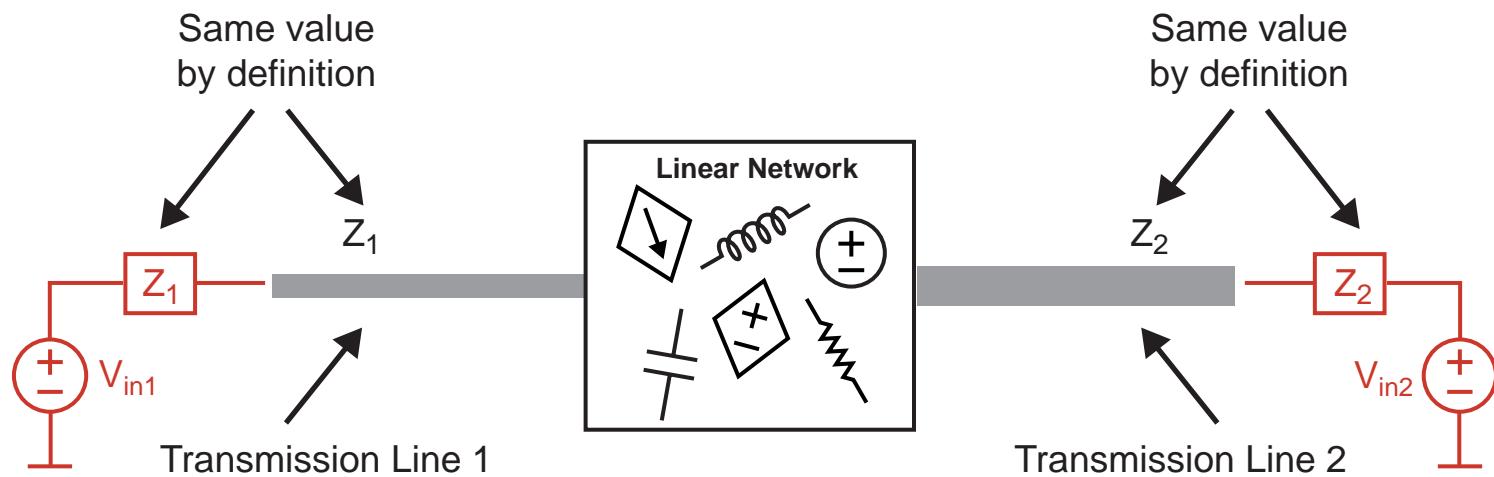- Assume source impedances match their respective transmission lines




Calculate Response to Input Voltage Sources

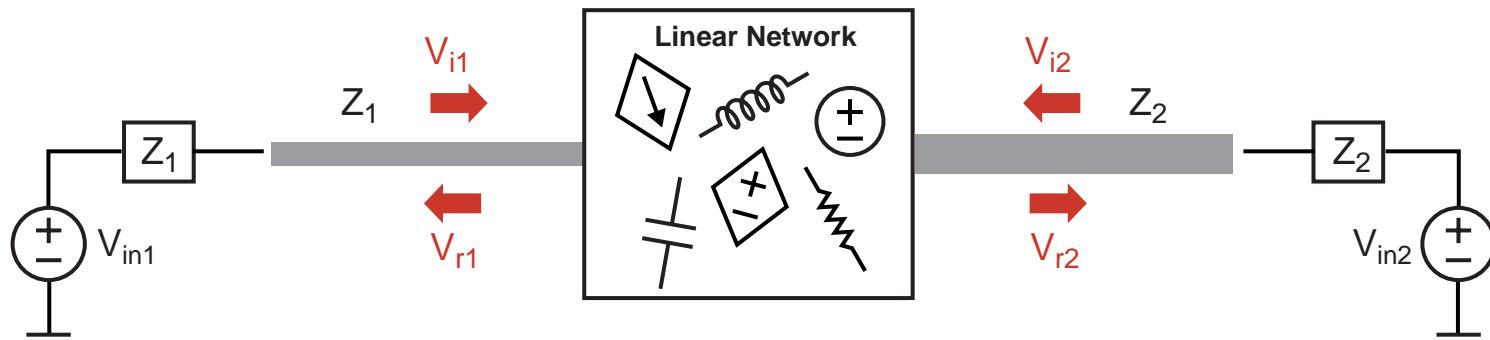- Sources create incident waves on their respective transmission line
- Circuit/pассив network causes
 - Reflections on same transmission line
 - Feedthrough to other transmission line



Calculate Response to Input Voltage Sources

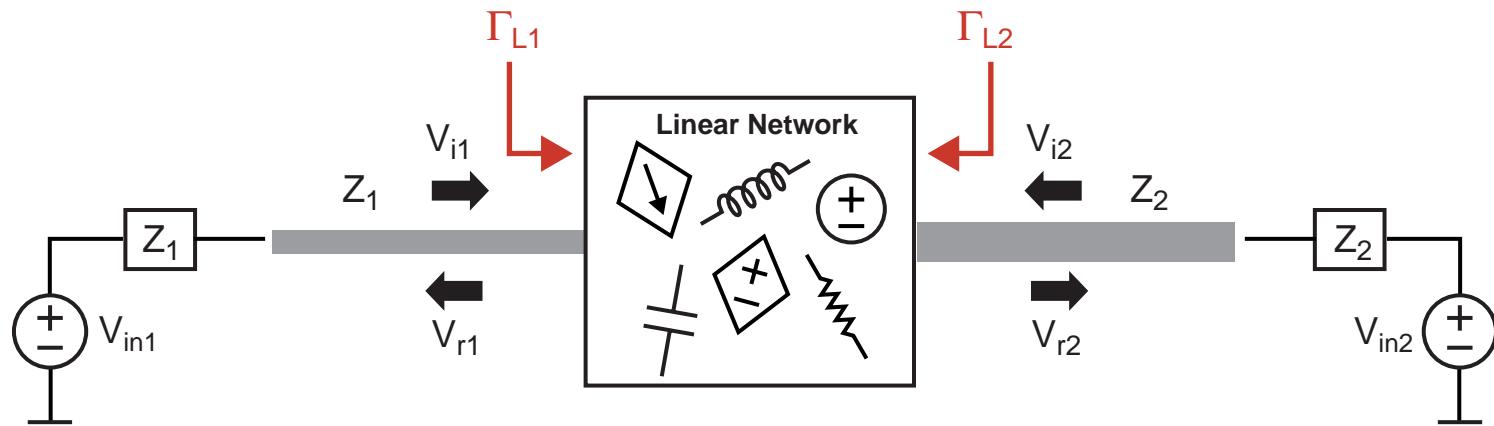
- Reflections on same transmission line are parameterized by Γ_L
 - Note that Γ_L is generally different on each side of the circuit/pассив network



How do we parameterize feedthrough to the other transmission line?

S-Parameters – Definition

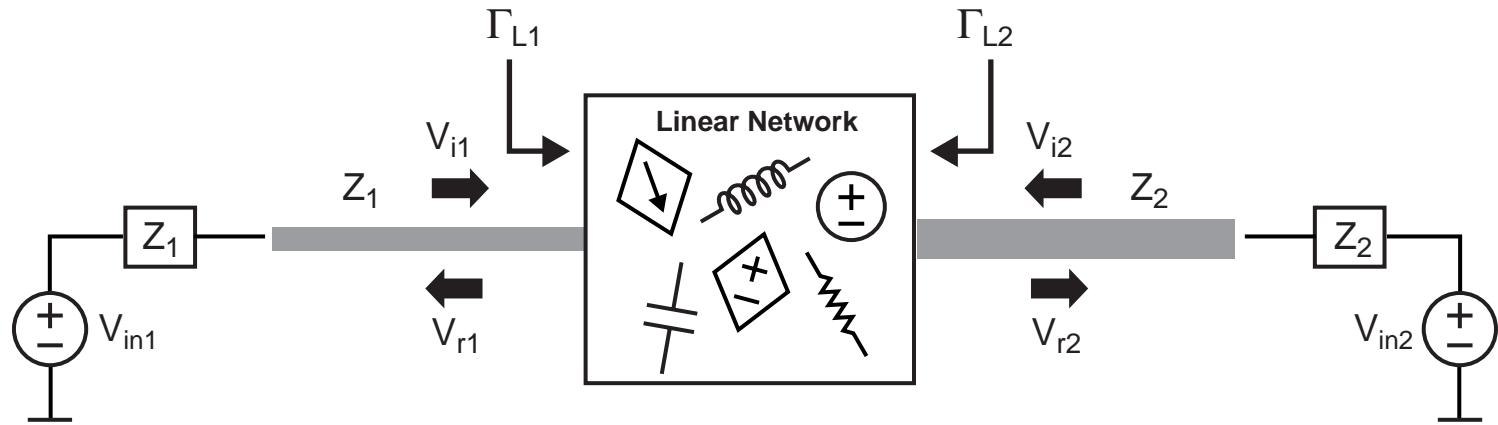- Model circuit/pассивный сеть using 2-port techniques
 - Similar idea to Thevenin/Norton modeling




- Defining equations:

$$\frac{V_{r1}}{\sqrt{Z_1}} = S_{11} \frac{V_{i1}}{\sqrt{Z_1}} + S_{12} \frac{V_{i2}}{\sqrt{Z_2}}$$

$$\frac{V_{r2}}{\sqrt{Z_2}} = S_{21} \frac{V_{i1}}{\sqrt{Z_1}} + S_{22} \frac{V_{i2}}{\sqrt{Z_2}}$$

S-Parameters – Calculation/Measurement

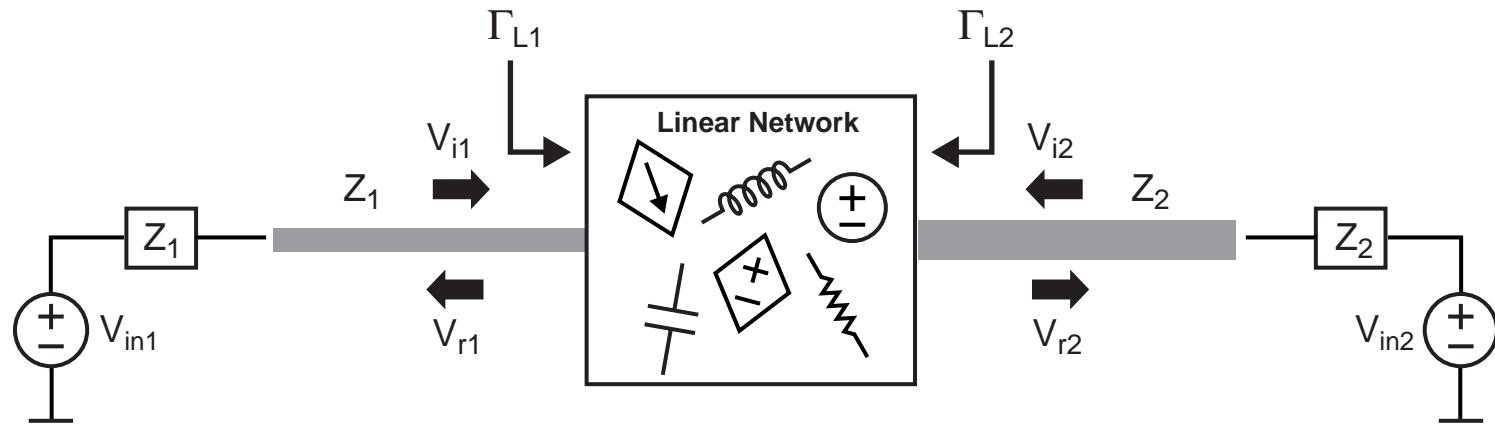

$$\frac{V_{r1}}{\sqrt{Z_1}} = S_{11} \frac{V_{i1}}{\sqrt{Z_1}} + S_{12} \frac{V_{i2}}{\sqrt{Z_2}}$$

$$\frac{V_{r2}}{\sqrt{Z_2}} = S_{21} \frac{V_{i1}}{\sqrt{Z_1}} + S_{22} \frac{V_{i2}}{\sqrt{Z_2}}$$

set $V_{in2} = 0$

$$\Rightarrow S_{11} = \frac{V_{r1}}{V_{i1}} = \Gamma_{L1}$$


$$\Rightarrow S_{21} = \sqrt{\frac{Z_1}{Z_2}} \left(\frac{V_{r2}}{V_{i1}} \right)$$

set $V_{in1} = 0$

$$\Rightarrow S_{22} = \frac{V_{r2}}{V_{i2}} = \Gamma_{L2}$$

$$\Rightarrow S_{12} = \sqrt{\frac{Z_2}{Z_1}} \left(\frac{V_{r1}}{V_{i2}} \right)$$

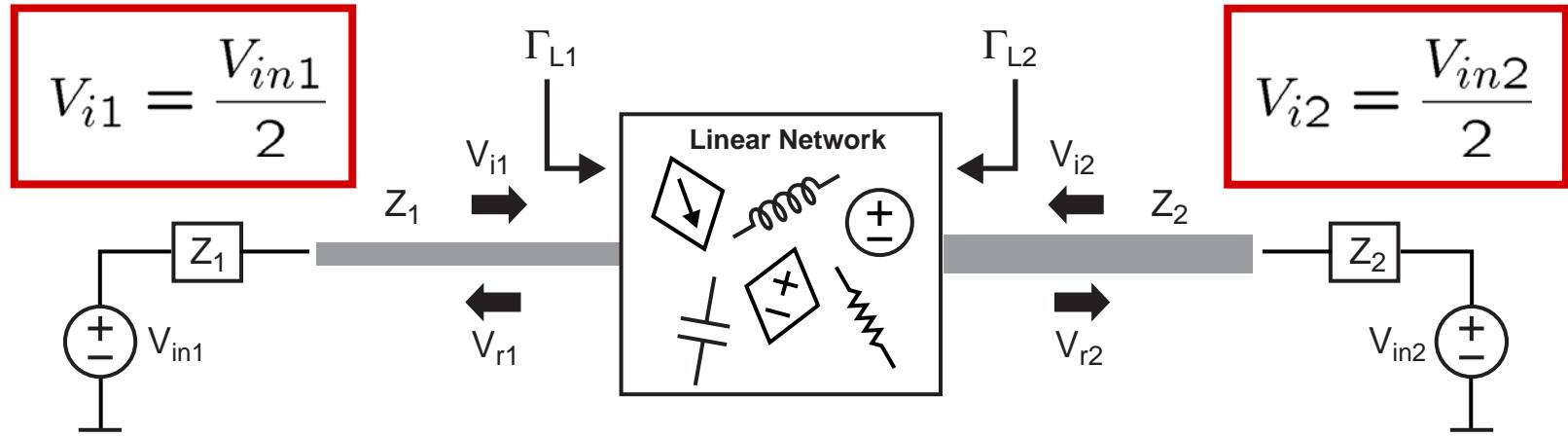Note: Alternate Form for S_{21} and S_{12}



$$\underline{\text{set } V_{in2} = 0}$$

$$\Rightarrow S_{11} = \frac{V_{r1}}{V_{i1}} = \Gamma_{L1}$$


$$\Rightarrow S_{21} = 2\sqrt{\frac{Z_1}{Z_2}} \left(\frac{V_{r2}}{V_{in1}} \right)$$

$$\underline{\text{set } V_{in1} = 0}$$

$$\Rightarrow S_{22} = \frac{V_{r2}}{V_{i2}} = \Gamma_{L2}$$


$$\Rightarrow S_{12} = 2\sqrt{\frac{Z_2}{Z_1}} \left(\frac{V_{r1}}{V_{in2}} \right)$$

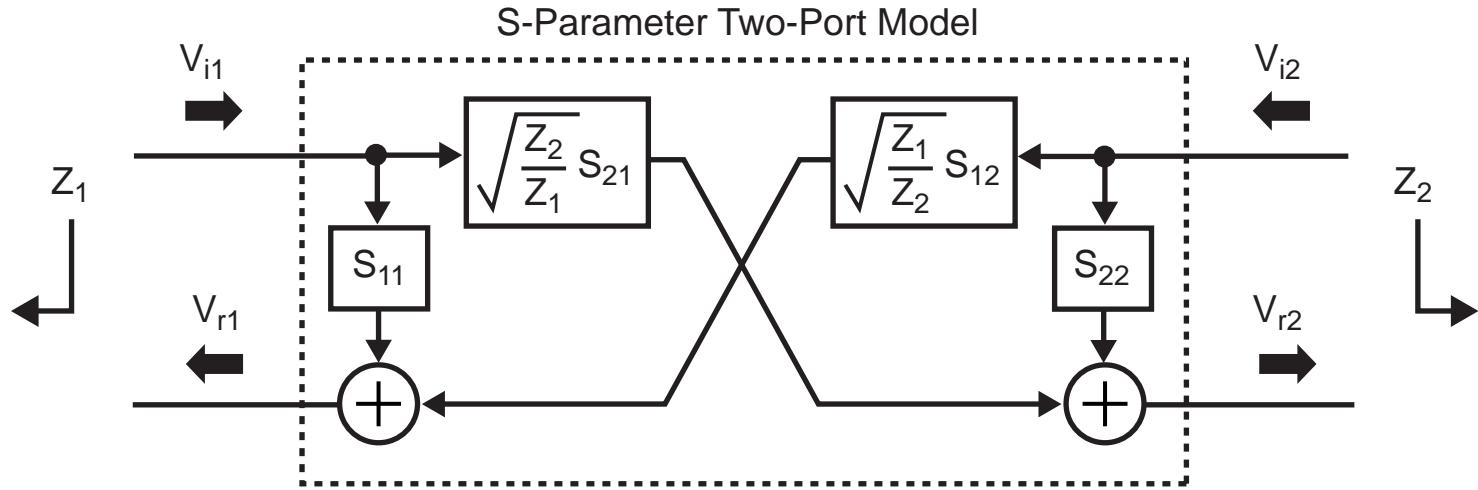Block Diagram of S-Parameter 2-Port Model



- Key issue – two-port is parameterized with respect to the left and right side load impedances (Z_1 and Z_2)
 - Need to recalculate S_{11} , S_{21} , etc. if Z_1 or Z_2 changes
 - Typical assumption is that $Z_1 = Z_2 = 50$ Ohms

S-Parameter Calculations – Example 1

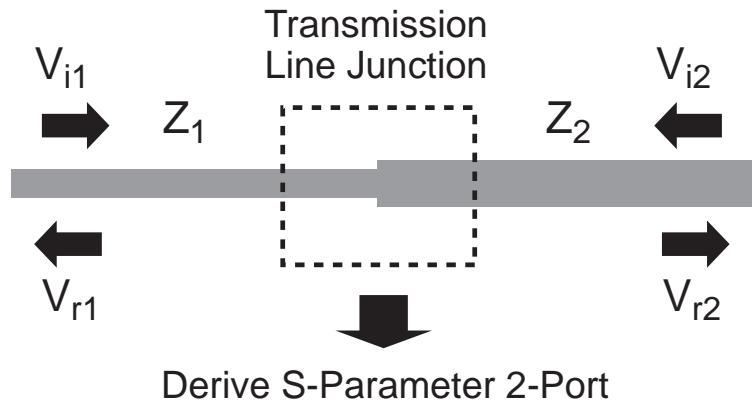

■ Set $V_{i2} = 0$

$$V_{r1} = \Gamma_1 V_{i1} = \frac{Z_2 - Z_1}{Z_2 + Z_1} V_{i1}$$

$$V_{r2} = V_{i1} + V_{r1} = (1 + \Gamma_1) V_{i1}$$

■ Set $V_{i1} = 0$

$$V_{r2} = \Gamma_2 V_{i2} = \frac{Z_1 - Z_2}{Z_1 + Z_2} V_{i2}$$

$$V_{r1} = V_{i2} + V_{r2} = (1 + \Gamma_2) V_{i2}$$


$$\Rightarrow S_{11} = \Gamma_1$$

$$\Rightarrow S_{21} = \sqrt{\frac{Z_1}{Z_2}} (1 + \Gamma_1)$$

$$\Rightarrow S_{22} = \Gamma_2$$

$$\Rightarrow S_{12} = \sqrt{\frac{Z_2}{Z_1}} (1 + \Gamma_2)$$

S-Parameter Calculations – Example 2

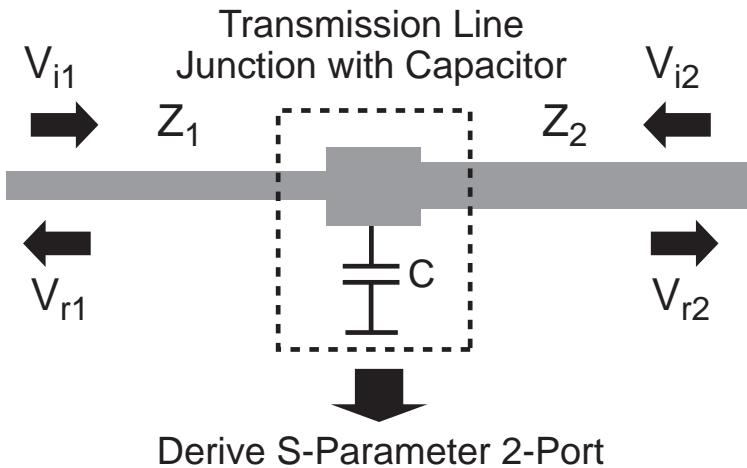

- Same as before:

$$\Rightarrow S_{11} = \Gamma_1$$

$$\Rightarrow S_{22} = \Gamma_2$$

$$\Rightarrow S_{21} = \sqrt{\frac{Z_1}{Z_2}}(1 + \Gamma_1)$$


$$\Rightarrow S_{12} = \sqrt{\frac{Z_2}{Z_1}}(1 + \Gamma_2)$$

- But now:

$$\Gamma_1 = \frac{Z_2||(1/sC) - Z_1}{Z_2||(1/sC) + Z_1}$$

$$\Gamma_2 = \frac{Z_1||(1/sC) - Z_2}{Z_1||(1/sC) + Z_2}$$

S-Parameter Calculations – Example 3

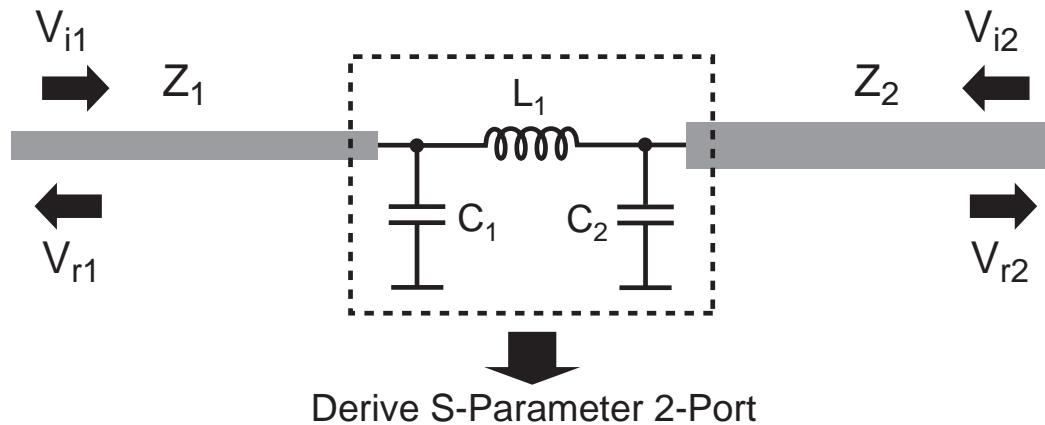

- The S-parameter calculations are now more involved
 - Network now has more than one node
- This is a homework problem

Impedance Transformers


Matching for Voltage versus Power Transfer

- Consider the voltage divider network

Given the Thevenin equivalent source with V_s and R_s , how do we deliver maximum voltage or power to the load?

- For maximum voltage transfer
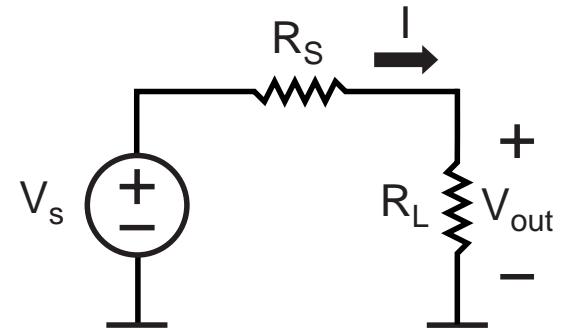
$$R_L \rightarrow \infty \Rightarrow V_{out} \rightarrow V_s$$




- For maximum power transfer

$$R_L = R_s \Rightarrow P_{out} = \frac{|V_{out}|^2}{R_L} = \frac{|V_s|^2}{4R_s}$$

Which one do we want?

Note: Maximum Power Transfer Derivation

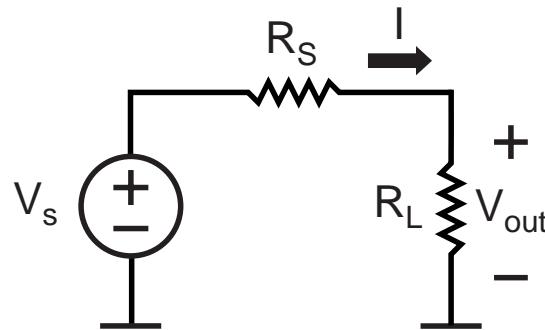

- Formulation: R_s is given, R_L is variable


$$P_{out} = I^2 R_L = \left(\frac{V_s}{R_s + R_L} \right)^2 R_L = \frac{R_L}{(R_s + R_L)^2} V_s^2$$

- Take the derivative and set it to zero

$$\frac{dP_{out}}{dR_L} = R_L(-2)(R_s + R_L)^{-3} + (R_s + R_L)^{-2} = 0$$
$$\Rightarrow 2R_L = R_s + R_L \Rightarrow R_L = R_s$$

Voltage Versus Power

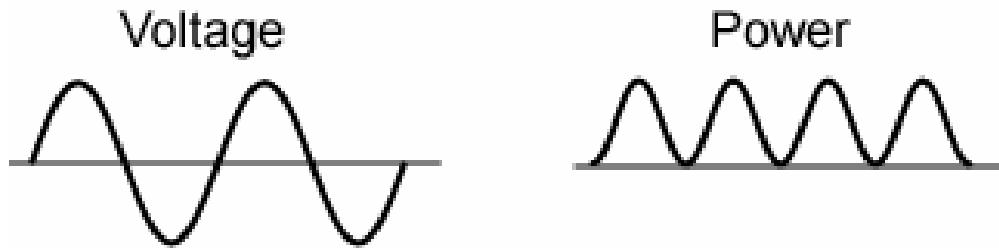- For most communication circuits, voltage (or current) is the key signal for detection
 - Phase information is important
 - Power is ambiguous with respect to phase information
 - Example:




- For high speed circuits with transmission lines, achieving maximum power transfer is important
 - Maximum power transfer coincides with having zero reflections (i.e., $\Gamma_L = 0$)

Can we ever win on both issues?

Broadband Impedance Transformers

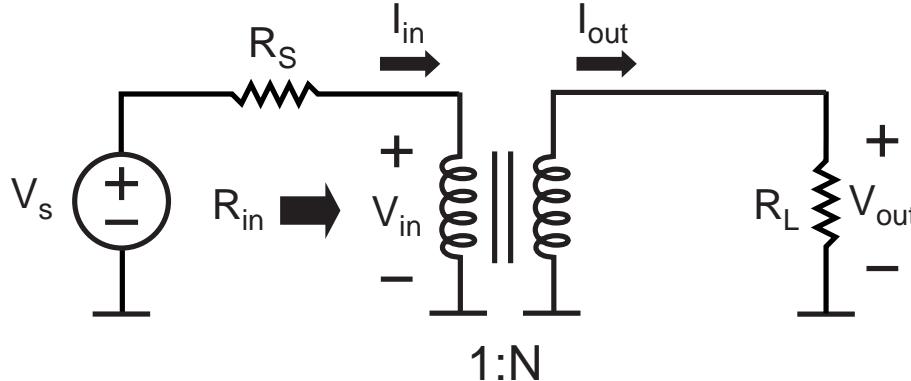- Consider placing an ideal transformer between source and load



- Transformer basics (passive, zero loss)

$$1) \quad V_{out} = NV_{in}$$

$$2) \quad \text{Power In} = \text{Power Out}$$

$$\Rightarrow \quad V_{in}I_{in} = V_{out}I_{out}$$

$$\text{From (1) and (2): } V_{in}I_{in} = NV_{in}I_{out} \Rightarrow I_{out} = \frac{I_{in}}{N}$$

- Transformer input impedance

$$R_{in} = \frac{V_{in}}{I_{in}} = \frac{V_{out}/N}{NI_{out}} = \frac{1}{N^2}R_L$$

What Value of N Maximizes Voltage Transfer?

- Derive formula for V_{out} versus V_{in} for given N value

$$\begin{aligned} V_{out} = NV_{in} &= N \frac{R_{in}}{R_s + R_{in}} V_s = N \frac{R_L/N^2}{R_s + R_L/N^2} V_s \\ &= N \frac{R_L}{R_L + N^2 R_s} V_s \end{aligned}$$

- Take the derivative and set it to zero

$$\begin{aligned} \frac{dV_{out}}{dN} &= NR_L(-1)(R_L+N^2R_S)^{-2}2NR_s+R_L(R_L+N^2R_S)^{-1} = 0 \\ \Rightarrow -2N^2R_s(R_L+N^2R_S)^{-2}+(R_L+N^2R_S)^{-1} &= 0 \\ \Rightarrow -2N^2R_s &= R_L + N^2R_S \quad \Rightarrow \boxed{N^2 = \frac{R_L}{R_s}} \end{aligned}$$

What is the Input Impedance for Max Voltage Transfer?

- We know from basic transformer theory that input impedance into transformer is

$$R_{in} = \frac{1}{N^2} R_L$$

- We just learned that, to maximize voltage transfer, we must set the transformer turns ratio to

$$N^2 = \frac{R_L}{R_s}$$


- Put them together

$$R_{in} = \frac{1}{N^2} R_L = \frac{1}{R_L/R_s} R_L = R_s \quad !!$$

So, N should be set for max power transfer into transformer to achieve the maximum voltage transfer at the load. This also ensures no reflection.

Benefit of Impedance Matching with Transformers

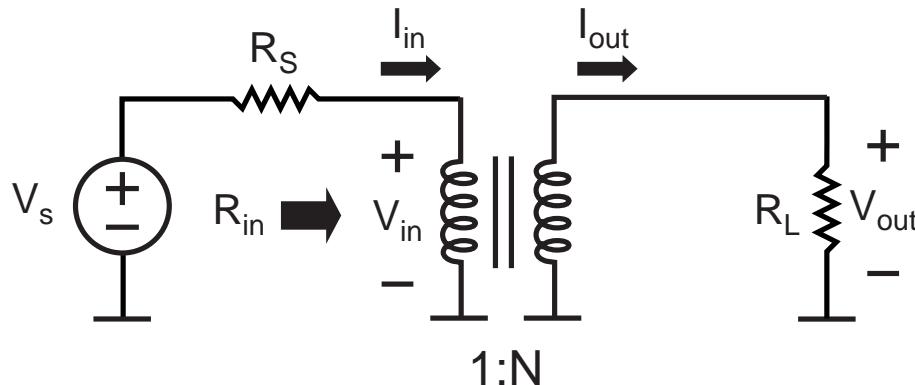- Transformers allow maximum voltage and power transfer relationship to coincide



- Turns ratio for max power/voltage transfer

$$N^2 = \frac{R_L}{R_s}$$

- Resulting voltage gain (can exceed one!)


$$V_{out} = NV_{in} = N \left(\frac{1}{2} V_s \right) = \sqrt{\frac{R_L}{R_s}} \left(\frac{1}{2} V_s \right)$$

Problems with True Transformers


- It's difficult to realize a transformer with good performance over a wide frequency range
 - Magnetic materials have limited frequency response (both low and high frequency limits)
 - Inductors have self-resonant frequencies, losses, and mediocre coupling to other inductors without magnetic material
- For wireless applications, we only need transformers that operate over a small frequency range (except UWB)
 - Can we take advantage of this?: use ‘impedance transformer’ instead of a true transformer

Consider Resonant Circuits (Chap. 3 (2nd ed.) or 4 (1st ed.) of Text)

Series Resonant Circuit

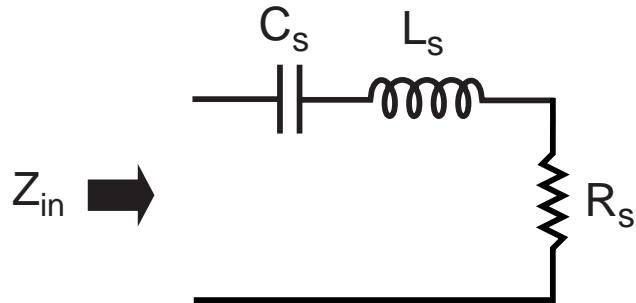

Parallel Resonant Circuit

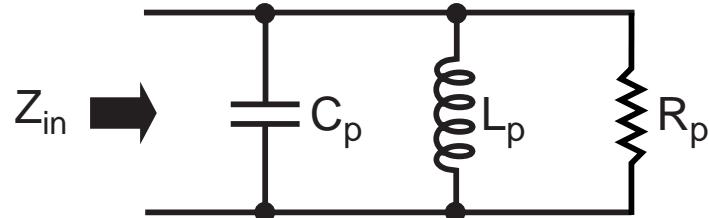

$$Z_{in} = \frac{1}{jwC_s} + jwL_s + R_s$$

$$= R_s \text{ for } w = \frac{1}{\sqrt{L_s C_s}} = w_o$$

$$Q = \frac{w_o L_s}{R_s} = \frac{1}{w_o C_s R_s}$$

$$Z_{in} = \frac{1}{jwC_p} || jwL_p || R_p$$


$$= R_p \text{ for } w = \frac{1}{\sqrt{L_p C_p}} = w_o$$

$$Q = \frac{R_p}{w_o L_p} = w_o C_p R_p$$

- Key insight: at resonance Z_{in} becomes purely real despite the presence of reactive elements

Equivalence of Series and Parallel RL Circuits


Series RL Circuit

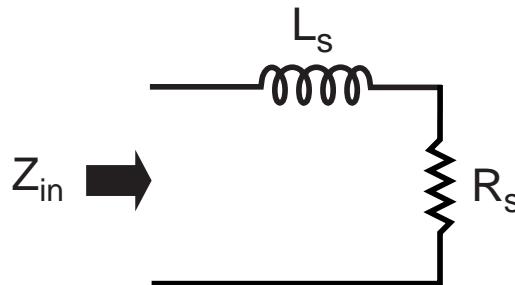

$$Q = \frac{w_o L_s}{R_s}$$

$$Z_{in} = j w_o L_s + R_s$$

Parallel RL Circuit

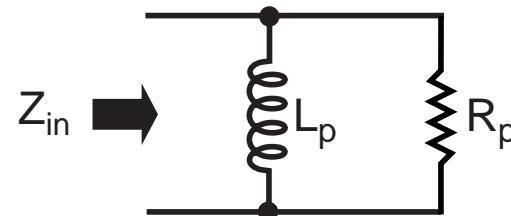

$$Q = \frac{R_p}{w_o L_p}$$

$$Z_{in} = j w_o L_p || R_p$$


- Equate real and imaginary parts of the left and right expressions (so that Z_{in} is the same for both)
 - Also equate Q values

$$R_p = R_s(Q^2 + 1) \approx R_s Q^2 \quad (\text{for } Q \gg 1)$$


$$L_p = L_s \left(\frac{Q^2 + 1}{Q^2} \right) \approx L_s \quad (\text{for } Q \gg 1)$$

Series-Parallel Equivalence Analysis

Series RL Circuit

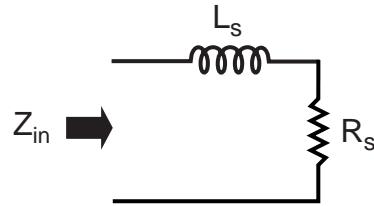

Parallel RL Circuit

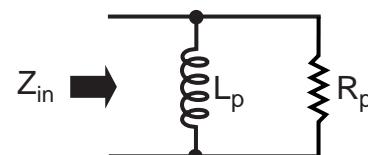


$$Z_{inp} = \frac{j\omega_o L_p R_p}{j\omega_o L_p R_p + R_p} = \frac{j\omega_o L_p R_p (-j\omega_o L_p R_p + R_p)}{\omega_o^2 L_p^2 + R_p^2}$$
$$= \frac{\omega_o^2 L_p^2 R_p + j\omega_o L_p^2 R_p^2}{\omega_o^2 L_p^2 + R_p^2}$$
$$R_s = \frac{\omega_o^2 L_p^2 R_p}{\omega_o^2 L_p^2 + R_p^2} = \frac{R_p}{1 + Q_p^2}$$

$$L_s = \frac{L_p^2 R_p^2}{\omega_o^2 L_p^2 + R_p^2} = L_p \frac{1}{\frac{\omega_o^2 L_p^2}{R_p^2} + 1} = L_p \frac{1}{1 + \frac{1}{Q_p^2}}$$

$$Q_s = \frac{\omega_o L_s}{R_s} = \frac{\omega L_p Q_p^2}{R_p} = Q_p = Q$$

Equivalence of Series and Parallel RC Circuits


Series RC Circuit

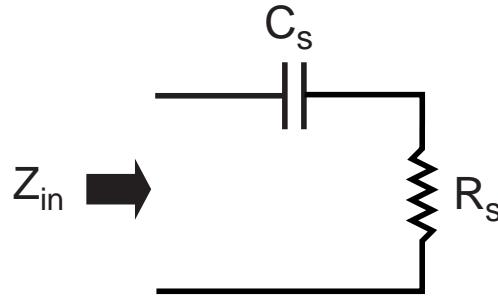

$$Q = \frac{1}{w_o C_s R_s}$$

$$Z_{in} = R_s + \frac{1}{j w_o C_s}$$

Parallel RC Circuit

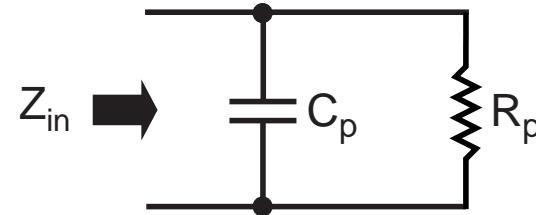

$$Q = w_o C_p R_p$$


$$Z_{in} = R_p \parallel \frac{1}{j w_o C_p}$$

- Equate real and imaginary parts of the left and right expressions (so that Z_{in} is the same for both)
 - Also equate Q values

$$R_p = R_s(Q^2 + 1) \approx R_s Q^2 \quad (\text{for } Q \gg 1)$$

$$C_p = C_s \left(\frac{Q^2}{Q^2 + 1} \right) \approx C_s \quad (\text{for } Q \gg 1)$$

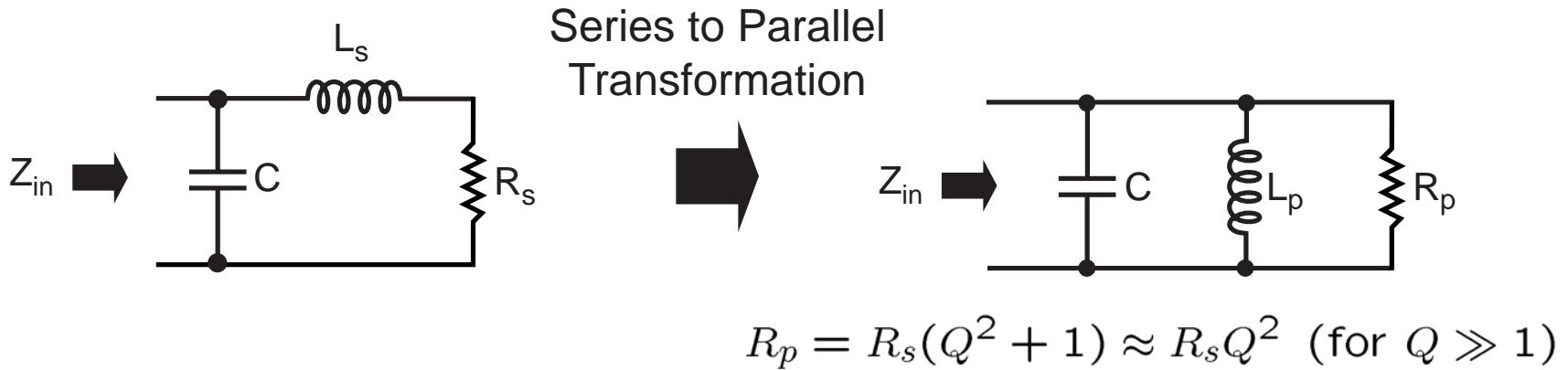A Narrowband Impedance Transformer: The L Match




- At resonance

$$L_p = L_s \left(\frac{Q^2 + 1}{Q^2} \right) \approx L_s \text{ (for } Q \gg 1\text{)}$$

$$Z_{in} = R_p = (1 + Q^2)R_s \approx Q^2R_s \text{ (purely real)}$$

- Transformer steps up impedance!

Alternate Implementation of L Match

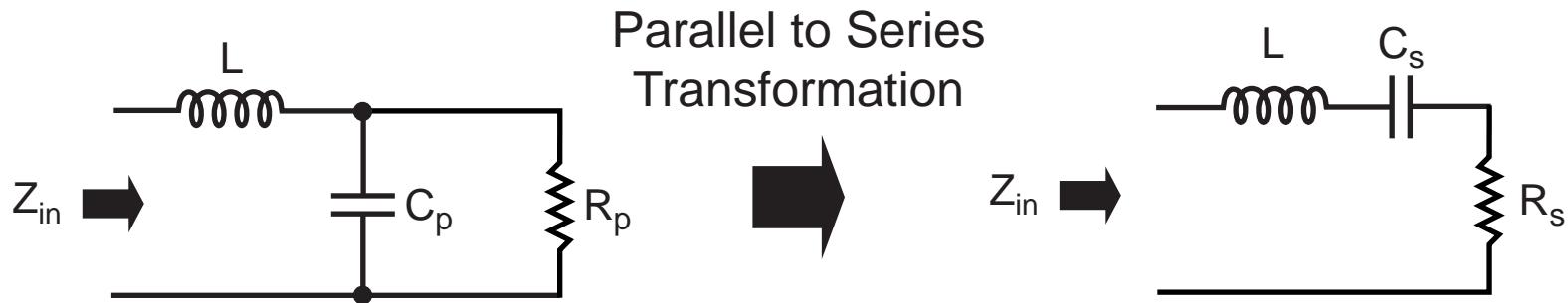

$$R_p = R_s(Q^2 + 1) \approx R_s Q^2 \quad (\text{for } Q \gg 1)$$

$$C_p = C_s \left(\frac{Q^2}{Q^2 + 1} \right) \approx C_s \quad (\text{for } Q \gg 1)$$


- At resonance

$$Z_{in} = R_s = \frac{R_p}{1 + Q^2} \approx \frac{R_p}{Q^2} \quad (\text{purely real})$$

- Transformer steps down impedance!

The π Match


- Combines two L sections

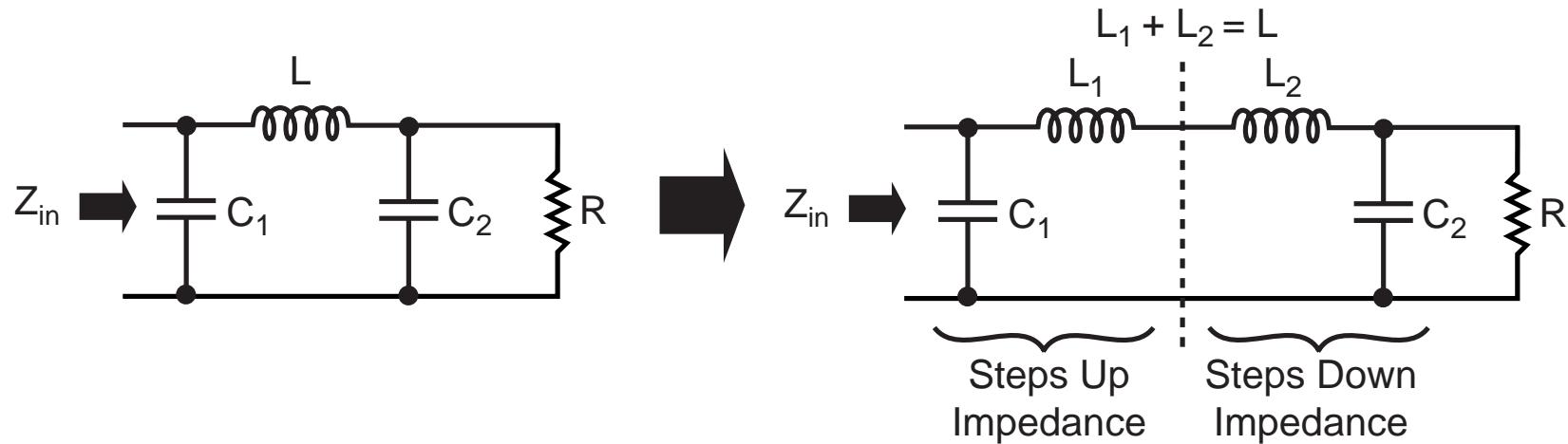

- Provides an extra degree of freedom for choosing component values for a desired transformation ratio


The T Match

- Also combines two L sections

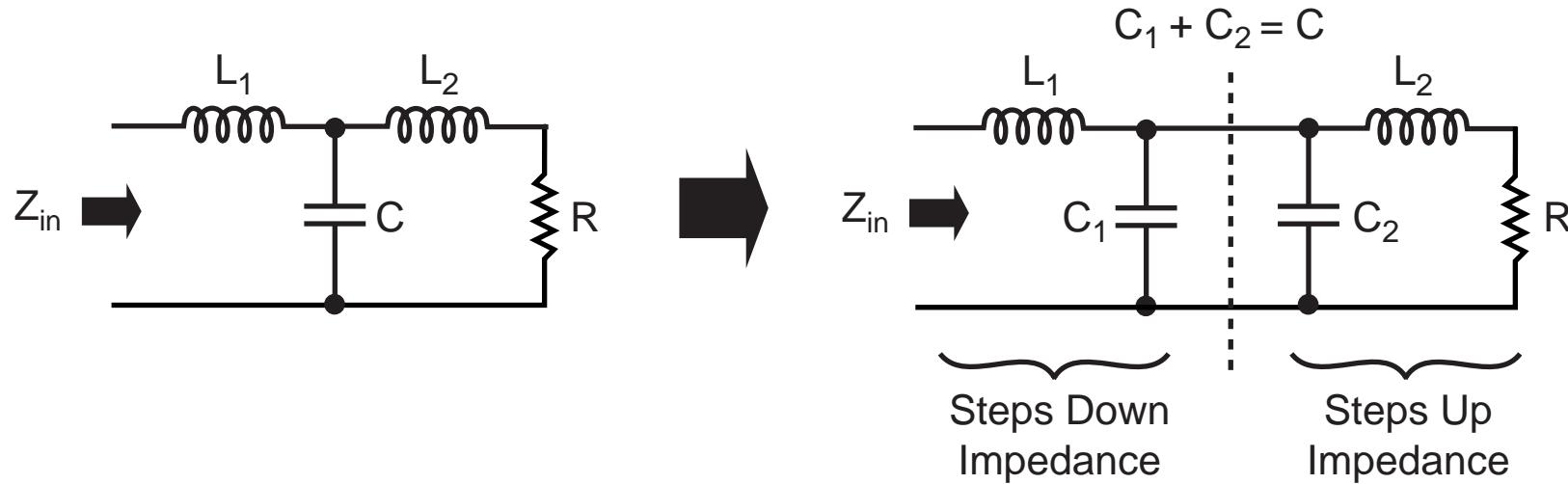

- Again, benefit is in providing an extra degree of freedom in choosing component values

Tapped Capacitor as a Transformer

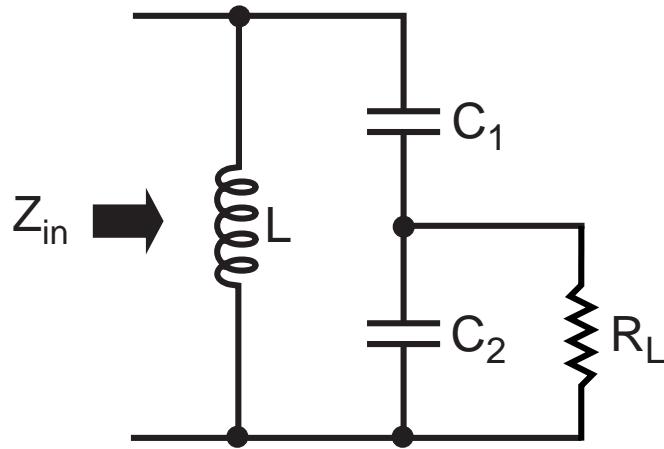

- To first order:

$$\frac{R_{in}}{R_L} \approx \left(\frac{C_1 + C_2}{C_1} \right)^2$$

- Useful in VCO design
- See Chap. 3 (2nd ed.) or 4 (1st ed.) of Text