



6.776

High Speed Communication Circuits and Systems
Lecture 5
Generalized Reflection Coefficient, Smith Chart

Massachusetts Institute of Technology
February 15, 2005

Copyright © 2005 by Hae-Seung Lee and Michael H.
Perrott

Reflection Coefficient

- We defined, at the load $\Gamma_L = \frac{V_r}{V_i}$
- Load and characteristic impedances were related

$$Z_o \left(\frac{1 + \Gamma_L}{1 - \Gamma_L} \right) = Z_L$$

- Alternately

$$\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o}$$

Can we find reflection coefficient at locations other than the load location?: Generalized reflection coefficient

Voltage and Current Waveforms


- In Lecture 3, we found that in sinusoidal steady-state in a transmission line,

$$V(z, t) = V_o e^{j(wt \pm kz)}$$

where the – sign is for the wave traveling in the +z direction, and the + sign is for the wave traveling in the –z direction.


- Thus, the incident wave has the voltage $V_i(z, t) = V_+ e^{j(wt+kz)}$
- And the reflected wave $V_r(z, t) = V_- e^{j(wt-kz)}$
- Similarly for currents: $I_i(z, t) = I_+ e^{j(wt+kz)}$
 $I_r(z, t) = I_- e^{j(wt-kz)}$

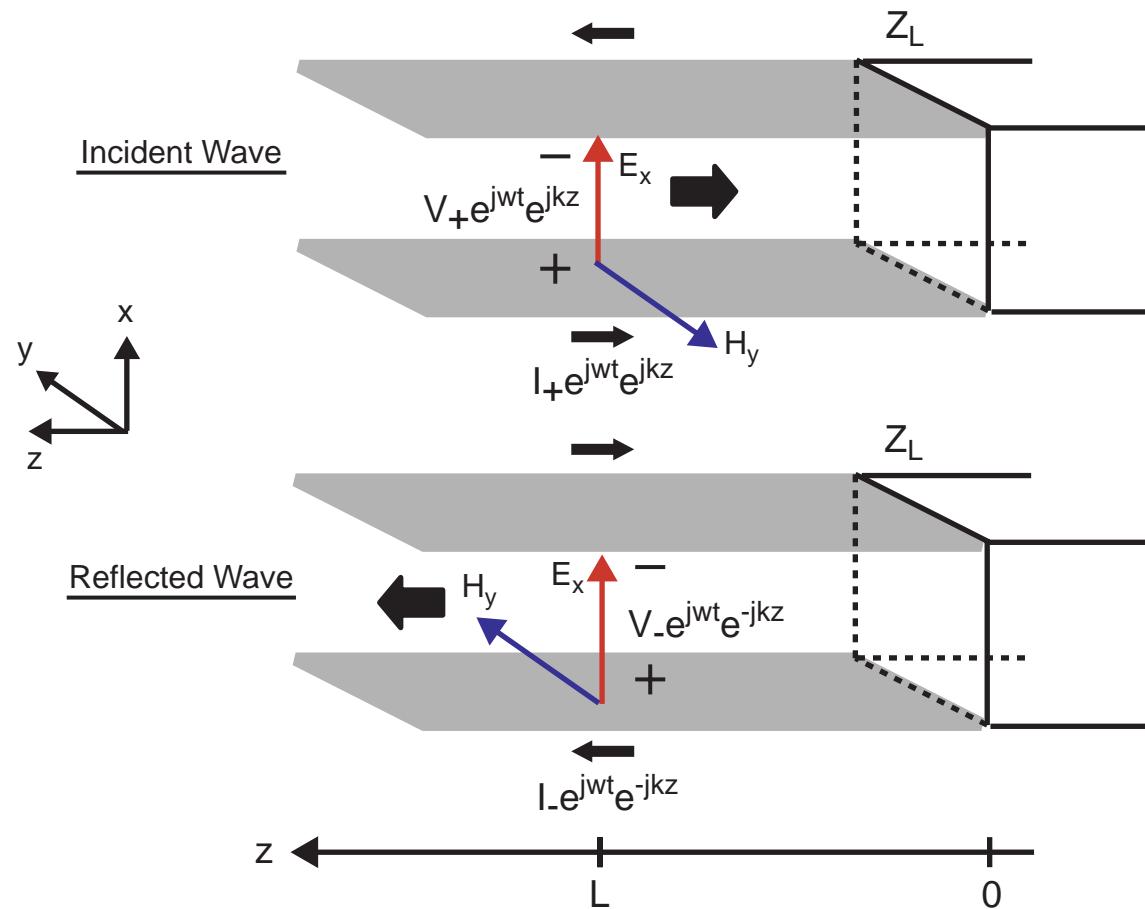Determine Voltage and Current At Different Positions



- Incident and reflected waves must be added together

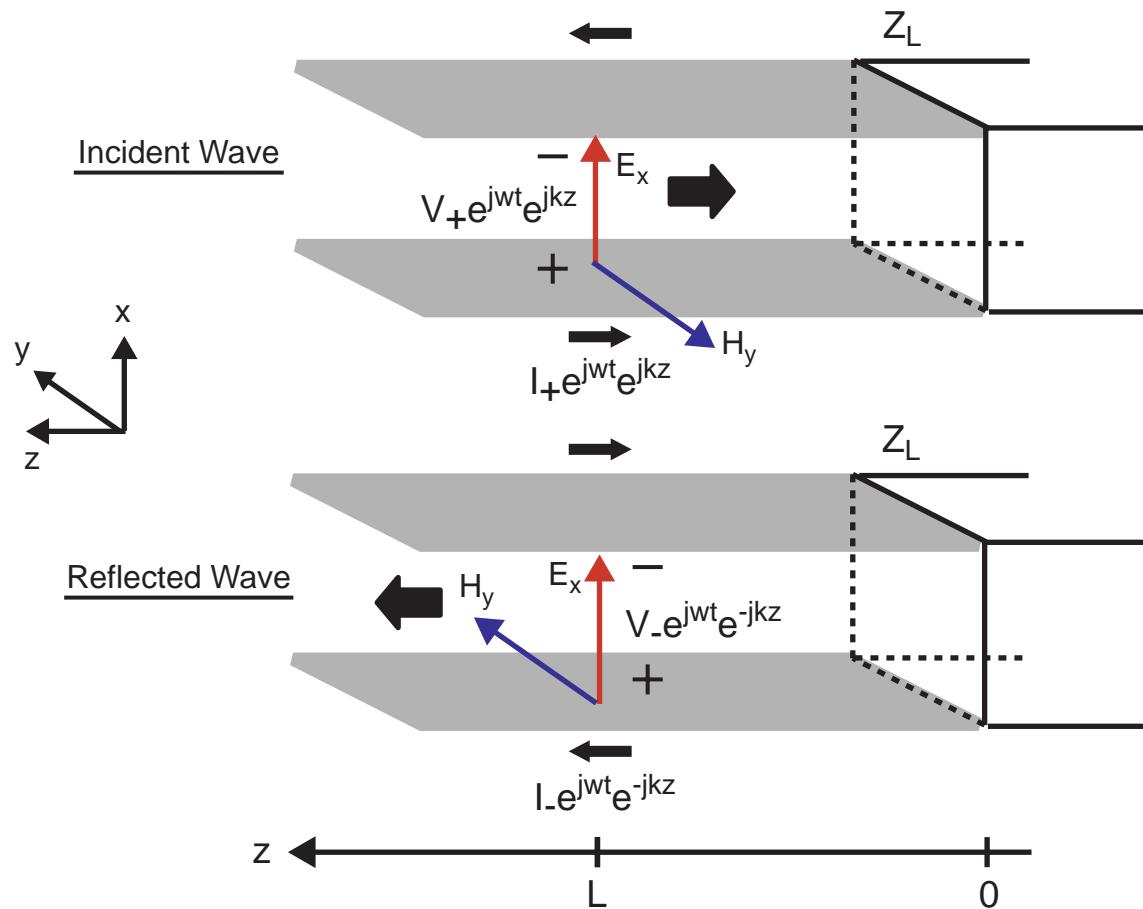Determine Voltage and Current At Different Positions



$$V(z, t) = V_+ e^{j\omega t} e^{jkz} + V_- e^{j\omega t} e^{-jkz}$$
$$I(z, t) = I_+ e^{j\omega t} e^{jkz} - I_- e^{j\omega t} e^{-jkz}$$

Define Generalized Reflection Coefficient

Recall: $\Gamma_L = \frac{V_r}{V_i}$

Define Generalized Reflection Coefficient: $\Gamma(z) = \frac{V_r(z, t)}{V_i(z, t)}$

$$\Gamma(z) = \frac{V_r(z, t)}{V_i(z, t)} = \frac{V_- e^{j\omega t} e^{-jkz}}{V_+ - e^{j\omega t} e^{jkz}} = \frac{V_-}{V_+} e^{-2jkz}$$

$$\Rightarrow \Gamma(z) = \Gamma_L e^{-2jkz}$$

Since $\frac{V_i(z, t)}{I_i(z, t)} = \frac{V_r(z, t)}{I_r(z, t)} = Z_o$

$$\Gamma(z) = \frac{I_r(z, t)}{I_i(z, t)}$$

Generalized Reflection Coefficient Cont'd

$$V(z, t) = V_+ e^{j\omega t} e^{jkz} + V_- e^{j\omega t} e^{-jkz}$$

$$I(z, t) = I_+ e^{j\omega t} e^{jkz} - I_- e^{j\omega t} e^{-jkz}$$

$$V(z, t) = V_+ e^{j\omega t} e^{jkz} \left(1 + \frac{V_-}{V_+} e^{-2jkz} \right)$$



$$V(z, t) = V_+ e^{j\omega t} e^{jkz} \left(1 + \Gamma_L e^{-2jkz} \right)$$



$$V(z, t) = V_+ e^{j\omega t} e^{jkz} (1 + \Gamma(z))$$

Similarly: $I(z, t) = I_+ e^{j\omega t} e^{jkz} (1 - \Gamma(z))$

A Closer Look at $\Gamma(z)$

- Recall Γ_L is


$$\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o}$$

Note: $|\Gamma_L| \leq 1$

for $Re\{Z_L/Z_o\} \geq 0$

- We can view $\Gamma(z)$ as a complex number that rotates clockwise as z (distance from the load) increases

$$\Gamma(z) = \Gamma_L e^{-2jkz}$$

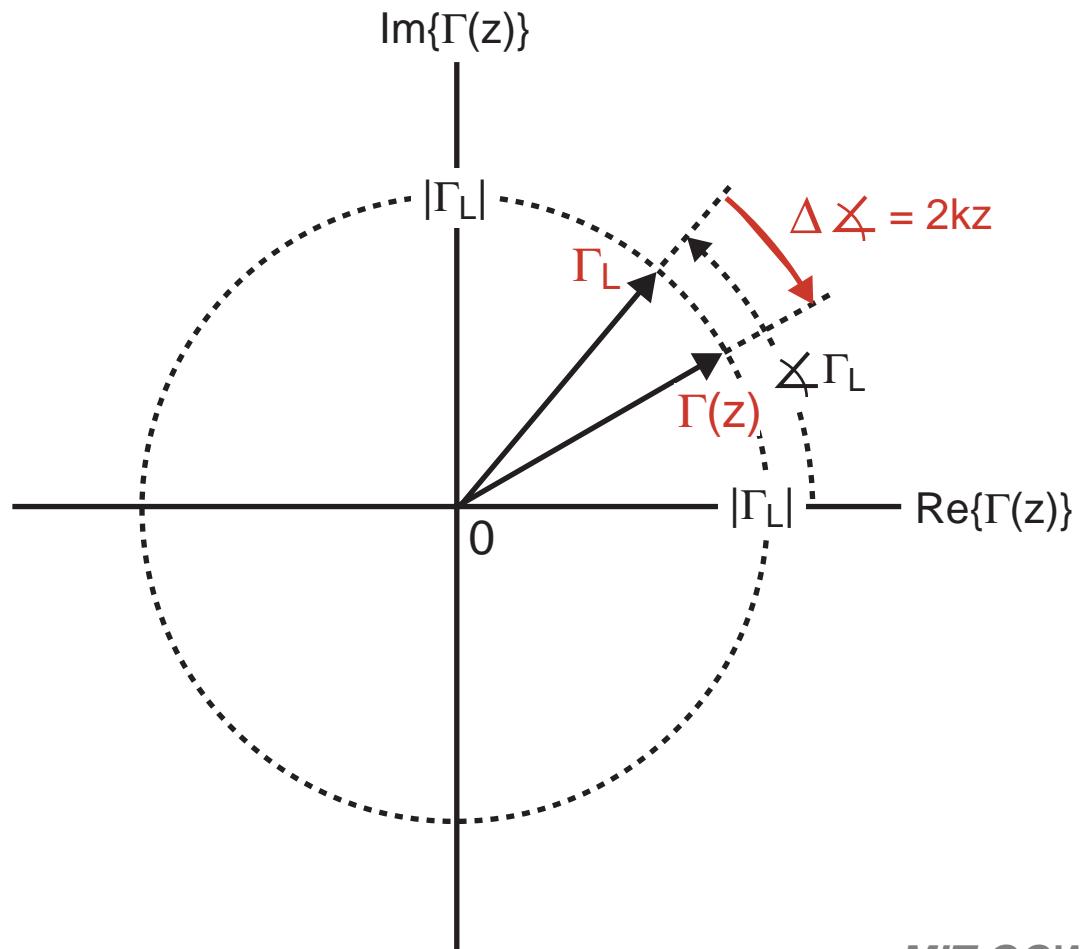

Calculate $|V_{max}|$ and $|V_{min}|$ Across The Transmission Line

- We found that

$$V(z, t) = V_+ e^{j\omega t} e^{jkz} (1 + \Gamma(z))$$


- So that the max and min of $V(z,t)$ are calculated as

$$\Rightarrow V_{max} = \max |V(z, t)| = |V_+| \max |1 + \Gamma(z)|$$

$$\Rightarrow V_{min} = \min |V(z, t)| = |V_+| \min |1 + \Gamma(z)|$$


- We can calculate this geometrically!

A Geometric View of $|1 + \Gamma(z)|$

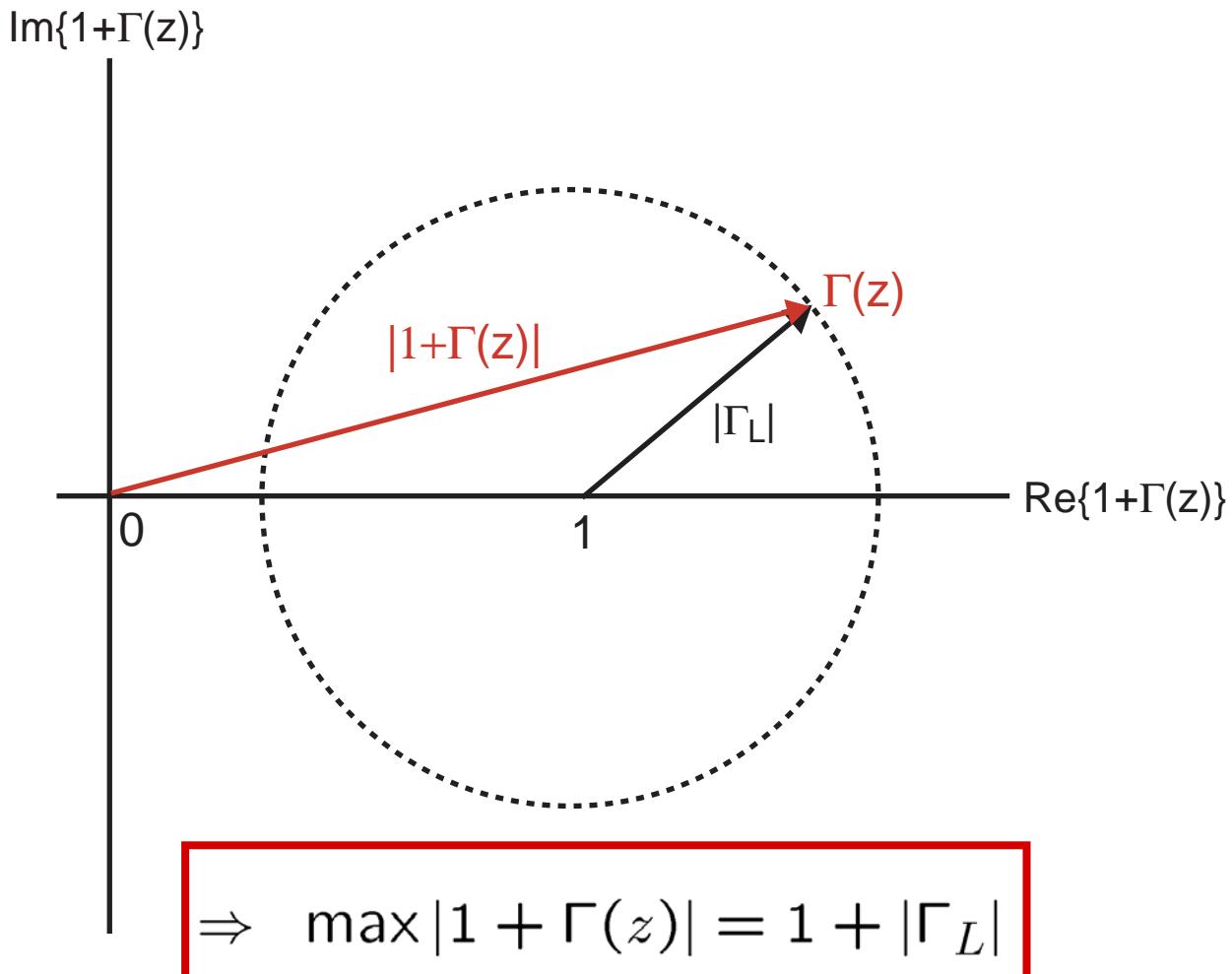

Reflections Cause Amplitude to Vary Across Line

- **Equation:** $V(z, t) = V_+ e^{j\omega t} e^{jkz} |1 + \Gamma(z)| e^{j\angle(1+\Gamma(z))}$
- **Graphical representation:**

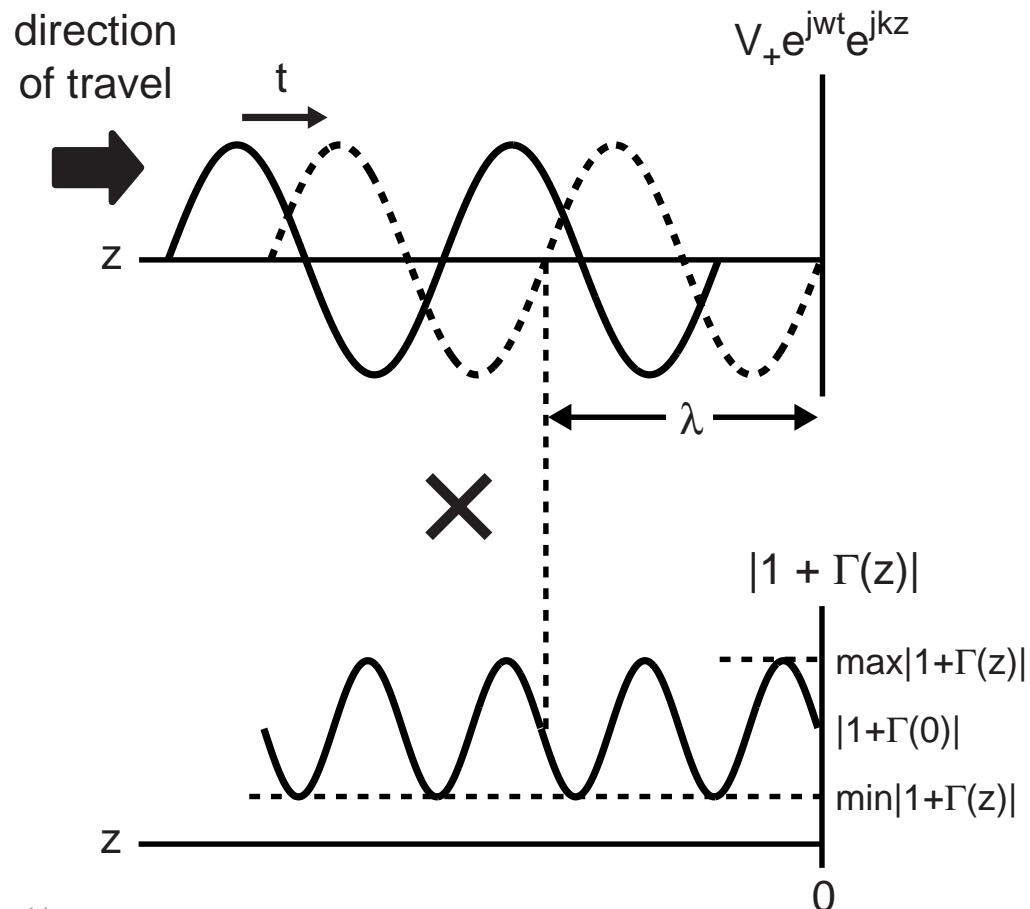

Voltage Standing Wave Ratio (VSWR)

- **Definition**

$$\text{VSWR} = \frac{V_{max}}{V_{min}} = \frac{|V_+|(1 + |\Gamma_L|)}{|V_+|(1 - |\Gamma_L|)} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$

- **For passive load (and line)**

$$|\Gamma_L| \leq 1 \Rightarrow 1 \leq \text{VSWR} \leq \infty$$

$$|\Gamma_L| = 0 \quad \quad \quad |\Gamma_L| = 1$$

- **We can infer the magnitude of the reflection coefficient based on VSWR**

$$|\Gamma_L| = \frac{\text{VSWR} - 1}{\text{VSWR} + 1}$$

Reflections Influence Impedance Across The Line

- From Slide 7

$$V(z, t) = V_+ e^{j\omega t} e^{jkz} (1 + \Gamma(z))$$

$$I(z, t) = I_+ e^{j\omega t} e^{jkz} (1 - \Gamma(z))$$

$$\Rightarrow Z(z, t) = \frac{V_+ (1 + \Gamma(z))}{I_+ (1 - \Gamma(z))} = Z_o \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$

- Note: not a function of time! (only of distance from load)

- Alternatively

$$Z(z) = Z_o \frac{1 + \Gamma_L e^{-2jkz}}{1 - \Gamma_L e^{-2jkz}}$$

- From Lecture 3: $\lambda = \frac{T}{\sqrt{\mu\epsilon}} = \frac{wT}{w\sqrt{\mu\epsilon}} = \frac{2\pi f T}{k} = \frac{2\pi}{k}$

Impedance as a Function of Location

We can now express $Z(z)$ as


$$Z(z) = Z_o \frac{1 + \Gamma_L e^{-j(4\pi/\lambda)z}}{1 - \Gamma_L e^{-j(4\pi/\lambda)z}}$$

Also

$$\Gamma(z) = \Gamma_L e^{-j(4\pi/\lambda)z}$$

Note: $Z(z)$ and $\Gamma(z)$ are periodic in z with a period of $\lambda/2$

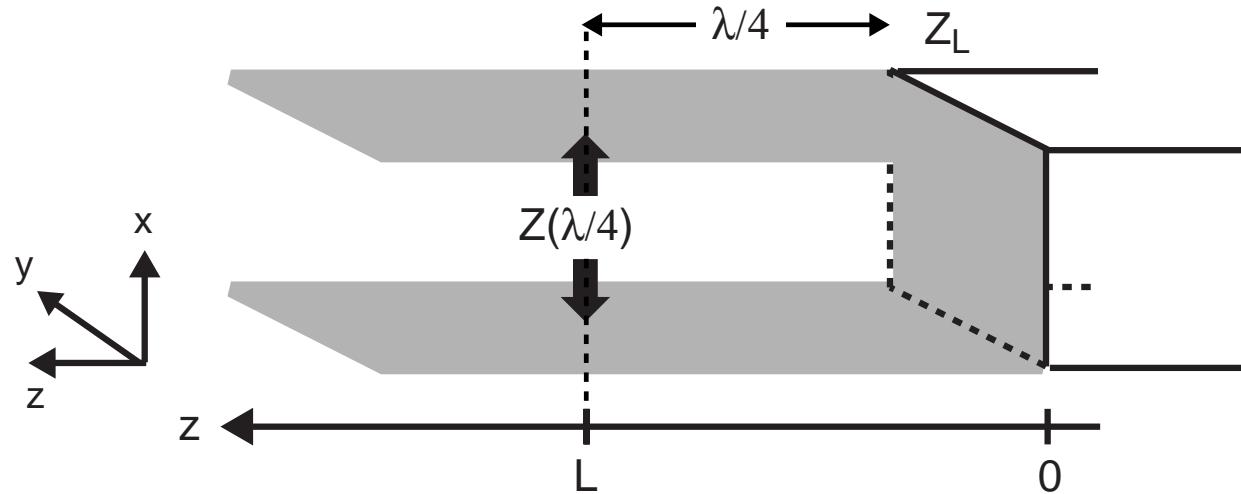Example: $Z(\lambda/4)$ with Shorted Load



- Calculate reflection coefficient

$$\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o} = \frac{0 - Z_o}{0 + Z_o} = -1$$

- Calculate generalized reflection coefficient

$$\Gamma(\lambda/4) = \Gamma_L e^{-j(4\pi/\lambda)(\lambda/4)} = \Gamma_L e^{-j\pi} = -\Gamma_L = 1$$

- Calculate impedance

$$Z(\lambda/4) = Z_o \frac{1 + \Gamma(z)}{1 - \Gamma(z)} = \infty !$$

Generalize Relationship Between $Z(\lambda/4)$ and $Z(0)$

- General formulation

$$Z(z) = Z_o \frac{1 + \Gamma_L e^{-j(4\pi/\lambda)z}}{1 - \Gamma_L e^{-j(4\pi/\lambda)z}}$$

- At load ($z=0$)

$$Z_L = Z(0) = Z_o \frac{1 + \Gamma_L}{1 - \Gamma_L}$$

- At quarter wavelength away ($z = \lambda/4$)

$$Z(\lambda/4) = Z_o \frac{1 - \Gamma_L}{1 + \Gamma_L} = \frac{Z_o^2}{Z_L}$$

- Impedance is inverted (Z_o is real)

- Shorts turn into opens
 - Capacitors turn into inductors

Now Look At $Z(\Delta)$ (Impedance Close to Load)

- Impedance formula (Δ very small)

$$Z(\Delta) = Z_o \frac{1 + \Gamma_L e^{-2jk\Delta}}{1 - \Gamma_L e^{-2jk\Delta}}$$

- A useful approximation: $e^{-jx} \approx 1 - jx$ for $x \ll 1$


$$\Rightarrow e^{-2jk\Delta} \approx 1 - 2jk\Delta$$

- Recall from Lecture 2: $k = w\sqrt{LC}$, $Z_o = \sqrt{\frac{L}{C}}$

- Overall approximation:

$$Z(\Delta) \approx \left(\sqrt{\frac{L}{C}} \right) \frac{1 + \Gamma_L (1 - 2jw\sqrt{LC}\Delta)}{1 - \Gamma_L (1 - 2jw\sqrt{LC}\Delta)}$$

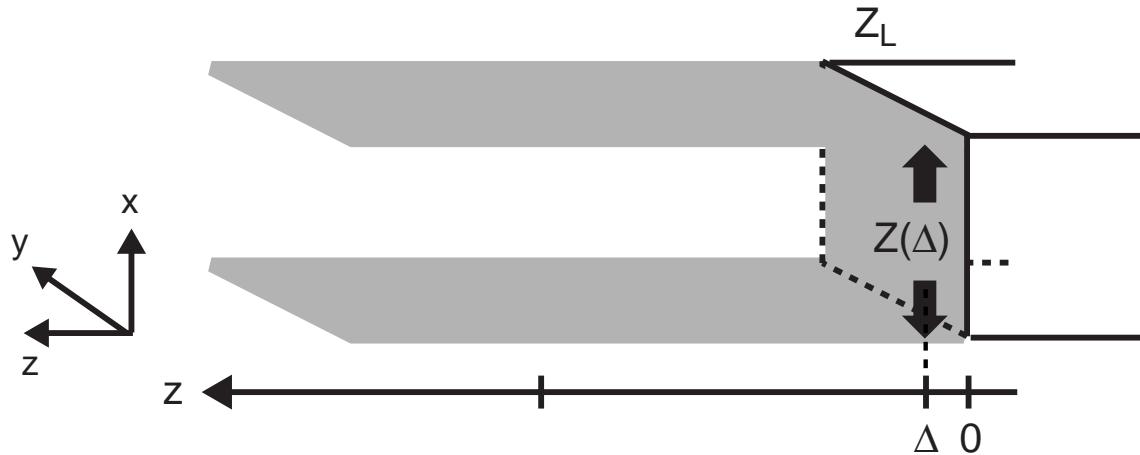Example: Look At $Z(\Delta)$ With Load Shorted




$$Z(\Delta) \approx \left(\sqrt{\frac{L}{C}} \right) \frac{1 + \Gamma_L (1 - 2jw\sqrt{LC}\Delta)}{1 - \Gamma_L (1 - 2jw\sqrt{LC}\Delta)}$$

- **Reflection coefficient:** $\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o} = \frac{0 - Z_o}{0 + Z_o} = -1$
- **Resulting impedance looks inductive!**

$$Z(\Delta) \approx \left(\sqrt{\frac{L}{C}} \right) \frac{1 - (1 - 2jw\sqrt{LC}\Delta)}{1 + (1 - 2jw\sqrt{LC}\Delta)} \approx jwL\Delta$$

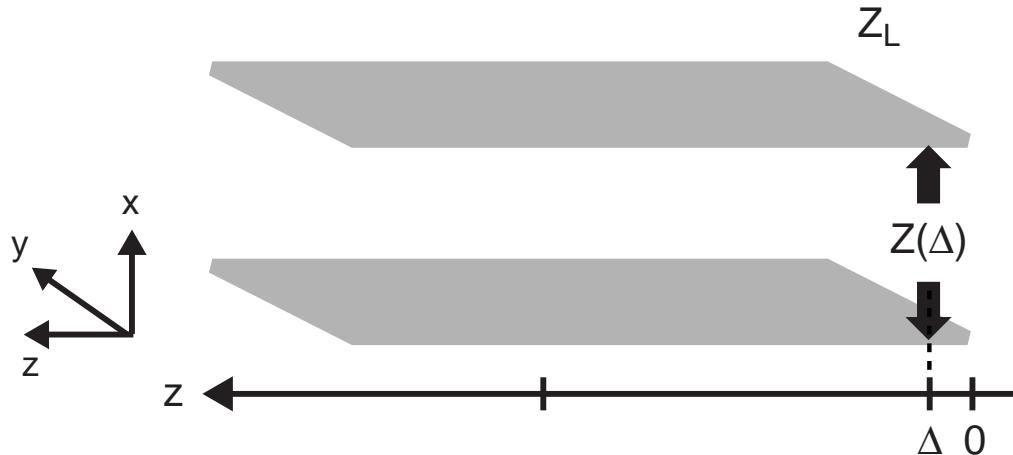Example: Look At $Z(\Delta)$ With Load Open




$$Z(\Delta) \approx \left(\sqrt{\frac{L}{C}} \right) \frac{1 + \Gamma_L (1 - 2jw\sqrt{LC}\Delta)}{1 - \Gamma_L (1 - 2jw\sqrt{LC}\Delta)}$$

- **Reflection coefficient:** $\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o} = \frac{\infty - Z_o}{\infty + Z_o} = 1$
- **Resulting impedance looks capacitive!**

$$Z(\Delta) \approx \left(\sqrt{\frac{L}{C}} \right) \frac{1 + (1 - 2jw\sqrt{LC}\Delta)}{1 - (1 - 2jw\sqrt{LC}\Delta)} \approx \frac{1}{jwC\Delta}$$

Compare to an Ideal LC Tank Circuit

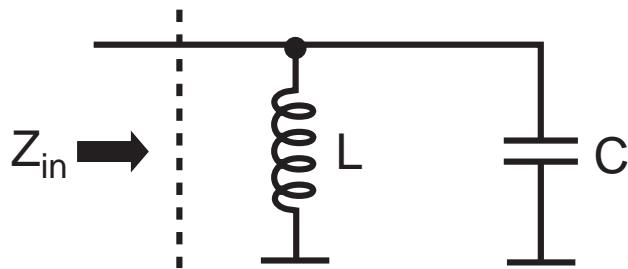

$$Z_{in}(w) = \frac{1}{jwC} || jwL = \frac{jwL}{1 - w^2LC}$$

- Calculate input impedance about resonance


Consider $w = w_o + \Delta w$, where $w_o = \frac{1}{\sqrt{LC}}$

$$\begin{aligned} Z_{in}(\Delta w) &= \frac{j(w_o + \Delta w)L}{1 - (w_o + \Delta w)^2LC} \\ &= \frac{j(w_o + \Delta w)L}{\underline{1 - w_o^2LC} - 2\Delta w(w_oLC) - \underline{\Delta w^2LC}} \\ &\quad = 0 \end{aligned}$$

negligible

$$\Rightarrow Z_{in}(\Delta w) \approx \frac{j(w_o + \Delta w)L}{-2\Delta w(w_oLC)} \approx \frac{jw_oL}{-2\Delta w(w_oLC)} = \boxed{-\frac{j}{2}\sqrt{\frac{L}{C}}\left(\frac{w_o}{\Delta w}\right)}$$

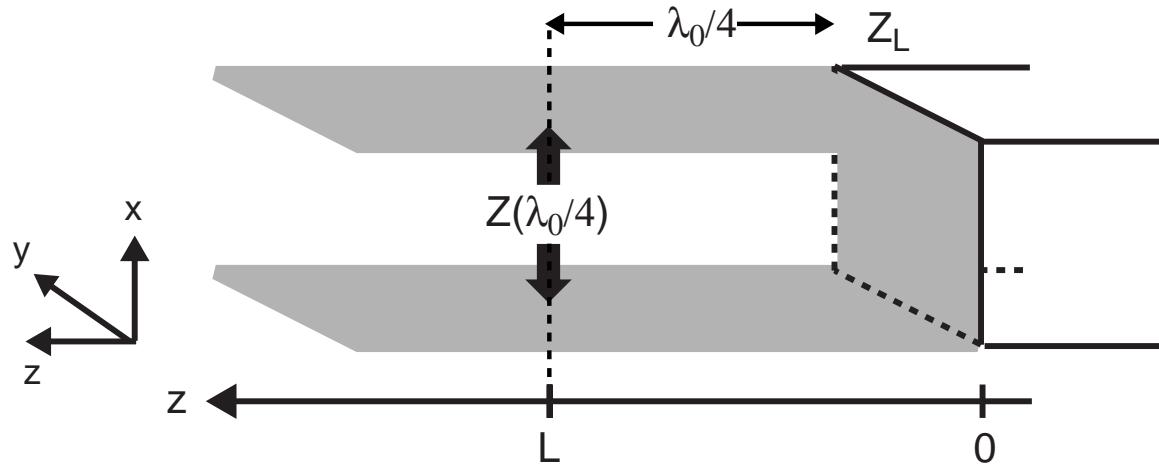Transmission Line Version: $Z(\lambda_0/4)$ with Shorted Load



- As previously calculated


$$\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o} = \frac{0 - Z_o}{0 + Z_o} = -1$$

- Impedance calculation

$$Z(z) = Z_o \frac{1 + \Gamma(z)}{1 - \Gamma(z)}, \text{ where } \Gamma(z) = \Gamma_L e^{-j(4\pi/\lambda)z}$$

- Relate λ to frequency $\lambda = \frac{1}{f \sqrt{\mu\epsilon}} = \frac{1}{(f_o + \Delta f) \sqrt{\mu\epsilon}}$

Calculate $Z(\Delta f)$ – Step 1

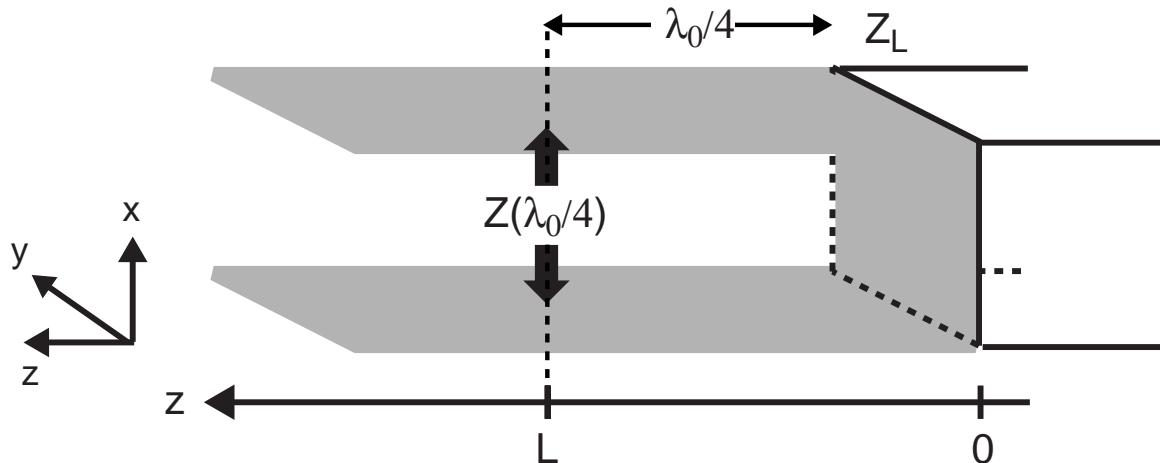

- Wavelength as a function of Δf


$$\lambda = \frac{1}{(f_o + \Delta f)\sqrt{\mu\epsilon}} = \frac{1}{f_o\sqrt{\mu\epsilon}(1 + \Delta f/f_o)} = \frac{\lambda_o}{1 + \Delta f/f_o}$$

- Generalized reflection coefficient

$$\Gamma(\lambda_o/4) = \Gamma_L e^{-j(4\pi/\lambda)\lambda_o/4} = \Gamma_L e^{-j\pi\lambda_o/\lambda} = \Gamma_L e^{-j\pi\lambda_o/\lambda}$$

$$\Rightarrow \Gamma(\lambda_o/4) = \Gamma_L e^{-j\pi(1+\Delta f/f_o)} = -\Gamma_L e^{-j\pi\Delta f/f_o}$$

Calculate $Z(\Delta f)$ – Step 2

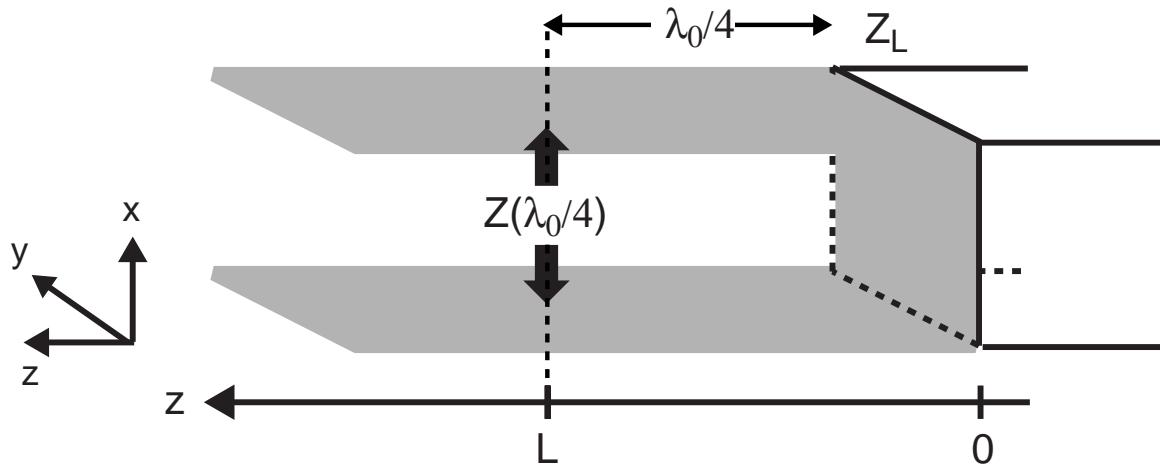

■ Impedance calculation

$$Z(\lambda_0/4) = Z_o \frac{1 - \Gamma_L e^{-j\pi\Delta f/f_o}}{1 + \Gamma_L e^{-j\pi\Delta f/f_o}} = Z_o \frac{1 + e^{-j\pi\Delta f/f_o}}{1 - e^{-j\pi\Delta f/f_o}}$$

■ Recall $e^{-j\pi\Delta f/f_o} \approx 1 - j\pi\Delta f/f_o$

$$\Rightarrow Z(z) \approx Z_o \frac{1 + 1 - j\pi\Delta f/f_o}{1 - 1 + j\pi\Delta f/f_o} \approx Z_o \frac{2}{j\pi\Delta f/f_o} = -j \frac{2}{\pi} \sqrt{\frac{L}{C}} \left(\frac{w_o}{\Delta w} \right)$$

– Looks like LC tank circuit (but more than one mode)!

Smith Chart

- Define normalized load impedance

$$Z_n = \frac{Z_L}{Z_o}$$

- Relation between Z_n and Γ_L


$$Z_n = \frac{1 + \Gamma_L}{1 - \Gamma_L}$$

- Consider working in coordinate system based on Γ
- Key relationship between Z_n and Γ

$$Re\{Z_n\} + j Im\{Z_n\} = \frac{1 + Re\{\Gamma_L\} + j Im\{\Gamma_L\}}{1 - (Re\{\Gamma_L\} + j Im\{\Gamma_L\})}$$


- Equate real and imaginary parts to get Smith Chart

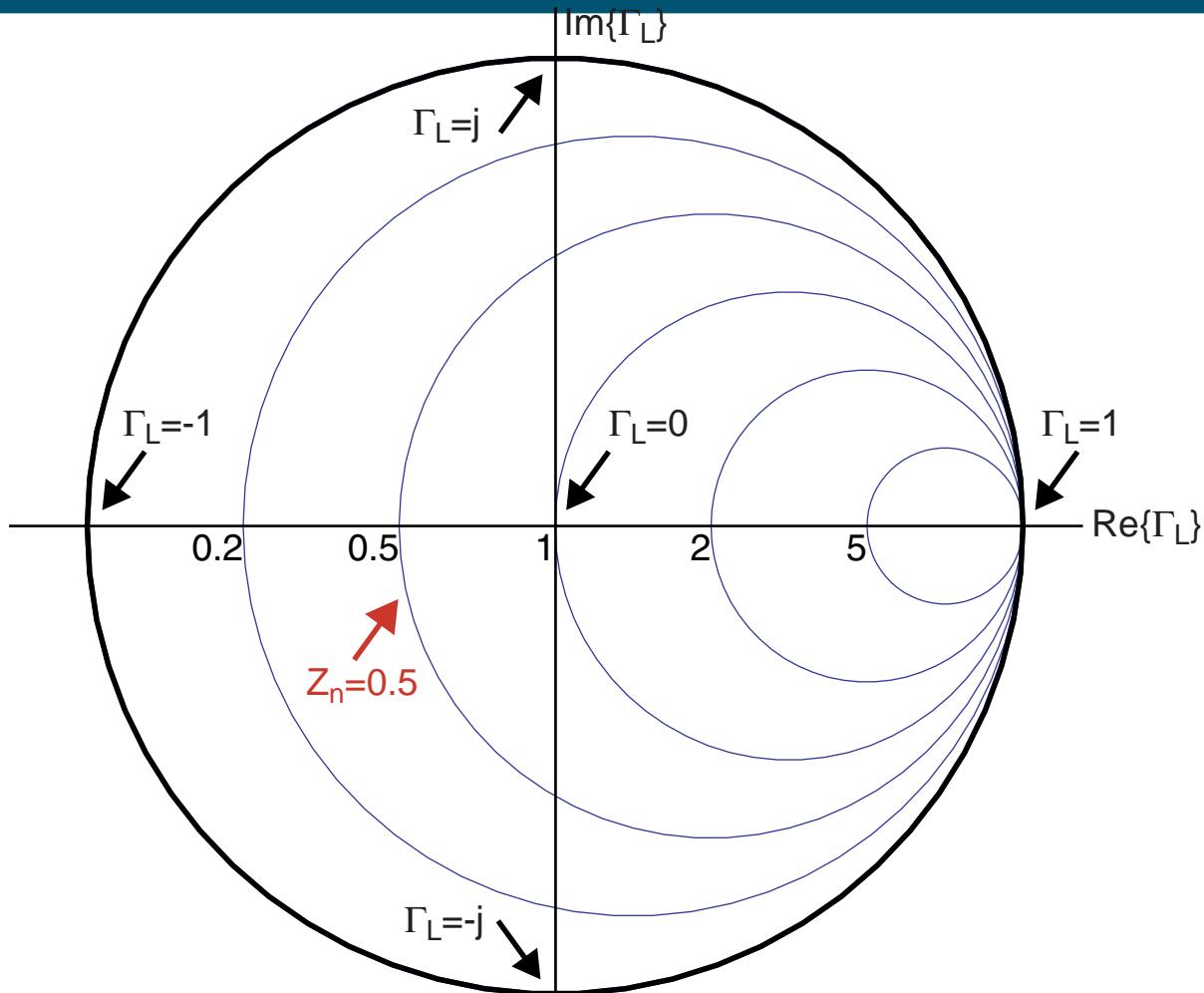Real Impedance in Γ Coordinates (Equate Real Parts)



$$\left(\text{Re}\{\Gamma_L\} - \frac{\text{Re}\{Z_n\}}{1 + \text{Re}\{Z_n\}} \right)^2 + (\text{Im}\{\Gamma_L\})^2 = \left(\frac{1}{1 + \text{Re}\{Z_n\}} \right)^2$$

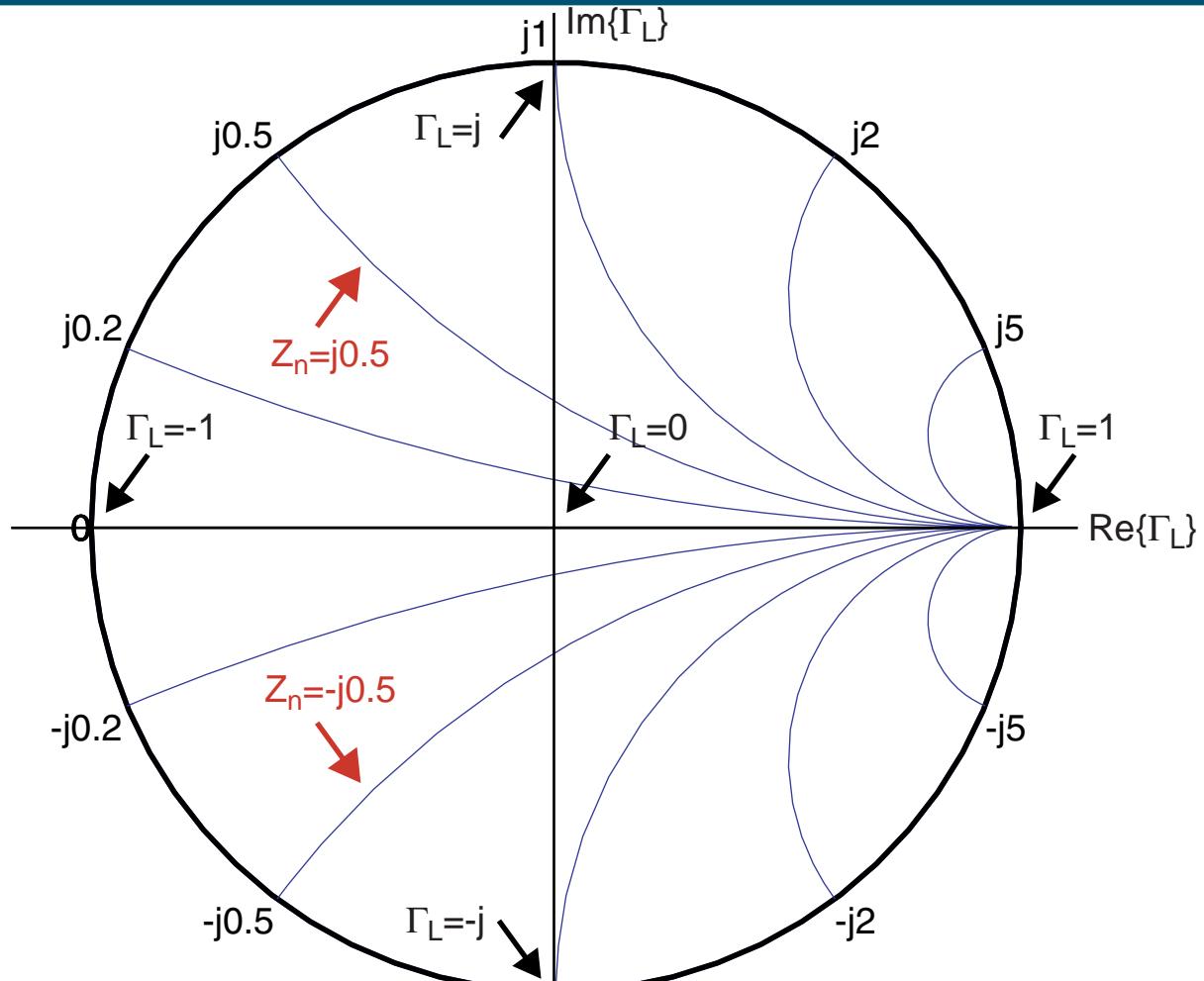Imag. Impedance in Γ Coordinates (Equate Imag. Parts)



$$(Re\{\Gamma_L\} - 1)^2 + \left(Im\{\Gamma_L\} - \frac{1}{Im\{Z_n\}} \right)^2 = \left(\frac{1}{Im\{Z_n\}} \right)^2$$

What Happens When We Invert the Impedance?

- **Fundamental formulas**

$$Z_n = \frac{1 + \Gamma_L}{1 - \Gamma_L} \Rightarrow \Gamma_L = \frac{Z_n - 1}{Z_n + 1}$$

- **Impact of inverting the impedance**

$$Z_n \rightarrow 1/Z_n \Rightarrow \Gamma_L \rightarrow -\Gamma_L$$

- **Derivation:**

$$\frac{1/Z_n - 1}{1/Z_n + 1} = \frac{1 - Z_n}{1 + Z_n} = -\left(\frac{Z_n - 1}{Z_n + 1}\right)$$

- **We can invert complex impedances in Γ plane by simply changing the sign of Γ !**

- **How can we best exploit this?**


The Smith Chart as a Calculator for Matching Networks

- Consider constructing both impedance and admittance curves on Smith chart


$$Z_n \rightarrow 1/Z_n \Rightarrow \Gamma_L \rightarrow -\Gamma_L$$

- Conductance curves derived from resistance curves
- Susceptance curves derived from reactance curves
- For series circuits, work with impedance
 - Impedances add for series circuits
- For parallel circuits, work with admittance
 - Admittances add for parallel circuits

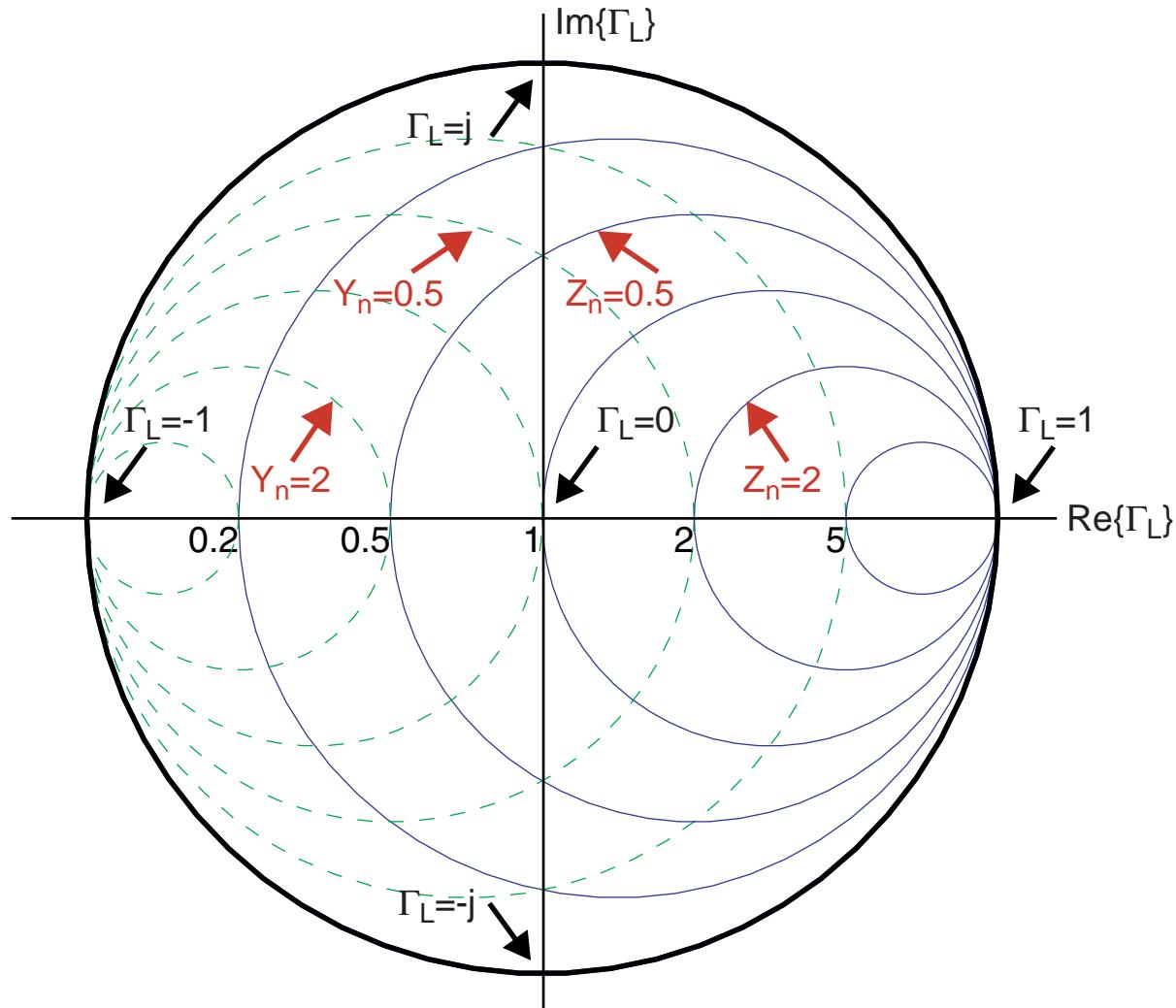
Resistance and Conductance on the Smith Chart



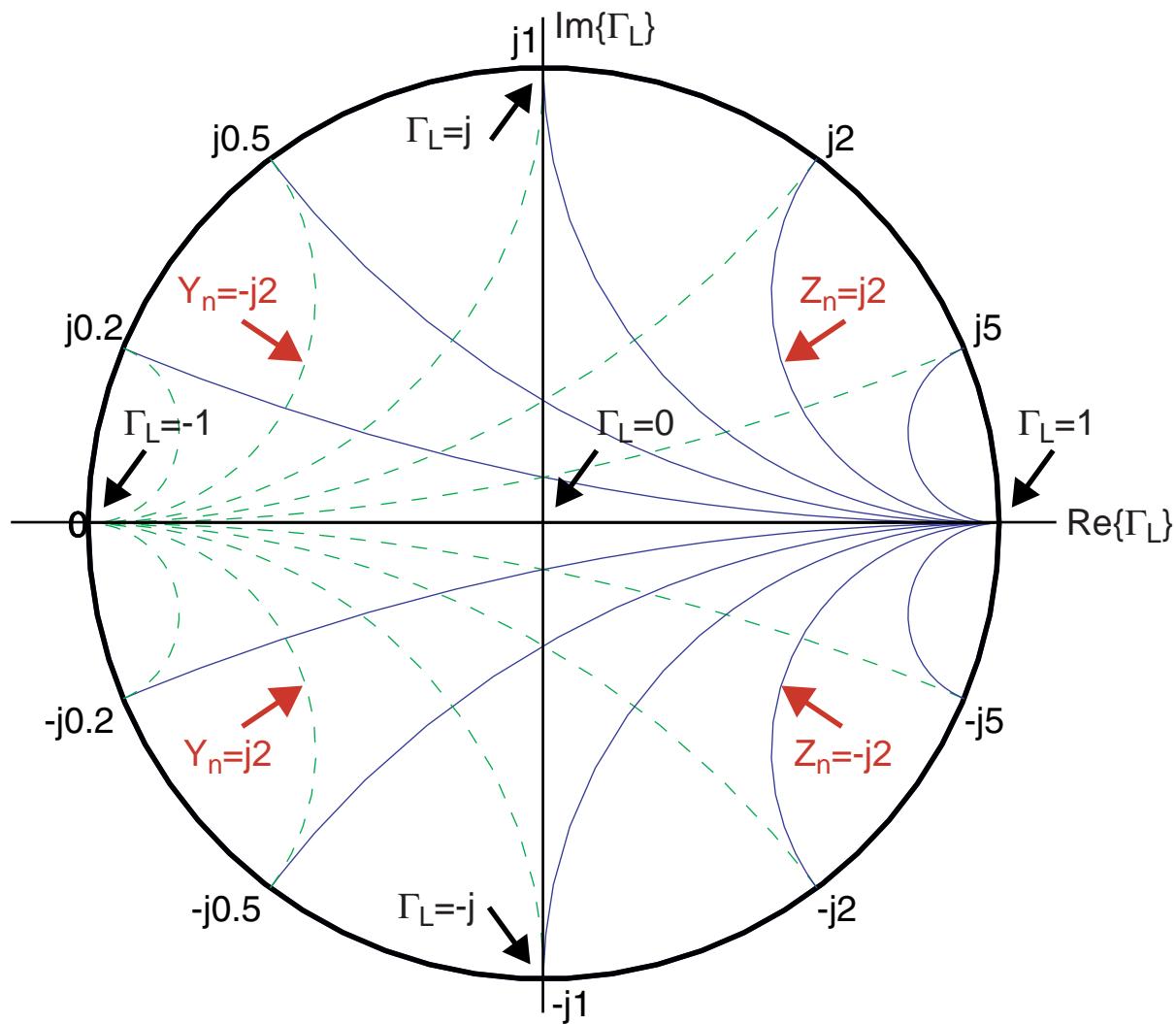
Reactance and Susceptance on the Smith Chart




Overall Smith Chart

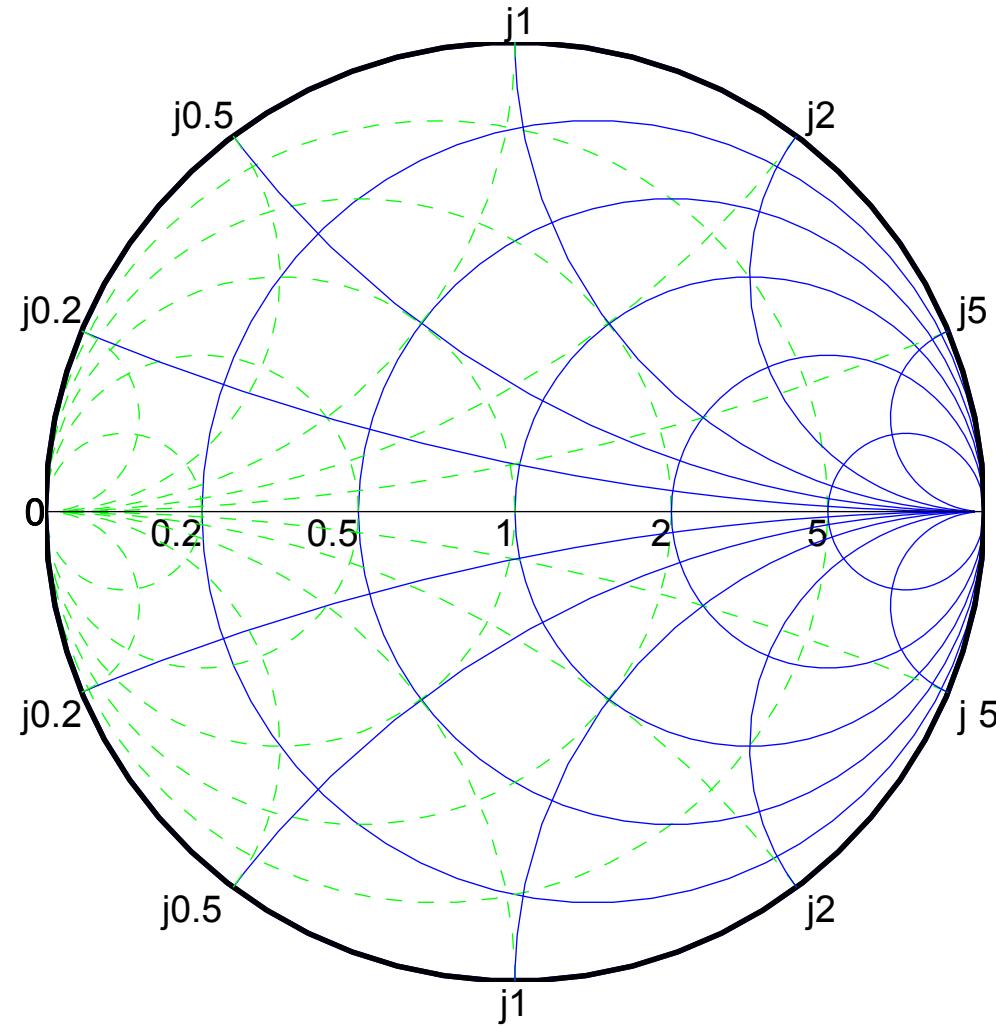


Smith Chart element Paths

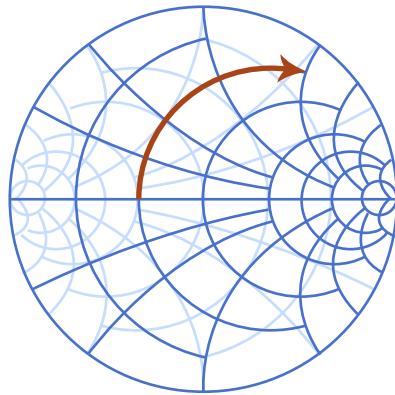


INCREASING SERIES L

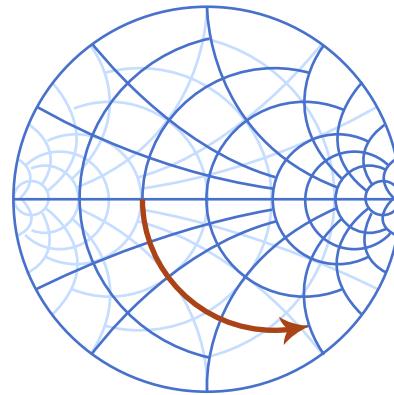

DECREASING SERIES C

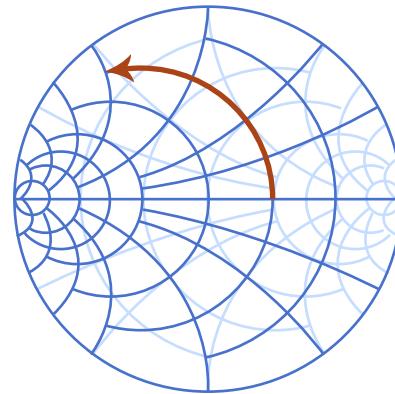


DECREASING SHUNT L

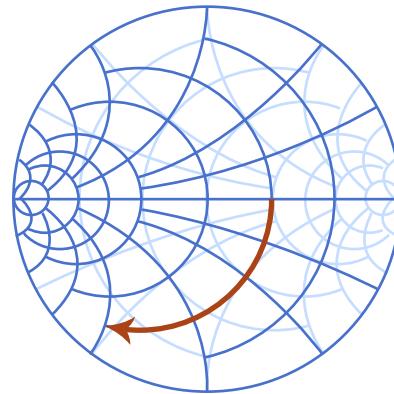

INCREASING SHUNT C

Figure by MIT OCW. Adapted from
<http://contact.tm.agilent.com/Agilent/tmo/an-95-1/classes/imatch.html>

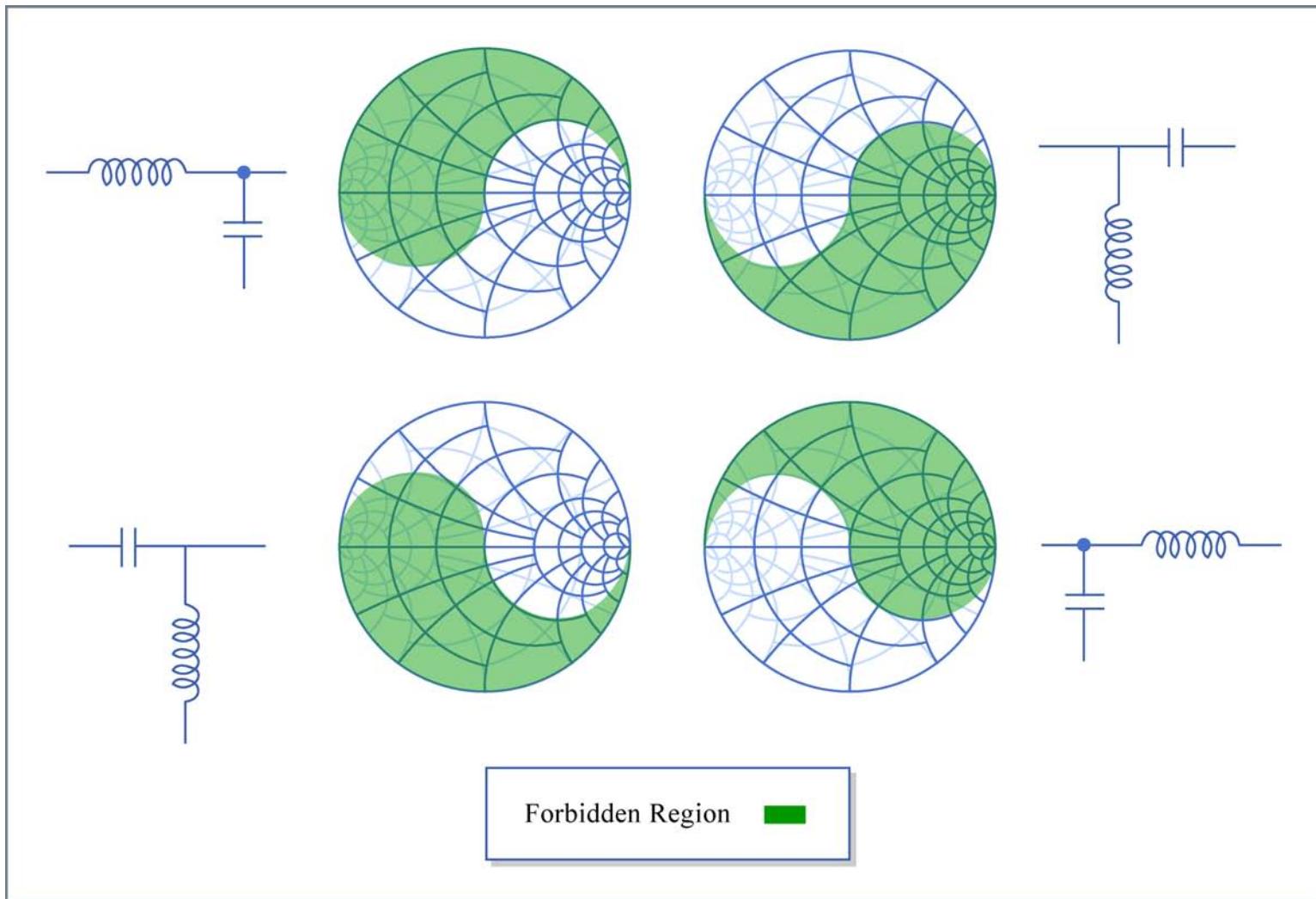L-Match Circuits (Matching Load to Source)




π or L match networks
remove forbidden regions

Figure by MIT OCW. Adapted from
<http://contact.tm.agilent.com/Agilent/tmo/an-95-1/classes/imatch.html>

Example – Match RC Network to 50 Ohms at 2.5 GHz

- Circuit

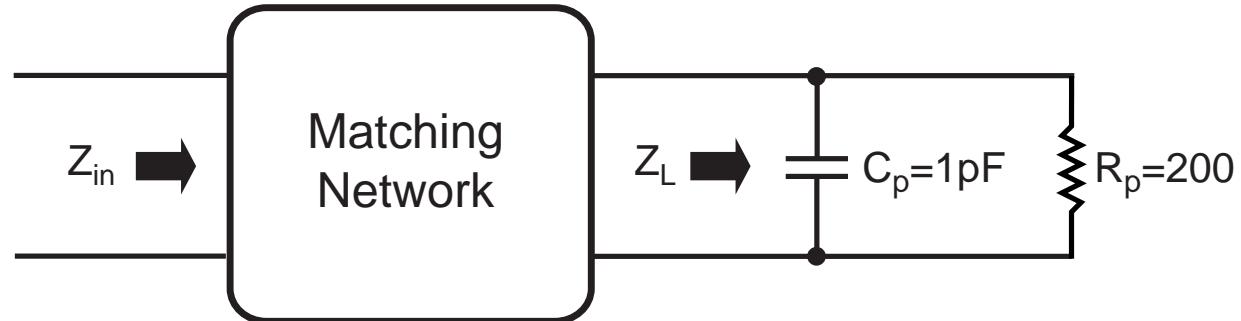


- Step 1: Calculate Z_{Ln}

$$\begin{aligned}Z_{Ln} &= \frac{Z_L}{Z_o} = \frac{R_L||(1/jwC)}{50} = \frac{1}{50(1/R_L + jwC)} \\&= \frac{1}{50(1/200 + j2\pi(2.5e9)10^{-12})} = \frac{1}{0.25 + j.7854}\end{aligned}$$

- Step 2: Plot Z_{Ln} on Smith Chart (use admittance, Y_{Ln})

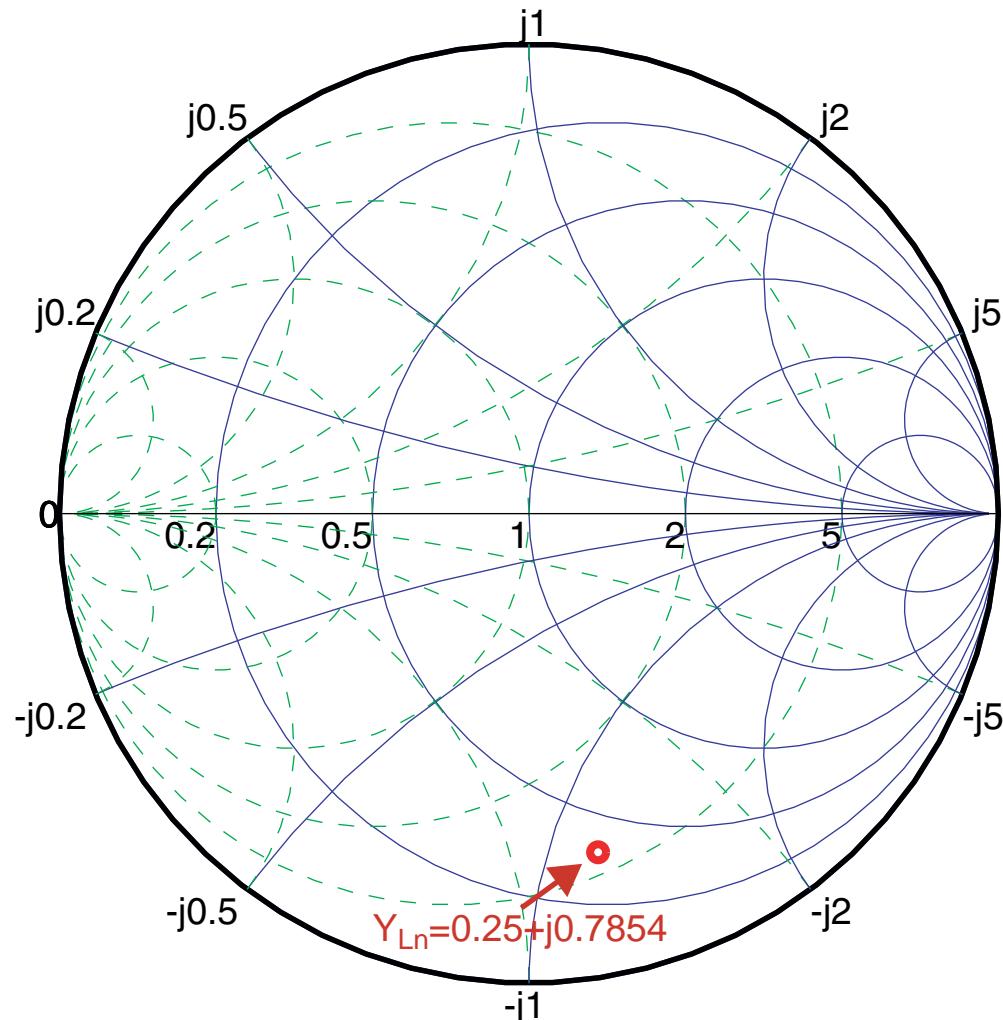
Plot Starting Impedance (Admittance) on Smith Chart



(Note: $Z_{L_n} = 0.37 - j1.16$)


Develop Matching “Game Plan” Based on Smith Chart

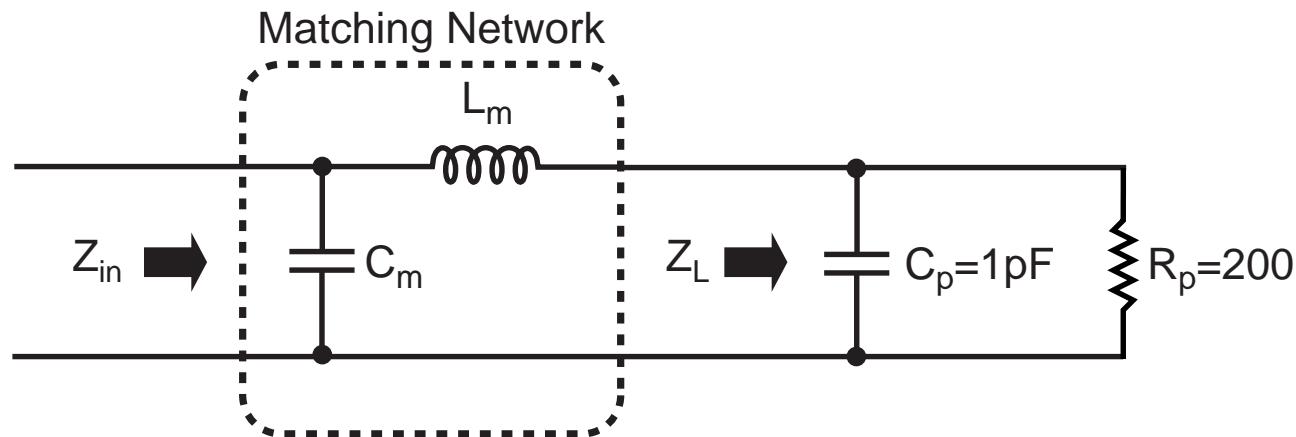- By inspection, we see that the following matching network can bring us to $Z_{in} = 50 \text{ Ohms}$ (center of Smith chart)-need to *step up* impedance



- Use the Smith chart to come up with component values
 - Inductance L_m shifts impedance up along reactance curve
 - Capacitance C_m shifts impedance down along susceptance curve

Add Reactance of Inductor L_m

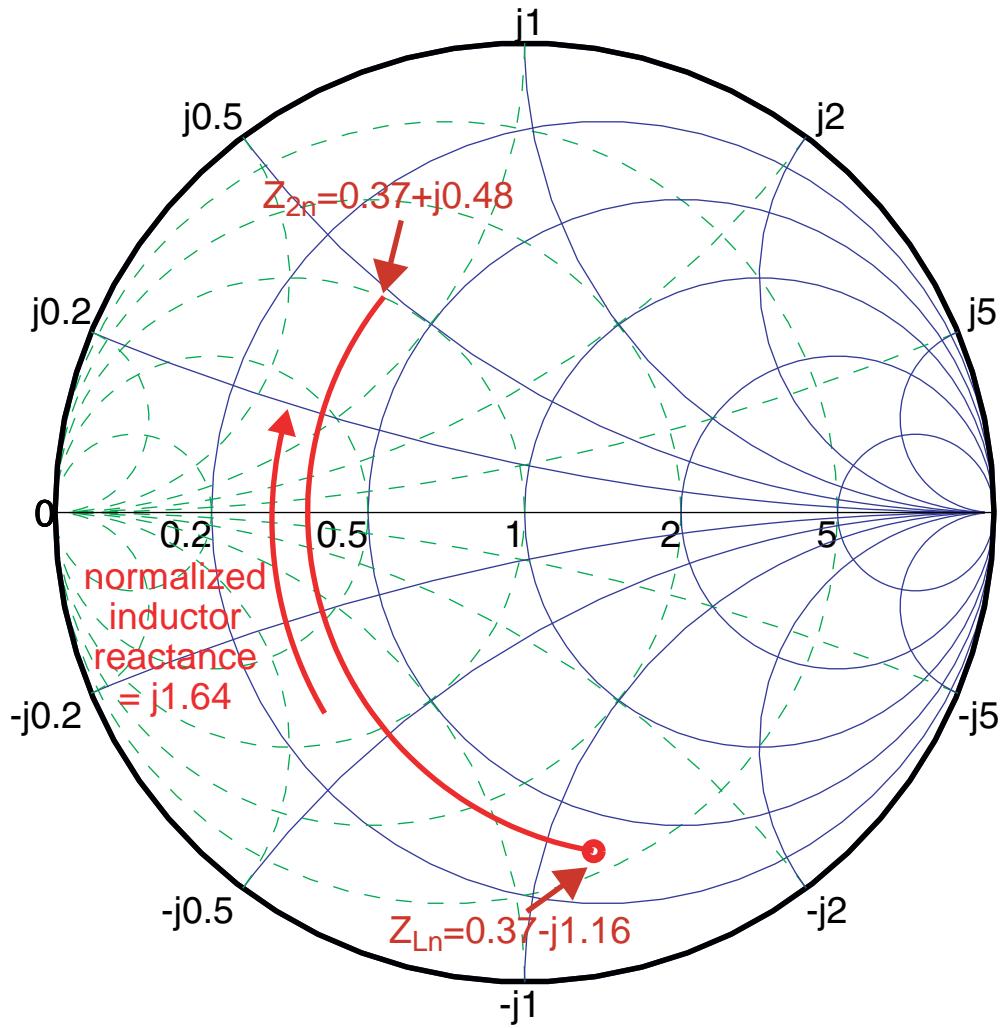

Inductor Value Calculation Using Smith Chart


- From Smith chart, we found that the desired normalized inductor reactance is

$$\frac{jwL_m}{Z_o} = \frac{jwL_m}{50} = j1.64$$

- Required inductor value is therefore

$$\Rightarrow L_m = \frac{50(1.64)}{2\pi 2.5e9} = 5.2nH$$

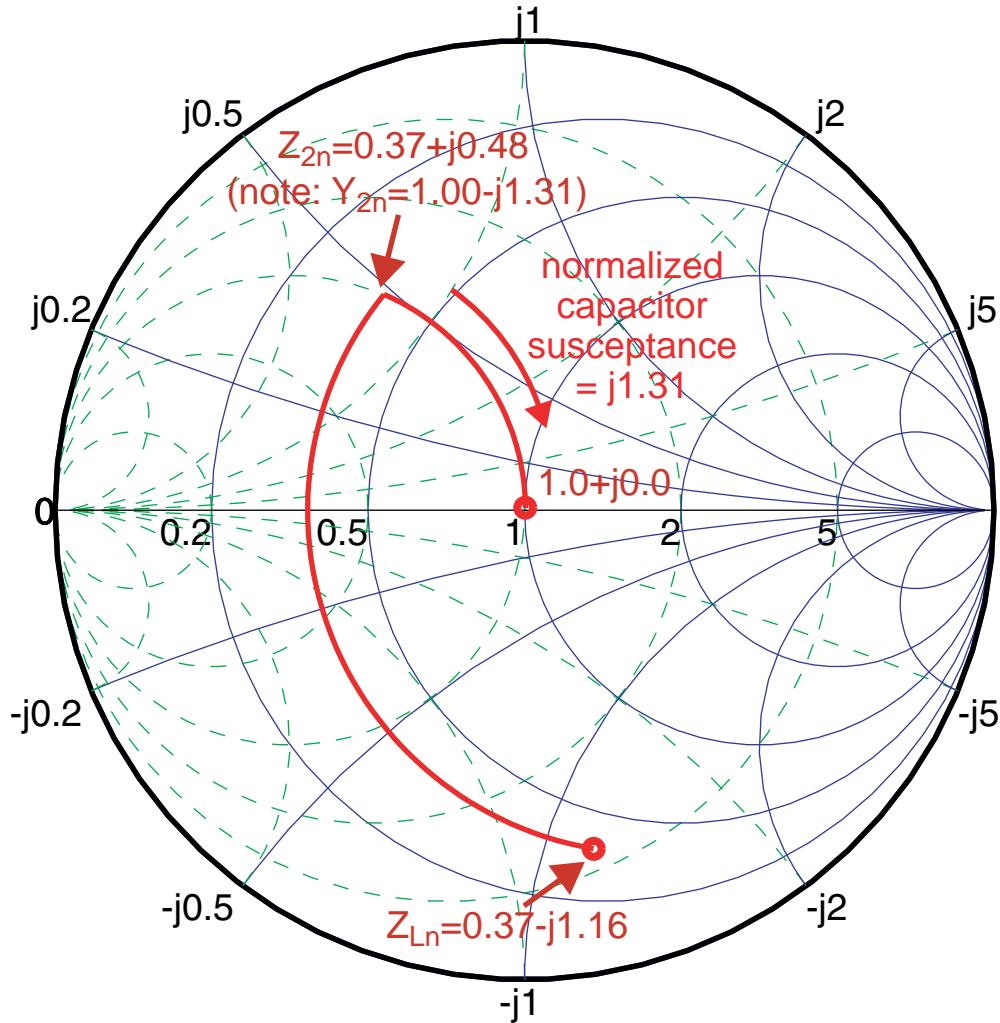Add Susceptance of Capacitor C_m (Achieves Match!)



Capacitor Value Calculation Using Smith Chart

- From Smith chart, we found that the desired normalized capacitor susceptance is

$$Z_0 j w C_m = 50 j w C_m = j 1.31$$

- Required capacitor value is therefore

$$\Rightarrow C_m = \frac{1.31}{50(2\pi 2.5e9)} = 1.67 pF$$

Useful Web Resource

- Play the “matching game” at

<http://contact.tm.agilent.com/Agilent/tmo/an-95-1/classes/imatch.html>

- Allows you to graphically tune several matching networks
- Note: it is set up to match **source** impedance to load impedance rather than match the load to the source impedance
 - Same results, just different viewpoint